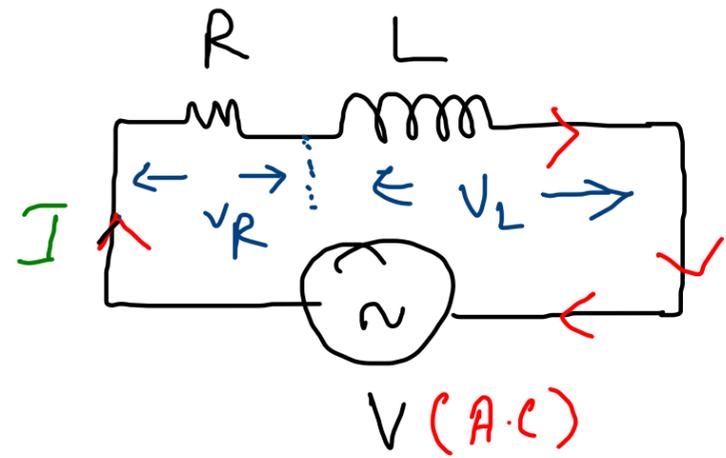


Series A.C Circuit (R-L Circuit)





$V =$ R.M.S value of applied voltage
 $I =$ R.M.S current.



$V = V_m \sin \omega t$, $V_{rms} = \frac{V_m}{\sqrt{2}}$

where V_m is the maximum value of the wave.



Same current flow throughout the circuit

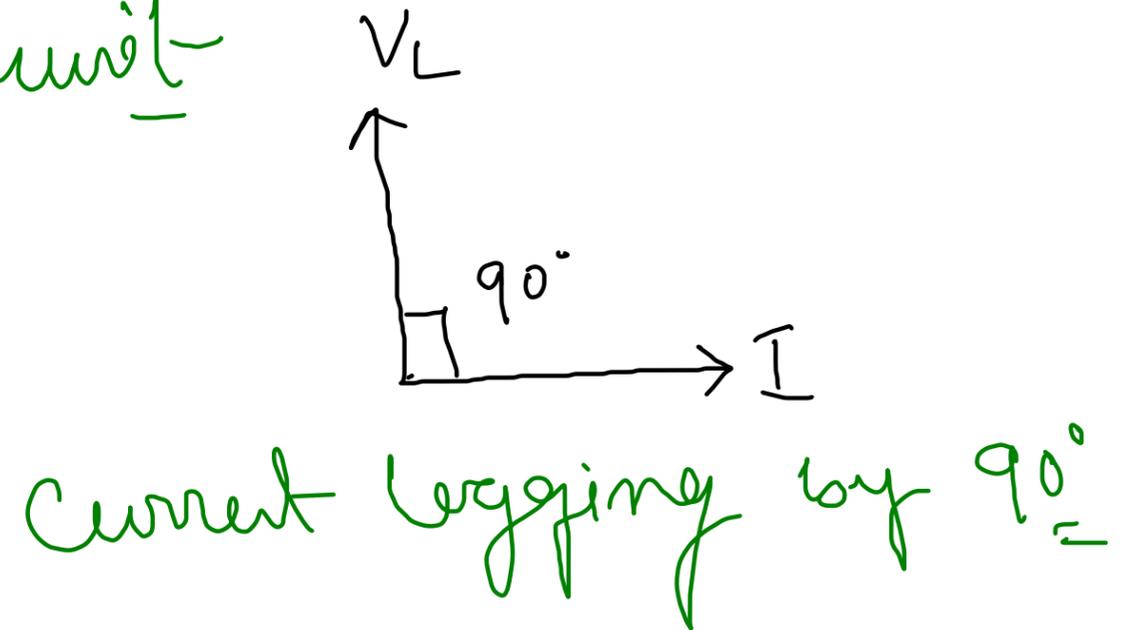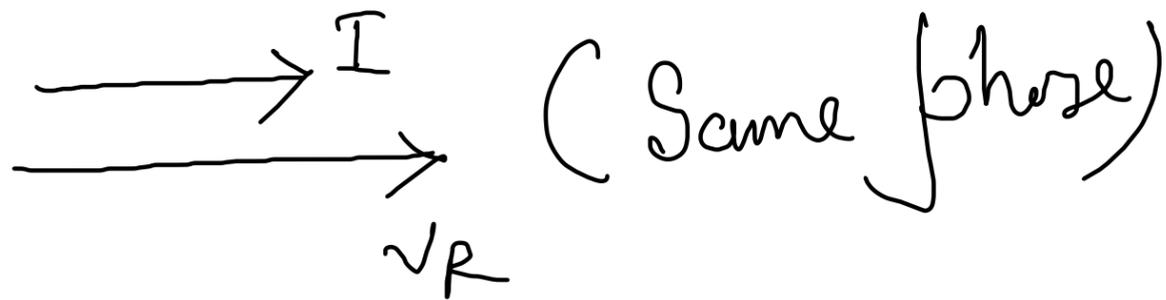


Phasor Diagram:-

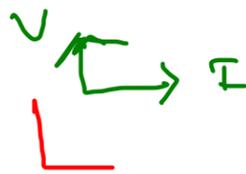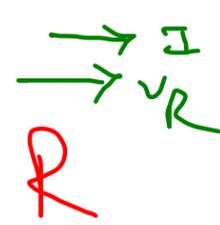

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

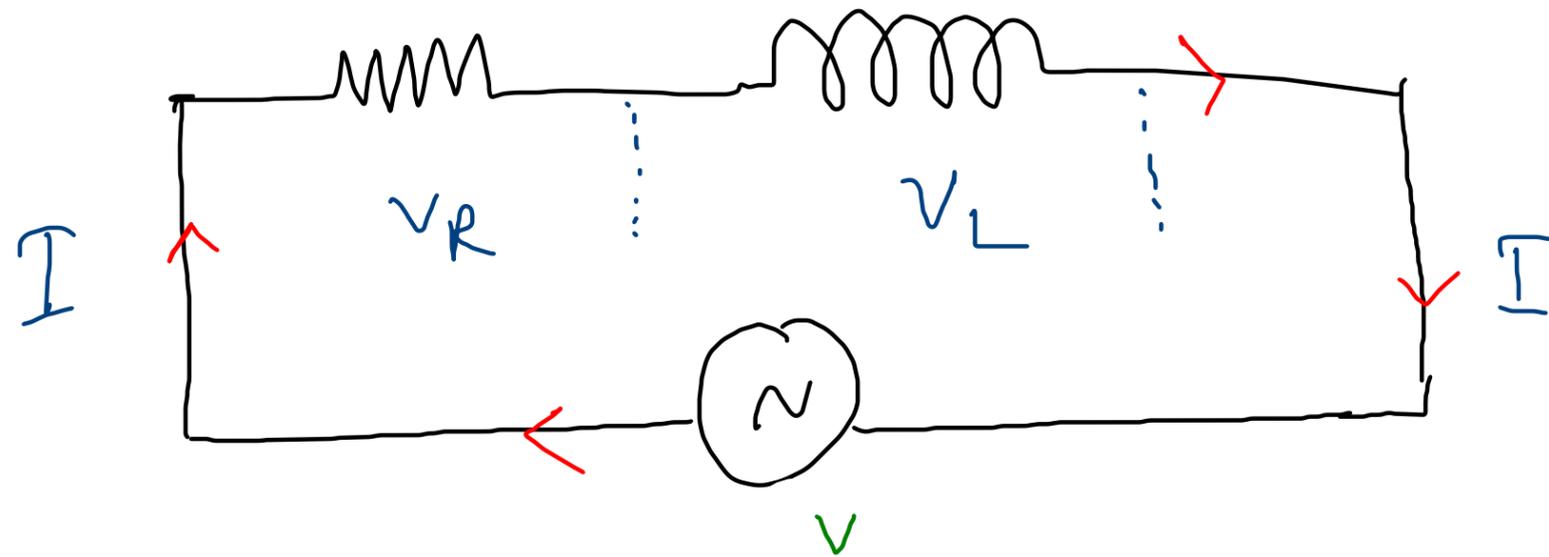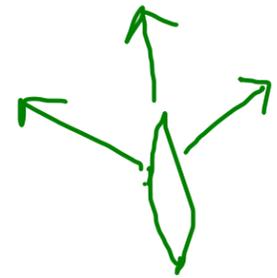

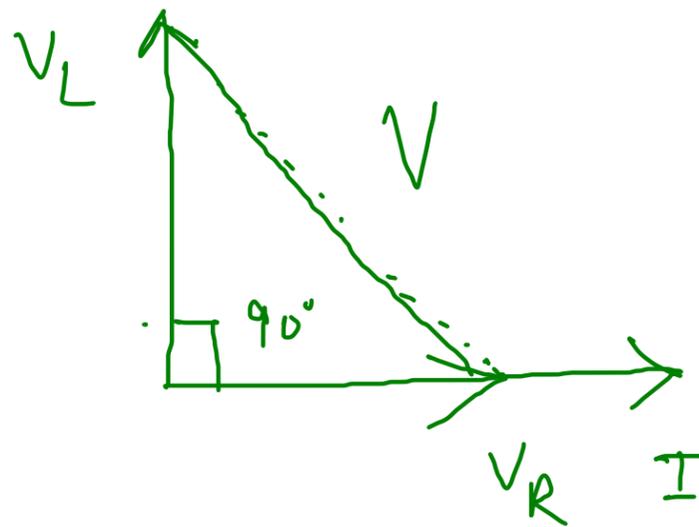Reference value. Should be the common quantity to the all components.




$$V^2 = V_L^2 + V_R^2 \quad (*)$$

$$\Rightarrow V = \sqrt{V_L^2 + V_R^2}$$

(*) Phasor algebra =

Phasor Diagram:-

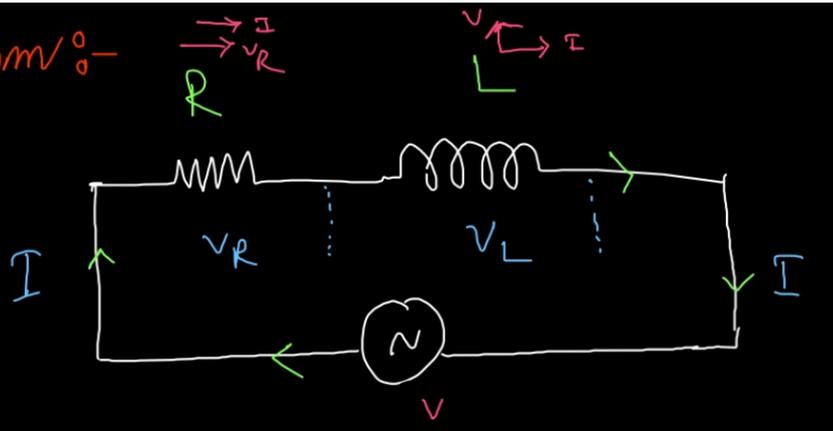

Calculations:-

$$V = \sqrt{V_R^2 + V_L^2}$$

I

Ohm's law

R, L \Rightarrow Impedance (Z)

$$V = I Z \otimes$$

R = Resistance
 X_L = Reactance

$$Z = \sqrt{R^2 + X_L^2}$$


X_L unit in ohm (Ω)

$$V = IZ$$

$$\Rightarrow V = I \sqrt{R^2 + X_L^2}$$

$$\Rightarrow I = \frac{V}{\sqrt{R^2 + X_L^2}}$$

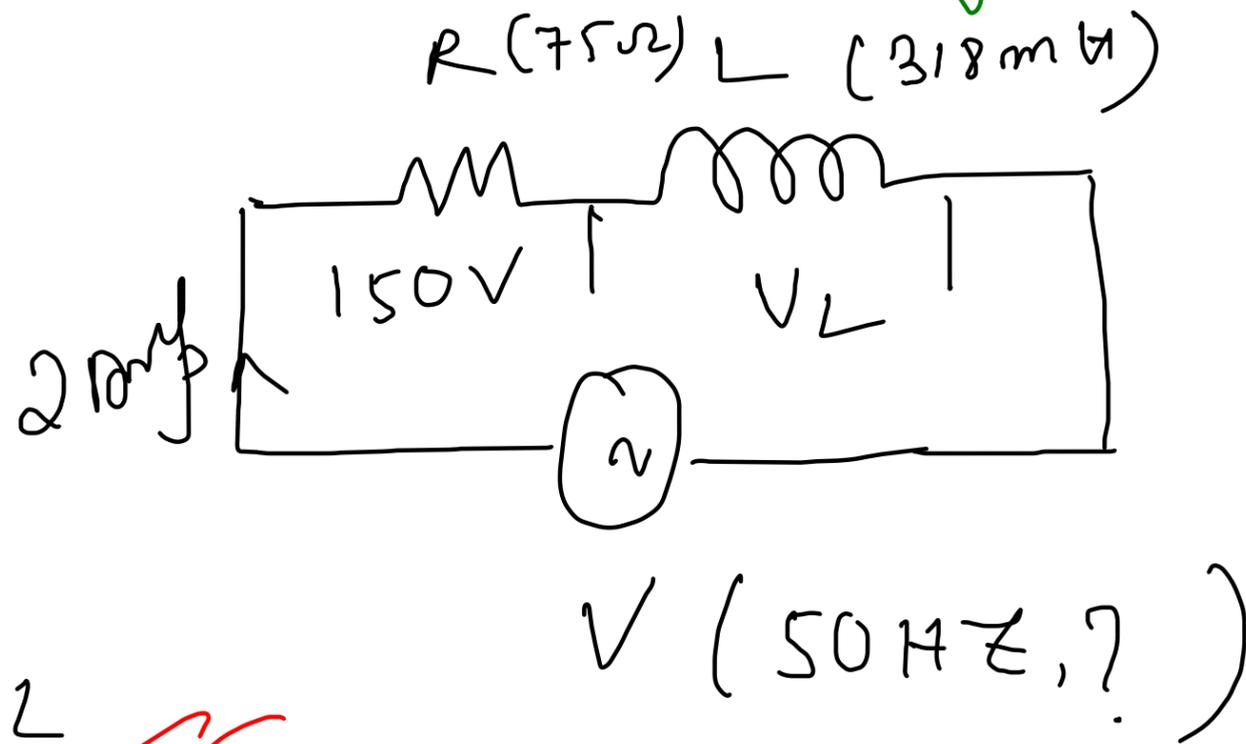Q1) A pure Inductor of 318 mH is connected in series with a pure resistance of 75Ω . The circuit is supplied from 50 Hz source and the voltage across 75Ω resistor is found to be 150 V . Calculate the supply voltage and phase angle.



$$V_R = 150 \text{ V}, R = 75 \Omega$$

$$V_R = IR$$

$$\Rightarrow 150 = I \times 75$$

$$\Rightarrow I = 2 \text{ Amp}$$

$$V_L = I \times X_L$$

$$X_L = \omega L$$

$$(318 \text{ mH} = 318 \times 10^{-3} \text{ H})$$

$$\Rightarrow X_L = 2\pi fL$$

$$\Rightarrow X_L = 2\pi \times 50 \times 318 \times 10^{-3} \Omega$$

$$\Rightarrow X_L = 99.90 \underline{\underline{\Omega}}$$

$$V_L = I X_L$$

$$\Rightarrow V_L = 2 \times 99.90$$

$$\Rightarrow V_L = 199.80 \text{ V} \approx 200 \text{ V}$$

$$V = \sqrt{V_R^2 + V_L^2}$$


$$\Rightarrow V = \sqrt{150^2 + (99.80)^2}$$

$$\Rightarrow V = 249.84 \text{ V} \approx 250 \text{ V}$$

(Ans)


⇒ Phase Angle :-

Current is lagging

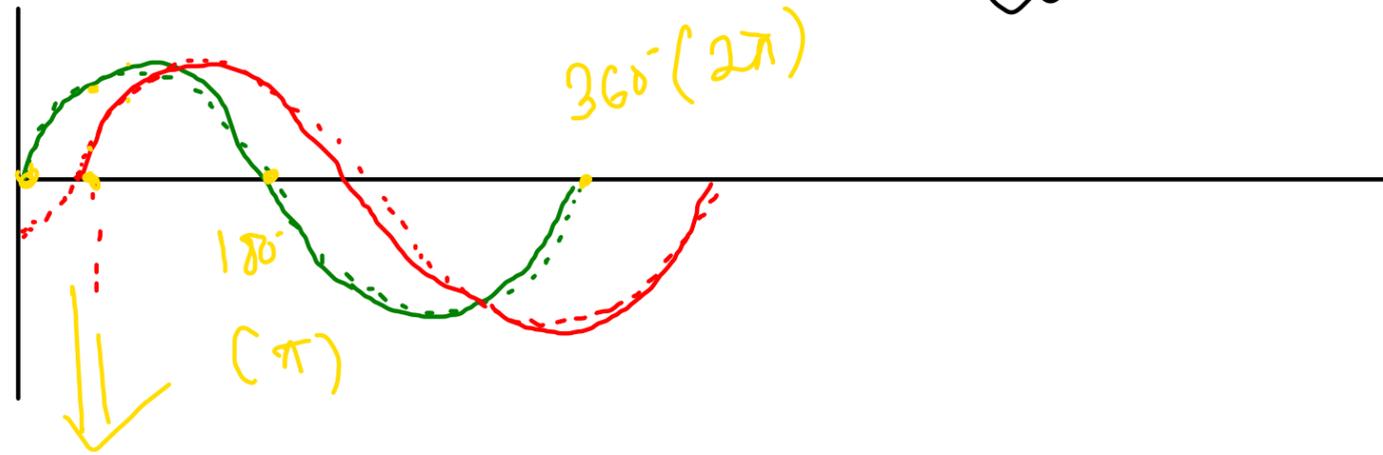


Phase angle = Angle between voltage and current.


(ϕ)

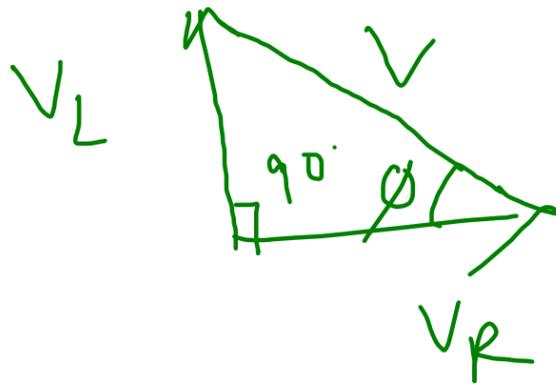
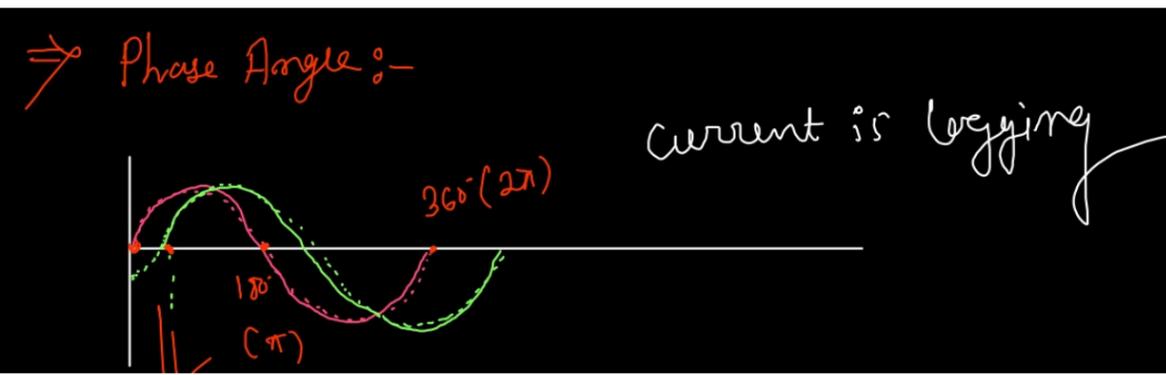
$$\begin{aligned} \tan \phi &= \frac{V_L}{V_R} \\ &= \frac{IX_2}{IR} = \frac{X_2}{R} \end{aligned}$$



⊗ Current lagging

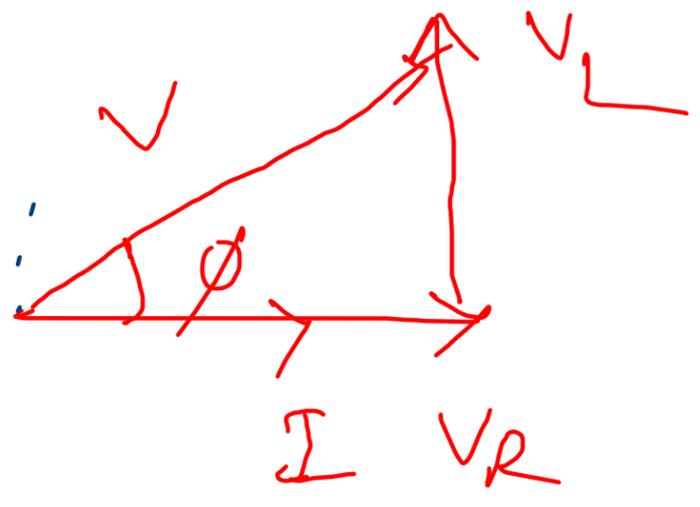

← lagging

$$v = V_m \sin \omega t$$

$$i = I_m \sin (\omega t - \phi)$$

$$\tan \phi = \frac{V_L}{V_R}$$

$$\Rightarrow \phi = \tan^{-1} \frac{V_L}{V_R}$$

$$V_R = 150 \text{ V} \quad V_L = 200 \text{ V}$$

$$\begin{aligned} \phi &= \tan^{-1} \frac{200}{150} \\ &= 53.13^\circ \end{aligned}$$

$$\tan \phi = \frac{X_L}{R}$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$

$$\begin{aligned} \phi &= \tan^{-1} \frac{100}{75} \\ &= \tan^{-1} 100/75 \\ &= 53.13^\circ \end{aligned}$$

Impedance :-
alternating

The Total opposition offered to the flow of current by a circuit called impedance.

$$Z = \sqrt{R^2 + X_2^2}$$

$$\text{where } X_2 = \omega L \\ = 2\pi fL$$

Admittance $\rightarrow Y = \frac{1}{Z}$

Siemens (S) \sim

Power :-

Instantaneous power

$$P = vi$$


$$= V_m \sin \omega t \quad I_m \sin (\omega t - \phi)$$

$\frac{1}{2} V_m I_m \cos \phi$: Average power

$$= \frac{1}{2} V_m I_m \cos \phi$$

$\frac{1}{2} V_m I_m \cos (2\omega t - \phi)$ ~~X~~

= Pulsating power
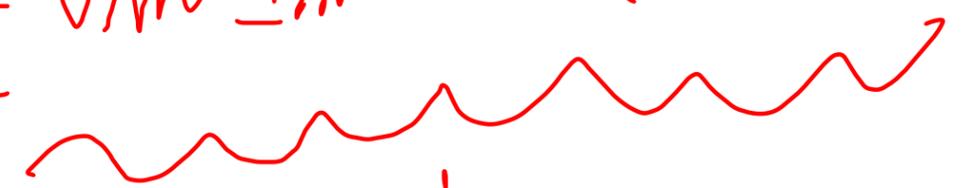
$$- \frac{1}{2} V_m I_m \cos (2\omega t - \phi)$$




Zero for one complete cycle.

$$\begin{aligned}\therefore \text{Average power} &= \frac{1}{2} V_m I_m \cos \phi \\ &= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi\end{aligned}$$

$$A.P(\phi) = V_{rms} I_{rms} \cos \phi$$

$$P = VI \cos \phi$$