
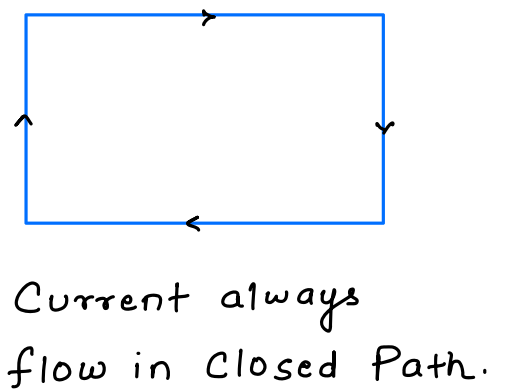
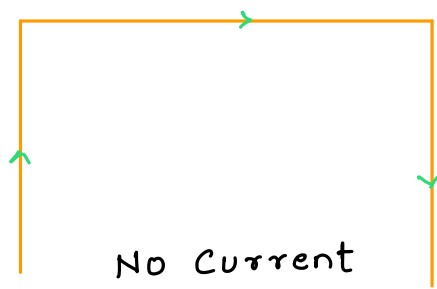
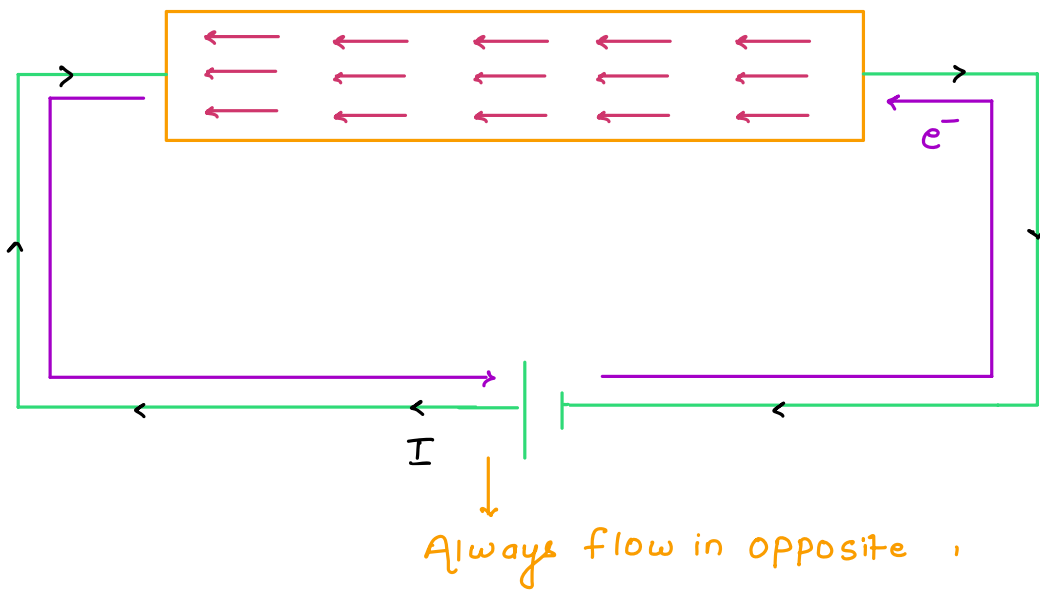


Electric Current :- Flow of Electrons

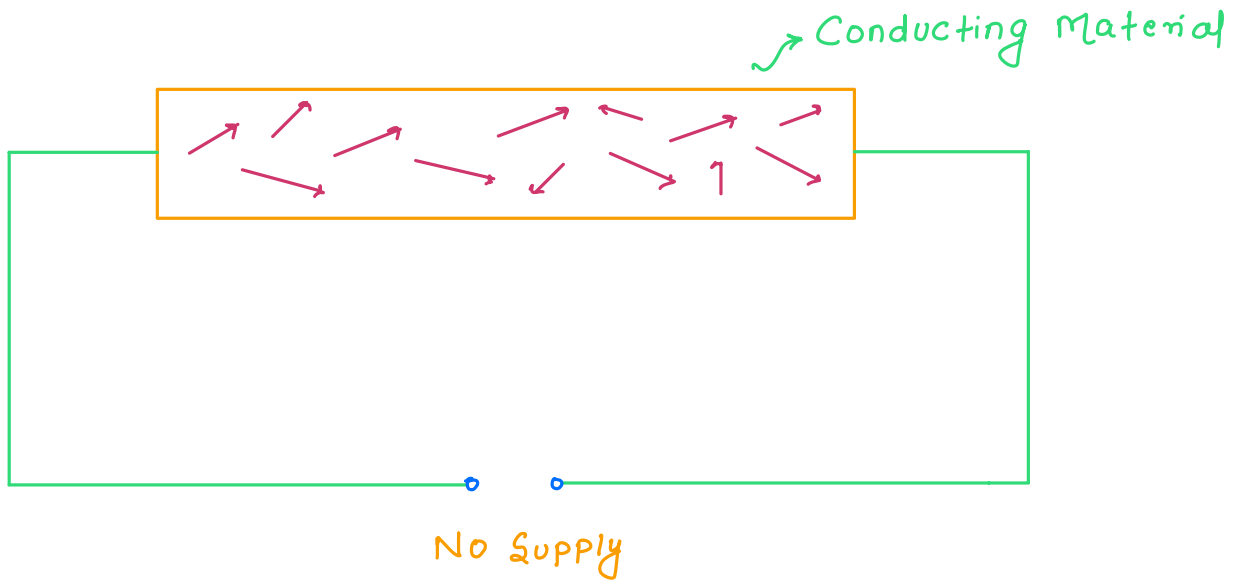

$$I = \frac{q}{t} \rightarrow \text{Charge (unit Coulomb)}$$

$$t \rightarrow \text{Time (unit Second)}$$

Charge flow per unit time

$$\text{Unit of Current} = \frac{\text{Coulomb}}{\text{Sec}} \quad \text{C/s} = \text{Ampere}$$

Ex:-

$$q = ? \quad I = 0.5 \text{ A} \quad t = 10 \text{ mins}$$

$$10 \times 60 = 600 \text{ Sec}$$

$$q = It$$

$$q = 0.5 \times \frac{600}{10} = 300 \text{ C}$$

Ans

$$q = ne$$

Charge of electron = $-1.6 \times 10^{-19} \text{ C}$

$$1 = n \times 1.6 \times 10^{-19}$$

$$n = \frac{1}{1.6 \times 10^{-19}} = 0.625 \times 10^{19}$$

Ans

Electric potential & Potential difference



$$V = \frac{W}{q}$$

unit = Joule/Coulomb
or Volt

Work done in moving unit positive charge from one point to other is called Potential difference

Potential Difference measured by Voltmeter

↓
Connected in parallel

Current is measured by Ammeter

↓
Connected in series

Q

$$Q = 2C \quad W = ? \quad V = 12V$$


$$V = \frac{W}{Q}$$

$$W = VQ$$

$$W = 2 \times 12 = 24J$$

~~Q~~

OHM'S LAW :-

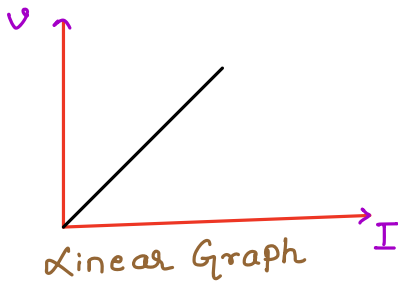

$V \propto I \rightarrow$ At Constant temperature

$$\boxed{V = RI}$$

↓
Constant



Resistance :- property of Conductor which Resist the flow of current

Unit \rightarrow ohms (Ω)


$$\boxed{\text{Current} \propto \frac{1}{\text{Resistance}}}$$

$$R = \frac{V}{I}$$

Rheostat is used to change Resistance of Circuit

Combination of Resistance :-

SERIES COMBINATION

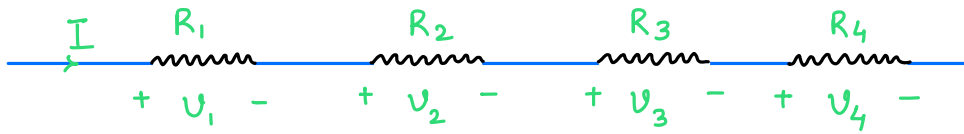

Series \rightarrow Current Same

$$V = V_1 + V_2 + V_3 + V_4$$

$$V = IR_1 + IR_2 + IR_3 + IR_4$$

$$V = I(R_1 + R_2 + R_3 + R_4)$$


$$V = I R_{eqv}$$

$$R_{eqv} = R_1 + R_2 + R_3 + R_4$$

Resistance gets Added

PARALLEL COMBINATION

Voltage Same

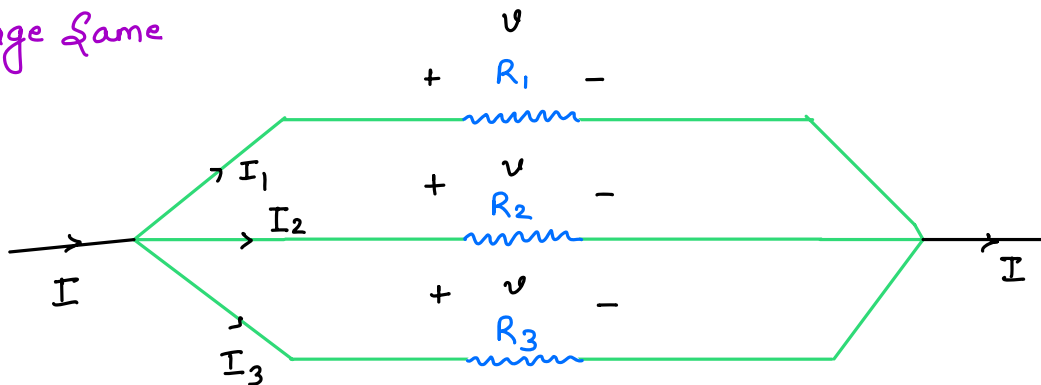

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$I = V R_{eqv}$$

$$R_{eqv} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Heating Effect of Current



$$H = I^2 R t$$

$$H = P t$$

$$H = \frac{V^2}{R} t$$

$$H = V I t$$

Electric power :- work done per unit time

$$P = \frac{W}{t}$$

unit \rightarrow Joule/sec = watt

$$P = V I$$

$$V = I R$$

$$P = I R \cdot I = I^2 R$$

$$P = V \cdot \frac{V}{R} = \frac{V^2}{R}$$

$$P = V I = I^2 R = \frac{V^2}{R}$$