

# Alternating Current




Visit : <https://bit.ly/next-v-a-p> or scan the given QR Code for video solutions of questions.



## 7.2 AC Voltage Applied to a Resistor

- The peak voltage of the ac source is equal to
  - the value of voltage supplied to the circuit
  - the rms value of the source
  - $\sqrt{2}$  times the rms value of the ac source
  - $1/\sqrt{2}$  times the rms value of the ac source

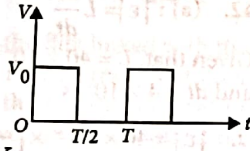(2022)
- The r.m.s. value of potential difference  $V$  shown in the figure is
 
  - $\frac{V_0}{\sqrt{3}}$
  - $\frac{V_0}{2}$
  - $\frac{V_0}{\sqrt{2}}$
  - $\frac{V_0}{2}$






(Mains 2011)
- In an A.C. circuit,  $I_{\text{rms}}$  and  $I_0$  are related as
  - $I_{\text{rms}} = \pi I_0$
  - $I_{\text{rms}} = \sqrt{2} I_0$
  - $I_{\text{rms}} = I_0 / \pi$
  - $I_{\text{rms}} = I_0 / \sqrt{2}$

(1994)
- Two cables of copper are of equal lengths. One of them has a single wire of area of cross-section  $A$ , while other has 10 wires of cross-sectional area  $A/10$  each. Give their suitability for transporting A.C. and D.C.
  - only multiple strands for A.C., either for D.C.
  - only multiple strands for A.C., only single strand for D.C.
  - only single strand for D.C., either for A.C.
  - only single strand for A.C., either for D.C.

(1994)


## 7.4 AC Voltage Applied to an Inductor

- A coil of self-inductance  $L$  is connected in series with a bulb  $B$  and an AC source. Brightness of the bulb decreases when
- a capacitance of reactance  $X_C = X_L$  is included in the same circuit.
  - an iron rod is inserted in the coil.
  - frequency of the AC source is decreased.
  - number of turns in the coil is reduced.
- (2013)

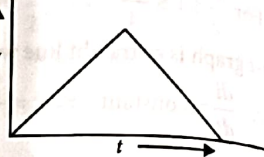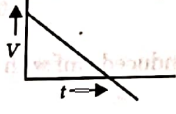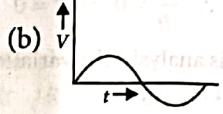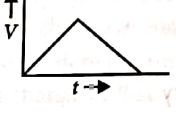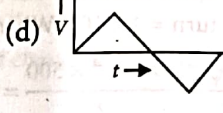- The current  $I$  in an A.C. circuit with inductance coil varies with time according to the graph given below. Which one of the following graphs gives the variation of voltage with time?
 
  - 
  - 
  - 
  - 

(1994)

## 7.5 AC Voltage Applied to a Capacitor

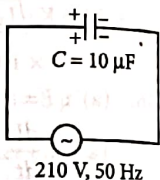- A  $10 \mu\text{F}$  capacitor is connected to a  $210 \text{ V}$ ,  $50 \text{ Hz}$  source as shown in figure. The peak current in the circuit is nearly ( $\pi = 3.14$ )
 
  - $0.58 \text{ A}$
  - $0.93 \text{ A}$
  - $1.20 \text{ A}$
  - $0.35 \text{ A}$

(2024)
- A  $40 \mu\text{F}$  capacitor is connected to a  $200 \text{ V}$ ,  $50 \text{ Hz}$  ac supply. The r.m.s value of the current in the circuit is, nearly
  - $1.7 \text{ A}$
  - $2.05 \text{ A}$
  - $2.5 \text{ A}$
  - $25.1 \text{ A}$

(2020)
- A small signal voltage  $V(t) = V_0 \sin \omega t$  is applied across an ideal capacitor  $C$ 
  - Current  $I(t)$  is in phase with voltage  $V(t)$ .
  - Current  $I(t)$  leads voltage  $V(t)$  by  $180^\circ$ .
  - Current  $I(t)$ , lags voltage  $V(t)$  by  $90^\circ$ .
  - Over a full cycle the capacitor  $C$  does not consume any energy from the voltage source.

(NEET-I 2016)
- In an ac circuit an alternating voltage  $200\sqrt{2} \sin 100t$  volts is connected to a capacitor of capacity  $1 \mu\text{F}$ . The r.m.s. value of the current in the circuit is
  - $10 \text{ mA}$
  - $100 \text{ mA}$
  - $200 \text{ mA}$
  - $20 \text{ mA}$

(2011)




Alternating Current

A capacitor of capacity  $C$  has reactance  $X$ . If capacitance and frequency become double then reactance will be  
(a)  $4X$  (b)  $X/2$  (c)  $X/4$  (d)  $2X$  (2001)
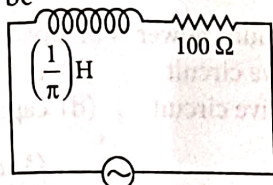
### 7.6 AC Voltage Applied to a Series LCR Circuit


An ac source is connected in the given circuit. The value of  $\phi$  will be



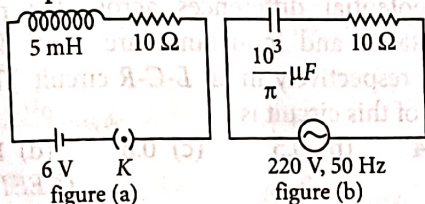- (a)  $60^\circ$  (b)  $90^\circ$   
(c)  $30^\circ$  (d)  $45^\circ$

(Manipur NEET 2023)


If  $Z_1$  and  $Z_2$  are the impedances of the given circuits (a) and (b) as shown in figures, then choose the correct option



- (a)  $Z_1 < Z_2$  (b)  $Z_1 + Z_2 = 20 \Omega$   
(c)  $Z_1 = Z_2$  (d)  $Z_1 > Z_2$

(Manipur NEET 2023)

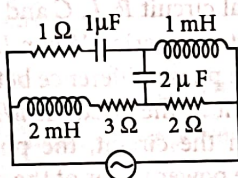4. For very high frequencies, the effective impedance of the circuit (shown in the figure) will be




- (a)  $4 \Omega$  (b)  $6 \Omega$   
(c)  $1 \Omega$  (d)  $3 \Omega$

(Manipur NEET 2023)

15. In a series LCR circuit, the inductance  $L$  is  $10 \text{ mH}$ , capacitance  $C$  is  $1 \mu\text{F}$  and resistance  $R$  is  $100 \Omega$ . The frequency at which resonance occurs is

- (a)  $1.59 \text{ rad/s}$  (b)  $1.59 \text{ kHz}$   
(c)  $15.9 \text{ rad/s}$  (d)  $15.9 \text{ kHz}$  (2023)

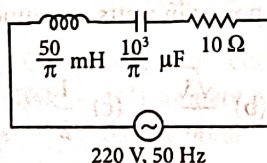16. The net impedance of circuit (as shown in figure) will be



- (a)  $5\sqrt{5} \Omega$  (b)  $25 \Omega$   
(c)  $10\sqrt{2} \Omega$  (d)  $15 \Omega$  (2023)

17. A series LCR circuit with inductance  $10 \text{ H}$ , capacitance  $10 \mu\text{F}$ , resistance  $50 \Omega$  is connected to an ac source of voltage,  $V = 200\sin(100t)$  volt. If the resonant frequency of the LCR circuit is  $\nu_0$  and the frequency of the ac source is  $\nu$ , then


- (a)  $\nu_0 = \nu = 50 \text{ Hz}$  (b)  $\nu_0 = \nu = \frac{50}{\pi} \text{ Hz}$   
(c)  $\nu_0 = \frac{50}{\pi} \text{ Hz}$ ,  $\nu = 50 \text{ Hz}$   
(d)  $\nu = 100 \text{ Hz}$ ,  $\nu_0 = \frac{100}{\pi} \text{ Hz}$  (2022)

18. A series LCR circuit containing  $5.0 \text{ H}$  inductor,  $80 \mu\text{F}$  capacitor and  $40 \Omega$  resistor is connected to  $230 \text{ V}$  variable frequency ac source. The angular frequencies of the source at which power transferred to the circuit half the power at the resonant angular frequency are likely to be

- (a)  $42 \text{ rad/s}$  and  $58 \text{ rad/s}$  (b)  $25 \text{ rad/s}$  and  $75 \text{ rad/s}$   
(c)  $50 \text{ rad/s}$  and  $25 \text{ rad/s}$  (d)  $46 \text{ rad/s}$  and  $54 \text{ rad/s}$  (2021)

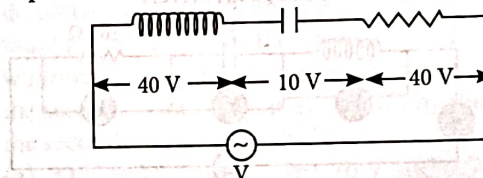19. An inductor of inductance  $L$ , a capacitor of capacitance  $C$  and a resistor of resistance ' $R$ ' are connected in series to an ac source of potential difference ' $V$ ' volts as shown in figure.

Potential difference across  $L$ ,  $C$  and  $R$  is  $40 \text{ V}$ ,  $10 \text{ V}$  and  $40 \text{ V}$ , respectively. The amplitude of current flowing through LCR series circuit is  $10\sqrt{2} \text{ A}$ . The impedance of the circuit is



- (a)  $5 \Omega$  (b)  $4\sqrt{2} \Omega$  (c)  $5/\sqrt{2} \Omega$  (d)  $4 \Omega$  (2021)

20. A series LCR circuit is connected to an ac voltage source. When  $L$  is removed from the circuit, the phase difference between current and voltage is  $\pi/3$ . If instead  $C$  is removed from the circuit, the phase difference is again  $\pi/3$  between current and voltage. The power factor of the circuit is

- (a) zero (b)  $0.5$   
(c)  $1.0$  (d)  $-1.0$  (2020)


21. A circuit when connected to an AC source of  $12 \text{ V}$  gives a current of  $0.2 \text{ A}$ . The same circuit when connected to a DC source of  $12 \text{ V}$ , gives a current of  $0.4 \text{ A}$ . The circuit is

- (a) series LR (b) series RC  
(c) series LC (d) series LCR

(Odisha NEET 2019)

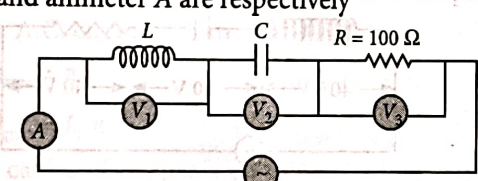22. Which of the following combinations should be selected for better tuning of an L-C-R circuit used for communication?



- (a)  $R = 20 \Omega$ ,  $L = 1.5 \text{ H}$ ,  $C = 35 \mu\text{F}$   
 (b)  $R = 25 \Omega$ ,  $L = 2.5 \text{ H}$ ,  $C = 45 \mu\text{F}$   
 (c)  $R = 15 \Omega$ ,  $L = 3.5 \text{ H}$ ,  $C = 30 \mu\text{F}$   
 (d)  $R = 25 \Omega$ ,  $L = 1.5 \text{ H}$ ,  $C = 45 \mu\text{F}$  (NEET-II 2016)
23. A series R-C circuit is connected to an alternating voltage source. Consider two situations :  
 (p) When capacitor is air filled.  
 (q) When capacitor is mica filled.  
 Current through resistor is  $i$  and voltage across capacitor is  $V$  then  
 (a)  $i_p > i_q$  (b)  $V_p = V_q$   
 (c)  $V_p < V_q$  (d)  $V_p > V_q$  (2015)
24. An ac voltage is applied to a resistance  $R$  and an inductor  $L$  in series. If  $R$  and the inductive reactance are both equal to  $3 \Omega$ , the phase difference between the applied voltage and the current in the circuit is  
 (a)  $\pi/6$  (b)  $\pi/4$  (c)  $\pi/2$  (d) zero (2011)
25. A coil has resistance  $30 \text{ ohm}$  and inductive reactance  $20 \text{ ohm}$  at  $50 \text{ Hz}$  frequency. If an ac source, of  $200 \text{ volt}$ ,  $100 \text{ Hz}$ , is connected across the coil, the current in the coil will be  
 (a)  $2.0 \text{ A}$  (b)  $4.0 \text{ A}$  (c)  $8.0 \text{ A}$  (d)  $\frac{20}{\sqrt{13}} \text{ A}$  (Mains 2011)
26. In the given circuit the reading of voltmeter  $V_1$  and  $V_2$  are  $300 \text{ volts}$  each. The reading of the voltmeter  $V_3$  and ammeter  $A$  are respectively
- 
- (a)  $150 \text{ V}$ ,  $2.2 \text{ A}$  (b)  $220 \text{ V}$ ,  $2.2 \text{ A}$   
 (c)  $220 \text{ V}$ ,  $2.0 \text{ A}$  (d)  $100 \text{ V}$ ,  $2.0 \text{ A}$  (2010)
27. What is the value of inductance  $L$  for which the current is maximum in a series LCR circuit with  $C = 10 \mu\text{F}$  and  $\omega = 1000 \text{ s}^{-1}$ ?  
 (a)  $1 \text{ mH}$   
 (b) cannot be calculated unless  $R$  is known  
 (c)  $10 \text{ mH}$  (d)  $100 \text{ mH}$  (2007)
28. In a circuit  $L$ ,  $C$  and  $R$  are connected in series with an alternating voltage source of frequency  $f$ . The current leads the voltage by  $45^\circ$ . The value of  $C$  is  
 (a)  $\frac{1}{\pi f(2\pi f L - R)}$  (b)  $\frac{1}{2\pi f(2\pi f L - R)}$   
 (c)  $\frac{1}{\pi f(2\pi f L + R)}$  (d)  $\frac{1}{2\pi f(2\pi f L + R)}$  (2005)
29. The value of quality factor is  
 (a)  $\frac{\omega L}{R}$  (b)  $\frac{1}{\omega RC}$  (c)  $\sqrt{LC}$  (d)  $L/R$  (2000)

30. A series L-C-R circuit is connected to a source of A.C. current. At resonance, the phase difference between the applied voltage and the current in the circuit, is  
 (a)  $\pi$  (b) zero (c)  $\pi/4$  (d)  $\pi/2$  (1994)

### 7.7 Power in AC Circuit : The Power Factor

31. The maximum power is dissipated for an ac in a/an  
 (a) resistive circuit (b) LC circuit  
 (c) inductive circuit (d) capacitive circuit (Manipur NEET 2023)
32. An inductor  $20 \text{ mH}$ , a capacitor  $100 \mu\text{F}$  and a resistor  $50 \Omega$  are connected in series across a source of emf,  $V = 10 \sin 314t$ . The power loss in the circuit is  
 (a)  $0.79 \text{ W}$  (b)  $0.43 \text{ W}$   
 (c)  $2.74 \text{ W}$  (d)  $1.13 \text{ W}$  (2018)
33. The potential differences across the resistance, capacitance and inductance are  $80 \text{ V}$ ,  $40 \text{ V}$  and  $100 \text{ V}$  respectively in an L-C-R circuit. The power factor of this circuit is  
 (a)  $0.4$  (b)  $0.5$  (c)  $0.8$  (d)  $1.0$  (NEET-II 2016)
34. An inductor  $20 \text{ mH}$ , a capacitor  $50 \mu\text{F}$  and a resistor  $40 \Omega$  are connected in series across a source of emf  $V = 10 \sin 340t$ . The power loss in A.C. circuit is  
 (a)  $0.76 \text{ W}$  (b)  $0.89 \text{ W}$   
 (c)  $0.51 \text{ W}$  (d)  $0.67 \text{ W}$  (NEET-I 2016)
35. In an electrical circuit  $R$ ,  $L$ ,  $C$  and ac voltage source are all connected in series. When  $L$  is removed from the circuit, the phase difference between the voltage and the current in the circuit is  $\pi/3$ . If instead,  $C$  is removed from the circuit, the phase difference is again  $\pi/3$ . The power factor of the circuit is  
 (a)  $\frac{1}{2}$  (b)  $\frac{1}{\sqrt{2}}$  (c)  $1$  (d)  $\frac{\sqrt{3}}{2}$  (2012)
36. The instantaneous values of alternating current and voltages in a circuit are given as  

$$i = \frac{1}{\sqrt{2}} \sin(100\pi t) \text{ ampere}$$

$$e = \frac{1}{\sqrt{2}} \sin\left(100\pi t + \frac{\pi}{3}\right) \text{ volt}$$
 The average power in watts consumed in the circuit is  
 (a)  $\frac{1}{4}$  (b)  $\frac{\sqrt{3}}{4}$  (c)  $\frac{1}{2}$  (d)  $\frac{1}{8}$  (Mains 2012)
37. Power dissipated in an LCR series circuit connected to an A.C. source of emf  $\epsilon$  is



$$(a) \frac{\epsilon^2 \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}{R}$$

$$(b) \frac{\epsilon^2 \left[ R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2 \right]}{R}$$

$$(c) \frac{\epsilon^2 R}{\sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}}$$

$$(d) \frac{\epsilon^2 R}{\left[ R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2 \right]}$$



(2009)

38. In an a.c. circuit the e.m.f. ( $\epsilon$ ) and the current ( $i$ ) at any instant are given respectively by

$$\epsilon = E_0 \sin \omega t, \quad i = I_0 \sin(\omega t - \phi)$$

The average power in the circuit over one cycle of a.c. is

$$(a) \frac{E_0 I_0}{2} \cos \phi$$

$$(b) E_0 I_0$$

$$(c) \frac{E_0 I_0}{2}$$

$$(d) \frac{E_0 I_0}{2} \sin \phi$$

(2008)

39. A coil of inductive reactance  $31 \Omega$  has a resistance of  $8 \Omega$ . It is placed in series with a condenser of capacitive reactance  $25 \Omega$ . The combination is connected to an a.c. source of  $110 \text{ V}$ . The power factor of the circuit is

$$(a) 0.33$$

$$(b) 0.56$$

$$(c) 0.64$$

$$(d) 0.80$$

(2006)

40. For a series LCR circuit, the power loss at resonance is

$$(a) \frac{V^2}{\left[ \omega L - \frac{1}{\omega C} \right]}$$

$$(b) I^2 L \omega$$

$$(c) I^2 R$$

$$(d) \frac{V^2}{C \omega}$$

(2002)

41. In an a.c. circuit with phase voltage  $V$  and current  $I$ , the power dissipated is

$$(a) V \cdot I$$

$$(b) \text{ depends on phase angle between } V \text{ and } I$$

$$(c) \frac{1}{2} \times V \cdot I$$

$$(d) \frac{1}{\sqrt{2}} \times V \cdot I$$

(1997)

42. In an A.C. circuit, the current flowing is  $I = 5 \sin(100t - \pi/2)$  ampere and the potential difference is  $V = 200 \sin(100t)$  volts. The power consumption is equal to

$$(a) 20 \text{ W}$$

$$(b) 0 \text{ W}$$

$$(c) 1000 \text{ W}$$

$$(d) 40 \text{ W}$$

(1995)

## 7.8 Transformers

43. In an ideal transformer, the turns ratio is  $\frac{N_p}{N_s} = \frac{1}{2}$ .

The ratio  $V_s : V_p$  is equal to (the symbols carry their usual meaning)

$$(a) 1:2 \quad (b) 2:1 \quad (c) 1:1 \quad (d) 1:4 \quad (2024)$$

44. A  $12 \text{ V}$ ,  $60 \text{ W}$  lamp is connected to the secondary of a step down transformer, whose primary is connected to ac mains of  $220 \text{ V}$ . Assuming the transformer to be ideal, what is the current in the primary winding?

$$(a) 3.7 \text{ A}$$

$$(b) 0.37 \text{ A}$$

$$(c) 0.27 \text{ A}$$

$$(d) 2.7 \text{ A}$$

(2023)

45. A step down transformer connected to an ac mains supply of  $220 \text{ V}$  is made to operate at  $11 \text{ V}$ ,  $44 \text{ W}$  lamp. Ignoring power losses in the transformer, what is the current in the primary circuit?

$$(a) 4 \text{ A}$$

$$(b) 0.2 \text{ A}$$

$$(c) 0.4 \text{ A}$$

$$(d) 2 \text{ A}$$

(2021)

46. A transformer having efficiency of  $90\%$  is working on  $200 \text{ V}$  and  $3 \text{ kW}$  power supply. If the current in the secondary coil is  $6 \text{ A}$ , the voltage across the secondary coil and the current in the primary coil respectively are

$$(a) 300 \text{ V}, 15 \text{ A}$$

$$(b) 450 \text{ V}, 15 \text{ A}$$

$$(c) 450 \text{ V}, 13.5 \text{ A}$$

$$(d) 600 \text{ V}, 15 \text{ A}$$

(2014)

47. The primary of a transformer when connected to a dc battery of  $10 \text{ volt}$  draws a current of  $1 \text{ mA}$ . The number of turns of the primary and secondary windings are  $50$  and  $100$  respectively. The voltage in the secondary and the current drawn by the circuit in the secondary are respectively

$$(a) 20 \text{ V and } 2.0 \text{ mA}$$

$$(b) 10 \text{ V and } 0.5 \text{ mA}$$

$$(c) \text{ Zero volt and therefore no current}$$

$$(d) 20 \text{ V and } 0.5 \text{ mA} \quad (\text{Karnataka NEET 2013})$$

48. A  $220 \text{ volt}$  input is supplied to a transformer. The output circuit draws a current of  $2.0 \text{ ampere}$  at  $440 \text{ volts}$ . If the efficiency of the transformer is  $80\%$ , the current drawn by the primary windings of the transformer is

$$(a) 3.6 \text{ ampere}$$

$$(b) 2.8 \text{ ampere}$$

$$(c) 2.5 \text{ ampere}$$

$$(d) 5.0 \text{ ampere}$$

(2010)

49. The primary and secondary coils of a transformer have  $50$  and  $1500$  turns respectively. If the magnetic flux  $\phi$  linked with the primary coil is given by  $\phi = \phi_0 + 4t$ , where  $\phi$  is in webers,  $t$  is time in seconds and  $\phi_0$  is a constant, the output voltage across the secondary coil is

$$(a) 120 \text{ volts}$$

$$(b) 220 \text{ volts}$$

$$(c) 30 \text{ volts}$$

$$(d) 90 \text{ volts}$$

(2007)

50. A transformer is used to light a  $100 \text{ W}$  and  $110 \text{ V}$  lamp from a  $220 \text{ V}$  mains. If the main current is  $0.5 \text{ amp}$ , the efficiency of the transformer is approximately

$$(a) 50\%$$

$$(b) 90\%$$

$$(c) 10\%$$

$$(d) 30\%$$


(2007)





51. The core of a transformer is laminated because  
 (a) ratio of voltage in primary and secondary may be increased  
 (b) energy losses due to eddy currents may be minimised  
 (c) the weight of the transformer may be reduced  
 (d) rusting of the core may be prevented. (2006)
52. A step-up transformer operates on a 230 V line and supplies a load of 2 ampere. The ratio of the primary and secondary windings is 1 : 25. The current in the primary is  
 (a) 15 A (b) 50 A  
 (c) 25 A (d) 12.5 A (1998)
53. The primary winding of a transformer has 500 turns whereas its secondary has 5000 turns. The primary is connected to an A.C. supply of 20 V, 50 Hz. The secondary will have an output of  
 (a) 2 V, 50 Hz (b) 2 V, 5 Hz  
 (c) 200 V, 50 Hz (d) 200 V, 500 Hz. (1997)

### RC/RL Circuits with DC Source\*

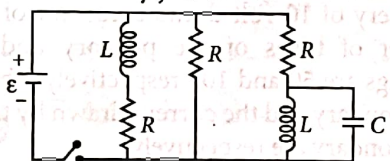54. Figure shows a circuit that contains three identical resistors with resistance  $R = 9.0 \Omega$  each, two identical inductors with inductance  $L = 2.0 \text{ mH}$  each, and an ideal battery with emf  $\epsilon = 18 \text{ V}$ . The current  $i$  through the battery just after the switch closed is



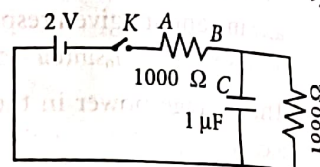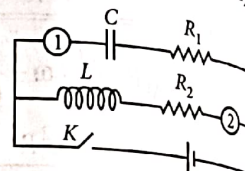- (a) 0.2 A (b) 2 A  
 (c) 0 ampere (d) 2 mA (2017)
55. A coil of 40 henry inductance is connected in series with a resistance of 8 ohm and the combination is joined to the terminals of a 2 volt battery. The time constant of the circuit is  
 (a) 5 seconds (b) 1/5 seconds  
 (c) 40 seconds (d) 20 seconds (2004)
56. In the circuit given in figure, 1 and 2 are ammeters. Just after key  $K$  is pressed to complete the circuit, the reading will be  
 (a) zero in 1, maximum in 2  
 (b) maximum in both 1 and 2  
 (c) zero in both 1 and 2  
 (d) maximum in 1, zero in 2. (1999)
57. When the key  $K$  is pressed at time  $t = 0$ , then which of the following statement about the current  $I$  in the resistor  $AB$  of the given circuit is true?  
 (a)  $I$  oscillates between 1 mA and 2 mA  
 (b) At  $t = 0$ ,  $I = 2 \text{ mA}$  and with time it goes to 1 mA  
 (c)  $I = 1 \text{ mA}$  at all  $t$   
 (d)  $I = 2 \text{ mA}$  at all  $t$ . (1995)
58. The time constant of C-R circuit is  
 (a)  $1/CR$  (b)  $C/R$   
 (c)  $CR$  (d)  $R/C$  (1992)




### ANSWER KEY

- |         |         |         |         |         |         |         |         |           |         |
|---------|---------|---------|---------|---------|---------|---------|---------|-----------|---------|
| 1. (c)  | 2. (c)  | 3. (d)  | 4. (a)  | 5. (b)  | 6. (a)  | 7. (b)  | 8. (c)  | 9. (d)    | 10. (d) |
| 11. (c) | 12. (d) | 13. (a) | 14. (d) | 15. (b) | 16. (a) | 17. (b) | 18. (d) | 19. (a)   | 20. (c) |
| 21. (a) | 22. (c) | 23. (d) | 24. (b) | 25. (b) | 26. (b) | 27. (d) | 28. (d) | 29. (a,b) | 30. (b) |
| 31. (a) | 32. (a) | 33. (c) | 34. (c) | 35. (c) | 36. (d) | 37. (d) | 38. (a) | 39. (d)   | 40. (c) |
| 41. (b) | 42. (b) | 43. (b) | 44. (c) | 45. (b) | 46. (b) | 47. (c) | 48. (d) | 49. (a)   | 50. (b) |
| 51. (b) | 52. (b) | 53. (c) | 54. (*) | 55. (a) | 56. (d) | 57. (b) | 58. (c) |           |         |

## Hints & Explanations

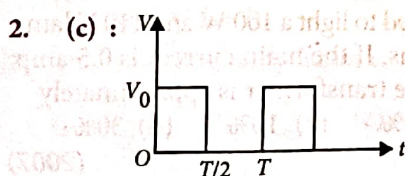1. (c) : The relation between the peak value and the rms value is:

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}; \text{ so, } V_0 = \sqrt{2} V_{\text{rms}}$$



$$V = V_0 \text{ for } 0 \leq t \leq \frac{T}{2} \Rightarrow V = 0 \text{ for } \frac{T}{2} \leq t \leq T$$

$$V_{\text{rms}} = \left[ \frac{\int_0^T V^2 dt}{\int_0^T dt} \right]^{1/2} = \left[ \frac{\int_0^{T/2} V_0^2 dt + \int_{T/2}^T (0)^2 dt}{\int_0^T dt} \right]^{1/2}$$

\*This topic is not in the latest NCERT textbook, but it is a part of current NEET syllabus.