

# SEMICONDUCTOR PHYSICS-2

[Transistor, constructional characteristics, biasing of transistors, transistor configuration, transistor as an amplifier, transistor as a switch, transistor as an oscillator]

## Transistor

It is an electronic device whose fundamental action is transfer of resistor/resistance. Transistor in general is known as bipolar junction transistor (BJT). It is a current operated device.

### Constructional characteristics:-

It consists of three main regions

- (i) **Emitter (E):** It provides majority charge carriers by which current flows in the transistor. Therefore the emitter semiconductor is heavily doped and is of moderate size.
- (ii) **Base (B):** The based region is lightly doped and thin.
- (iii) **Collector (C):** The size of collector region is larger than the two other regions and is moderately doped. It collects a major portion of the majority charge carriers supplied by the emitter.

Junction transistor are of two types :

- (i) **NPN transistor:** It is formed by sandwiching a thin layer of P-type semiconductor between two N-type semiconductors


In NPN transistor electrons are majority charge carriers and flow from emitter to base.



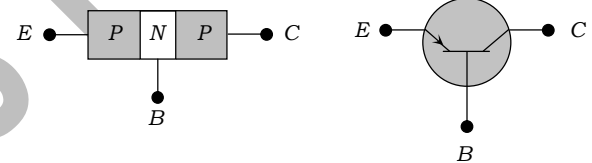- (ii) **PNP transistor:** It is formed by sandwiching a thin layer of N-type semiconductor between two P-type semiconductor

In PNP transistor holes are majority charge carriers and flow from emitter to base.

In the symbols of both NPN and PNP transistor, arrow indicates the direction of conventional current.



### Working of Transistor

(1) There are four possible ways of biasing the two P-N junctions (emitter junction and collector junction) of transistor.

- (i) Active mode: Also known as linear mode operation.
- (ii) Saturation mode: Maximum collector current flows and transistor acts as a closed switch from collector to emitter terminals.
- (iii) Cut-off mode: Denotes operation like an open switch where only leakage current flows.
- (iv) Inverse mode: The emitter and collector are inter changed.

### Different modes of operation of a transistor

Operating mode	Emitter base bias	Collector base bias
Active	Forward	Reverse
Saturation	forward	Forward
Cut off	Reverse	Reverse
Inverse	Reverse	Forward

(2) A transistor is mostly used in the active region of operation i.e. emitter base junction is forward biased and collector base junction is reverse biased.

(3) From the operation of junction transistor it is found that when the current in emitter circuit changes, there is corresponding change in collector current.

(4) In each state of the transistor there is an input port and an output port. In general each electrical quantity ( $V$  or  $I$ ) obtained at the output is controlled by the input.

### Circuit diagram of PNP/NPN transistor

NPN – transistor	PNP – transistor
<p>5% emitter electron combine with the holes in the base region resulting in small base current. Remaining 95% electrons enter the collector region.</p>	<p>5% emitter holes combine with the electrons in the base region resulting in small base current. Remaining 95% holes enter the collector region.</p>
<p><math>I_e &gt; I_c</math>, and <math>I_e = I_b + I_c</math></p>	<p><math>I_e &gt; I_c</math>, and <math>I_e = I_b + I_c</math></p>


### Transistor Configurations

A transistor can be connected in a circuit in the following three different configurations. Common base (CB), Common emitter (CE) and Common collector (CC) configuration.


(1) **CE configurations :** [The transistor is most widely used in the CE configuration and we shall restrict our discussion to only this configuration. Since more commonly used transistors are n-p-n Si transistors, we shall confine our discussion to such transistors only. With p-n-p transistors the polarities of the external power supplies are to be inverted.]
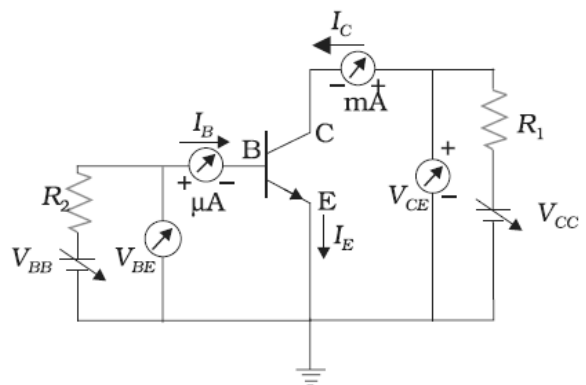
#### (i) Input Characteristics:-

When a transistor is used in CE configuration, the input is between the base and the emitter and the output is between the collector and the emitter. The variation of the base current  $I_B$  with the base-emitter voltage  $V_{BE}$  is called the input characteristic. To study the input characteristics of the transistor in CE configuration, a curve is plotted between the base current  $I_B$  against the base-emitter voltage  $V_{BE}$ . The collector-emitter voltage  $V_{CE}$  is kept fixed while studying the dependence of  $I_B$  on  $V_{BE}$ . We are interested to obtain the input characteristic when the transistor is in active state. So the collector-emitter voltage  $V_{CE}$  is kept large enough to make the base collector junction reverse biased. Since  $V_{CE} = V_{CB} + V_{BE}$  and for Si transistor  $V_{BE}$  is 0.6 to 0.7 V,  $V_{CE}$  must be sufficiently larger than 0.7 V. Since the transistor is operated as an amplifier over large range of  $V_{CE}$ , the reverse bias across the base collector junction is high most of the time. Therefore, the input characteristics may be obtained for  $V_{CE}$  somewhere in the range of 3 V to 20 V. Since the increase in  $V_{CE}$  appears as increase in  $V_{CB}$ , its effect on  $I_B$  is negligible. As a consequence, input characteristics for various values of  $V_{CE}$  will give almost




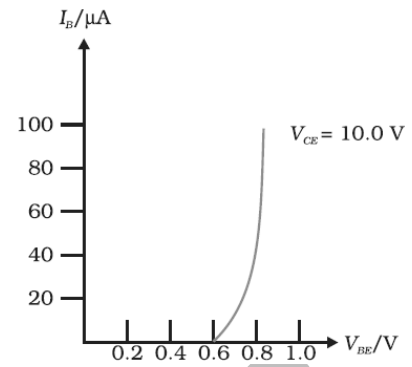identical curves. Hence, *it is enough to determine only one input characteristics*. The input characteristics of a transistor is as shown in Fig.



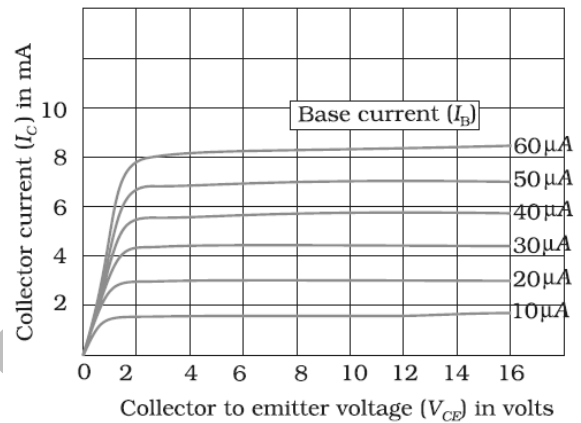**(ii) Output Characteristics:-**

The output characteristic is obtained by observing the variation of  $I_C$  as  $V_{CE}$  is varied keeping  $I_B$  constant. It is obvious that if  $V_{BE}$  is increased by a small amount, both hole current from the emitter region and the electron current from the base region will increase. As a consequence both  $I_B$  and  $I_C$  will increase proportionately. This shows that when  $I_B$  increases  $I_C$  also increases. The plot of  $I_C$  versus  $V_{CE}$  for different fixed values of  $I_B$  gives one output characteristic. So there will be different output characteristics corresponding to different values of  $I_B$  as shown in Fig.



**(iii) Input resistance ( $r_i$ ):** This is defined as the ratio of change in base emitter voltage ( $\Delta V_{BE}$ ) to the resulting change in base current ( $\Delta I_B$ ) at constant collector-emitter voltage ( $V_{CE}$ ). This is dynamic (ac resistance) and as can be seen from the input characteristic, its value varies with the operating current in the transistor:

$$r_i = \left( \frac{\Delta V_{BE}}{\Delta I_B} \right)_{V_{CE}}$$

The value of  $r_i$  can be anything from a few hundreds to a few thousand ohms.

**(iv) Output resistance ( $r_o$ ):** This is defined as the ratio of change in collector-emitter voltage ( $\Delta V_{CE}$ ) to the change in collector current ( $\Delta I_C$ ) at a constant base current  $I_B$ .

$$r_o = \left( \frac{\Delta V_{CE}}{\Delta I_C} \right)_{I_B}$$

The output characteristics show that initially for very small values of  $V_{CE}$ ,  $I_C$  increases almost linearly. This happens because the base-collector junction is not reverse biased and the transistor is not in active state. In fact, the transistor is in the saturation state and the current is controlled by the supply voltage  $V_{CC}$  ( $=V_{CE}$ ) in this part of the characteristic. When  $V_{CE}$  is more than that required to reverse bias the base-collector junction,  $I_C$  increases very little with  $V_{CE}$ . The reciprocal of the slope of the linear part of the output characteristic gives the values of  $r_o$ . The output resistance of the transistor is mainly controlled by the bias of the base collector junction. The high magnitude of the output resistance (of the order of 100 k $\Omega$ ) is due to the reverse-biased state of this diode. This also explains why the resistance at the initial part of the characteristic, when the transistor is in saturation state, is very low.

**(v) Current amplification factor ( $\beta$ ):** This is defined as the ratio of the change in collector current to the change in base current at a constant collector-emitter voltage ( $V_{CE}$ ) when the transistor is in active state.

$$\beta_{ac} = \left( \frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE}}$$

This is also known as *small signal current gain* and its value is very large.

If we simply find the ratio of  $I_C$  and  $I_B$  we get what is called dc  $\beta$  of the transistor. Hence,

$$\beta_{dc} = \frac{I_C}{I_B}$$

Since  $I_C$  increases with  $I_B$  almost linearly and  $I_C = 0$  when  $I_B = 0$ , the values of both  $\beta_{dc}$  and  $\beta_{ac}$  are nearly equal. So, for most calculations  $\beta_{dc}$  can be used. Both  $\beta_{ac}$  and  $\beta_{dc}$  vary with  $V_{CE}$  and  $I_B$  (or  $I_C$ ) slightly.

**Understanding Concept:-**

1. From the output characteristics shown in Fig. above, calculate the values of  $\beta_{ac}$  and  $\beta_{dc}$  of the transistor when  $V_{CE}$  is 10 V and  $I_C = 4.0$  mA.


2. For transistor action, which of the following statements are correct:

- (a) Base, emitter and collector regions should have similar size and doping concentrations.
- (b) The base region must be very thin and lightly doped.
- (c) The emitter junction is forward biased and collector junction is reverse biased.
- (d) Both the emitter junction as well as the collector junction are forward biased.


3. In a npn transistor circuit, the collector current is 10mA. If 95 per cent of the electrons emitted reach the collector, which of the following statements are true?

- (a) The emitter current will be 8 mA.
- (b) The emitter current will be 10.53 mA.
- (c) The base current will be 0.53 mA.
- (d) The base current will be 2 mA.

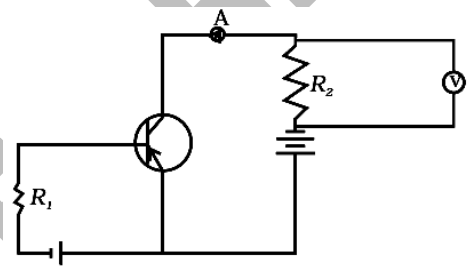4. If the resistance  $R_1$  is increased (Fig.), how will the readings of the ammeter and voltmeter change?




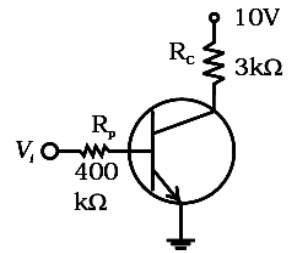
5. In the circuit shown in Fig., when the input voltage of the base resistance is 10V,  $V_{be}$  is zero and  $V_{ce}$  is also zero. Find the values of  $I_b$ ,  $I_c$  and  $\beta$ .



THE PHYSICS TUTOR

## Transistor as a device

### (i) Transistor as a switch

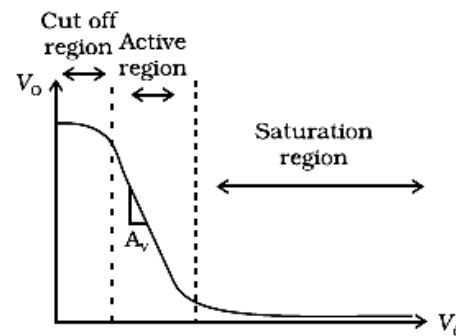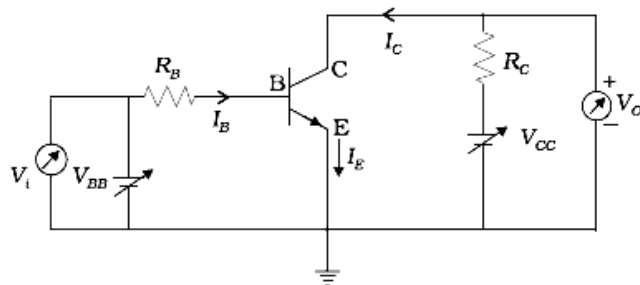

Applying Kirchoff's voltage rule to the input and output sides of this circuit, we get

$$V_{BB} = I_B R_B + V_{BE} \quad \text{-----(1)}$$

and

$$V_{CE} = V_{CC} - I_C R_C \quad \text{-----(2)}$$

We shall treat  $V_{BB}$  as the dc input voltage  $V_i$  and  $V_{CE}$  as the dc output voltage  $V_o$ . So, we have

$$V_i = I_B R_B + V_{BE}$$

and

$$V_o = V_{CC} - I_C R_C.$$

[Taking the case of Si transistor, as long as input  $V_i$  is less than 0.6 V, the transistor will be in cut off state and current  $I_C$  will be zero.

Hence  $V_o = V_{CC}$

When  $V_i$  becomes greater than 0.6 V the transistor is in active state with some current  $I_C$  in the output path and the output  $V_o$  decrease as the term  $I_C R_C$  increases. With increase of  $V_i$ ,  $I_C$  increases almost linearly and so  $V_o$  decreases linearly till its value becomes less than about 1.0 V.

Beyond this, the change becomes non linear and transistor goes into saturation state. With further increase in  $V_i$  the output voltage is found to decrease further towards zero though it may never become zero.

According to the plot of  $V_o$  vs  $V_i$  curve, [also called the **transfer characteristics** of the base-biased transistor, we see that between cut off state and active state and also between active state and saturation state there are regions of non-linearity showing that the transition from cutoff state to active state and from active state to saturation state are not sharply defined.]

As long as  $V_i$  is low and unable to forward-bias the transistor,  $V_o$  is high (at  $V_{CC}$ ). If  $V_i$  is high enough to drive the transistor into saturation, then  $V_o$  is low, very near to zero. When the transistor is not conducting it is said to be switched off and when it is driven into saturation it is said to be switched on. Hence we can define low and high states as below and above certain voltage levels corresponding to cutoff and saturation of the transistor, then we can say that a **low input switches** the transistor **off** and a **high input switches** it **on**.

Alternatively, we can say that a low input to the transistor gives a high output and a high input gives a low output.


**The switching circuits are designed in such a way that the transistor does not remain in active state. {C.T.M.}**

#### Understanding Concept:-

1. In Fig. (above), the  $V_{BB}$  supply can be varied from 0V to 5.0 V. The Si transistor has  $\beta_{dc} = 250$  and  $R_B = 100 \text{ K}\Omega$ ,  $R_C = 1 \text{ K}\Omega$ ,  $V_{CC} = 5.0\text{V}$ . Assume that when the transistor is saturated,  $V_{CE} = 0\text{V}$  and  $V_{BE} = 0.8\text{V}$ . Calculate (a) the minimum base current, for which the transistor will reach saturation. Hence, (b) determine  $V_i$  when the transistor is 'switched on'. (c) find the ranges of  $V_i$  for which the transistor is 'switched off' and 'switched on'.

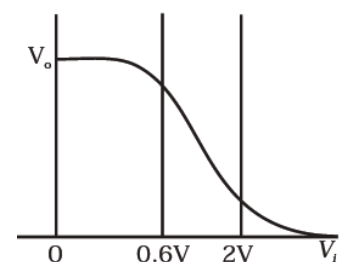2. Figure shows the transfer characteristics of a base biased CE transistor. Which of the following statements are true?

- At  $V_i = 0.4\text{V}$ , transistor is in active state.
- At  $V_i = 1\text{V}$ , it can be used as an amplifier.
- At  $V_i = 0.5\text{V}$ , it can be used as a switch turned off.
- At  $V_i = 2.5\text{V}$ , it can be used as a switch turned on.




## Transistor as an Amplifier

A device which increases the amplitude of the input signal is called amplifier.

(i). The transistor can be used as an amplifier in the following three configuration

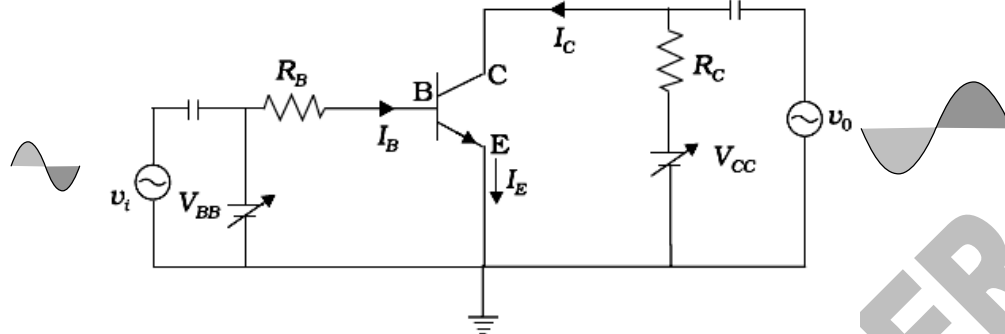(a) CB amplifier      (b) CE amplifier **(in Syllabus)**      (c) CC amplifier



[To operate the transistor as an amplifier it is necessary to fix its operating point somewhere in the middle of its active region. If we fix the value of  $V_{BB}$  corresponding to a point in the middle of the linear part of the transfer curve then the dc base current  $I_B$  will be constant and corresponding collector current  $I_C$  will also be constant. The dc voltage  $V_{CE} = V_{CC} - I_C R_C$  would also remain constant. The operating values of  $V_{CE}$  and  $I_B$  determine the operating point, of the amplifier.

If a small sinusoidal voltage with amplitude  $v_s$  is superposed on the dc base bias by connecting the source of that signal in series with the  $V_{BB}$  supply, then the base current will have sinusoidal variations superimposed on the value of  $I_B$ . As a consequence the collector current also will have sinusoidal variations superimposed on the value of  $I_C$ , producing in turn corresponding change in the value of  $V_o$ . We can measure the ac variations across the input and output terminals by blocking the dc voltages by large capacitors.

**Working:-** Suppose we superimpose an ac input signal  $v_i$  (to be amplified) on the bias  $V_{BB}$  (dc) as shown in Fig. The output is taken between the collector and the ground.

Let  $v_i = 0$ . Then applying Kirchhoff's law to the output loop, we get

$$V_{CC} = V_{CE} + I_C R_C \text{ -----(1)}$$

Likewise, the input loop gives

$$V_{BB} = V_{BE} + I_B R_B \text{ -----(2)}$$

When  $v_i$  is not zero, we get

$$V_{BE} + v_i = V_{BE} + I_B R_B + \Delta I_B (R_B + r_i)$$

The change in  $V_{BE}$  can be related to the input resistance  $r_i$  and the change in  $I_B$ . Hence

$$v_i = \Delta I_B (R_B + r_i) = r \Delta I_B$$

Now the change in  $I_C$  due to a change in  $I_B$  causes a change in  $V_{CE}$  and the voltage drop across the resistor  $R_C$  because  $V_{CC}$  is fixed. Therefore

$$\Delta V_{CC} = \Delta V_{CE} + R_C \Delta I_C = 0$$

$$\text{or } \Delta V_{CE} = -R_C \Delta I_C = v_o$$

where the change in  $V_{CE}$  is the output voltage  $v_o$ .

Hence, the voltage gain of the amplifier is

$$A_V = \frac{v_o}{v_i} = \frac{\Delta V_{CE}}{r \Delta I_B} = \frac{-R_C \Delta I_C}{r \Delta I_B} = -\beta_{ac} \frac{R_C}{r}; \text{ where } \beta_{ac} \text{ is defines as the a.c current gain of the}$$

amplifier.

**The negative sign represents that output voltage is opposite with phase with the input voltage.**

Similarly, the power gain  $A_P$  can be expressed as the product of the current gain and voltage gain. Mathematically

$$A_P = \beta_{ac} \times A_V$$


Since  $\beta_{ac}$  and  $A_V$  are greater than 1, we get ac power gain. However it should be realized that transistor is not a power generating device. The energy for the higher ac power at the output is supplied by the battery.

\* Trans conductance ( $g_m$ ): The ratio of the change in collector current to the change in emitter base voltage is called trans conductance. *i.e.*  $g_m = \frac{\Delta I_C}{\Delta V_{EB}}$ . Also  $g_m = \frac{A_V}{R_C}$ ;  $R_C = \text{Load}$

resistance

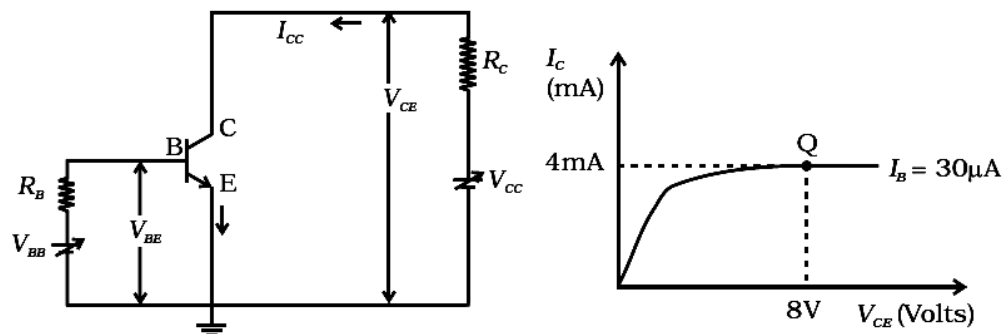
### Understanding Concept:-

- For a CE transistor amplifier, the audio signal voltage across the collector resistance of  $2.0\text{ k}\Omega$  is  $2.0\text{ V}$ . Suppose the current amplification factor of the transistor is 100, What should be the value of  $R_B$  in series with  $V_{BB}$  supply of  $2.0\text{ V}$  if the dc base current has to be 10 times the signal current. Also calculate the dc drop across the collector resistance. (Refer to Fig. above for amplifier).
- For a transistor amplifier, the voltage gain
  - remains constant for all frequencies.
  - is high at high and low frequencies and constant in the middle frequency range.
  - is low at high and low frequencies and constant at mid frequencies.
  - None of the above.
- For a CE-transistor amplifier, the audio signal voltage across the collected resistance of  $2\text{ k}\Omega$  is  $2\text{ V}$ . Suppose the current amplification factor of the transistor is 100, find the input signal voltage and base current, if the base resistance is  $1\text{ k}\Omega$ .
- Two amplifiers are connected one after the other in series (cascaded). The first amplifier has a voltage gain of 10 and the second has a voltage gain of 20. If the input signal is  $0.01\text{ volt}$ , calculate the output ac signal.
- The amplifiers X, Y and Z are connected in series. If the voltage gains of X, Y and Z are 10, 20 and 30, respectively and the input signal is  $1\text{ mV}$  peak value, then what is the output signal voltage (peak value)
  - if dc supply voltage is  $10\text{V}$ ?
  - if dc supply voltage is  $5\text{V}$ ?
- In a CE transistor amplifier there is a current and voltage gain associated with the circuit. In other words there is a power gain. Considering power a measure of energy, does the circuit violate conservation of energy?
- Consider the circuit arrangement shown in Fig. for studying input and output characteristics of npn transistor in CE configuration.




Select the values of  $R_B$  and  $R_C$  for a transistor whose  $V_{BE} = 0.7\text{ V}$ , so that the transistor is operating at point Q as shown in the characteristics shown in Fig. Given that the input impedance of the transistor is very small and  $V_{CC} = V_{BB} = 16\text{ V}$ , also find the voltage gain and power gain of circuit making appropriate assumptions.

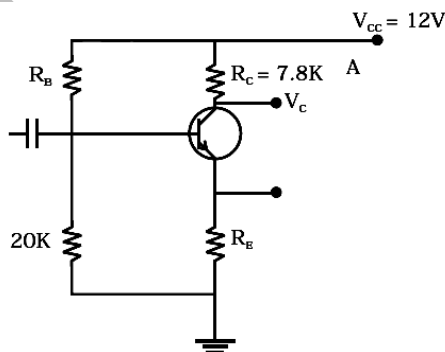- For the transistor circuit shown in Fig., evaluate  $V_E$ ,  $R_B$ ,  $R_E$  given  $I_C = 1\text{ mA}$ ,  $V_{CE} = 3\text{V}$ ,  $V_{BE} = 0.5\text{ V}$  and  $V_{CC} = 12\text{ V}$ ,  $\beta = 100$ .



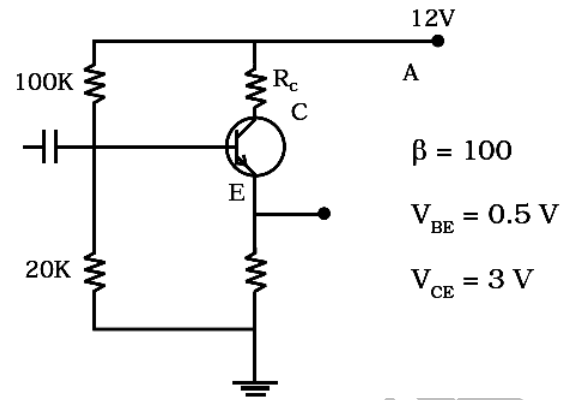9. In the circuit shown in Fig., find the value of  $R_C$ .



10. When npn transistor is used as an amplifier:

- (1) electrons move from base to collector
- (2) holes move from emitter to base
- (3) electrons move from collector to base
- (4) holes move from base to emitter

[AIEEE-2004]

THE PHYSICS TEACHER



### Transistor as an Oscillator

(1) It is defined as a circuit which generates an *ac* output signal without any externally applied input signal.

Audio frequency oscillators generates signals of frequencies ranging from a few *Hz* to 20 *kHz* and radio frequency oscillators have a range from few *kHz* to *MHz*.

(2) In an oscillator the frequency, waveform, and magnitude of *ac* power generated is controlled by circuit itself.

(3) An oscillator may be considered as amplifier which provides it's own input signal.


(4) The essential of a transistor oscillator are

(i) **Tank circuit:** Parallel combination of *L* and *C*. This network resonates at a frequency

$$v_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

(ii) **Amplifier:** It receives *dc* power from the battery and converts into *ac* power. The amplifier increases the strength of oscillations.


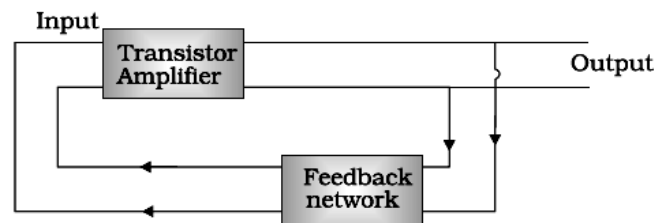
(iii) **Feed back circuit:** A portion of the output power is returned back (feedback) to the input in phase with the starting power (this process is termed positive feedback)




**[NOTE:-Need for positive feedback:** The oscillations are damped due to the presence of some inherent electrical resistance in the circuit. Consequently, the amplitude of oscillations decreases rapidly and the oscillations ultimately stop. Such oscillations are of little practical importance. In order to obtain oscillations of constant amplitude, we make an arrangement for regenerative or positive feedback from the output circuit to the input circuit so that the losses in the circuit can be compensated.]
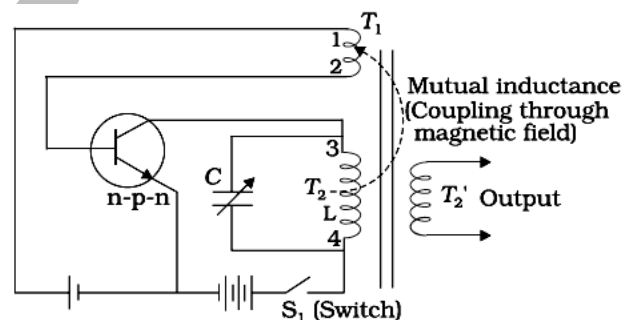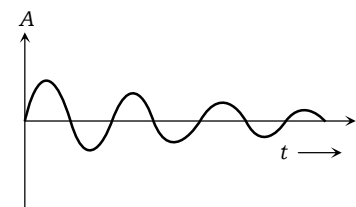
#### Working:-

Suppose switch *S*<sub>1</sub> is put on to apply proper bias for the first time. Obviously, a surge of collector current flows in the transistor. This current flows through the coil *T*<sub>2</sub> where terminals are numbered 3 and 4 [Fig.]. This current does not reach full amplitude instantaneously but increases from *X* to *Y*, as shown in Fig.(i). The inductive coupling between coil *T*<sub>2</sub> and coil *T*<sub>1</sub> now causes a current to flow in the emitter circuit (note that this actually is the feedback from input to output). As a result of this positive feedback, this current (in *T*<sub>1</sub>; emitter current) also increases from *X'* to *Y'* Fig.(ii). The current in *T*<sub>2</sub> (collector current) connected in the collector circuit acquires the value *Y* when the transistor becomes saturated. This means that maximum collector current is flowing and can increase no further. Since there is no further change in collector current, the magnetic field around *T*<sub>2</sub> ceases to grow. As soon as the field becomes static, there will be no further feedback from *T*<sub>2</sub> to *T*<sub>1</sub>. Without continued feedback, the emitter current begins to fall. Consequently, collector current decreases from *Y* towards *Z* [Fig.(i)]. However, a decrease of collector current causes the magnetic field to decay around the coil *T*<sub>2</sub>. Thus, *T*<sub>1</sub> is now seeing a decaying field in *T*<sub>2</sub> (opposite from what it saw when the field was growing at the initial start operation). This causes a further decrease in the emitter current till it reaches *Z'* when the transistor is cut-off. This means that both *I*<sub>E</sub> and *I*<sub>C</sub> cease to flow. Therefore, the transistor has reverted back to its original state (when the power was first switched on). The whole process now repeats itself. That is, the transistor is driven to saturation, then to cut-off, and then back to



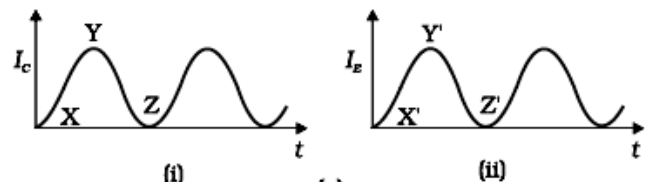Note that the coils *T*<sub>2</sub> and *T*<sub>1</sub> are wound on the same core and hence are inductively coupled through their mutual inductance.



saturation. The time for change from saturation to cut-off and back is determined by the constants of the tank circuit or tuned circuit (inductance L of coil T<sub>2</sub> and C connected in parallel to it). The resonance frequency ( $\nu$ ) of this tuned circuit determines the frequency at which the oscillator will oscillate.

$$\nu = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

In the circuit as shown, the tank or tuned circuit is connected in the collector side. Hence, it is known as tuned collector oscillator. If the tuned circuit is on the base side, it will be known as tuned base oscillator. There are many other types of tank circuits (say RC) or feedback circuits giving different types of oscillators like Colpit's oscillator, Hartley oscillator, RC-oscillator.

THE PHYSICS TEACHER