

Power System - Ist

Syllabus —

- (1) N/w matrices
- (2) Load flow studies
- (3) short circuit studies
- (4) switch gear & protection
- (5) Power system stability
- (6) Economic deposition problem

Power system Analysis - Ist - Ramana



$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} P_{12} \\ P_{13} \\ P_{24} \\ P_{34} \end{bmatrix}$$

Network Matrices


Network matrices:-

For the purpose of conductivity various kind

of studies of P.S. we need the properties of a passive large size power system N/w.

- Network matrices decides the properties of the N/w.
- For analysing the system under steady state or dynamic state. The properties of the N/w is quite essential.

Frame of Reference :-

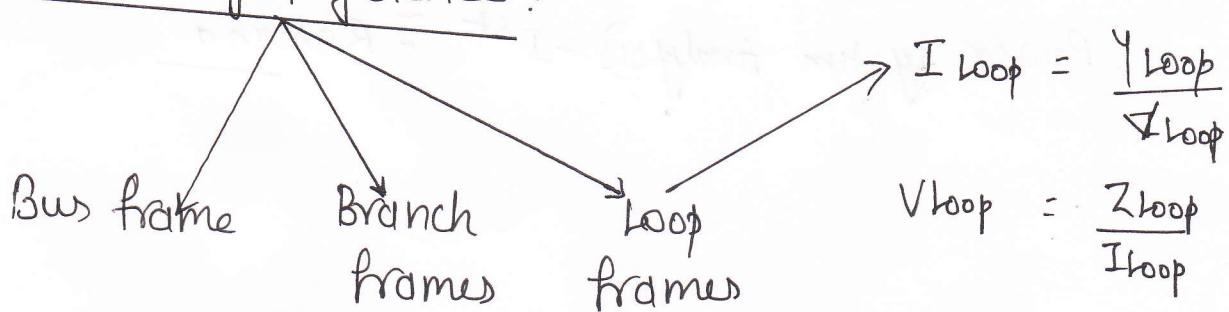


$$V_i \xrightarrow{\text{mwmw}} U_k$$

$$V_i - V_k \rightarrow \text{Branch Voltage}$$

Bus means electrical Junction

$$I_{\text{bus}} = Y_{\text{bus}} \cdot V_{\text{bus}}$$
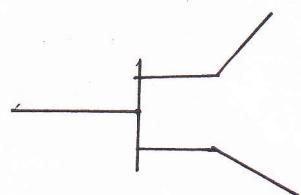
$$\begin{bmatrix} V_{\text{bus}} \\ \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$



Form Y-Bus:-

Leaving out the ref. bus @ the no. of buses $\neq 3$.
 \therefore size of the Y-bus is 3×3

The values marked as reactance into admittance matrix form.

$$Z \rightarrow Y$$

$$ex \rightarrow j0.1 \rightarrow -j10$$

$$-j10 \rightarrow +j0.1$$

$$j0.2 \rightarrow -j5$$

$$-j5 \rightarrow j0.2$$

$$j0.2 \rightarrow \frac{10}{j0.2} = -j15$$

$$Y_{Bws} = \begin{bmatrix} Y_{11} & Y_{12} & Y_{13} \\ Y_{21} & Y_{22} & Y_{23} \\ Y_{31} & Y_{32} & Y_{33} \end{bmatrix}$$


$$Y_{11} - \text{Total admittance connected to bus } ① \\ = -j10 + j0.1 = -j.99$$

$$Y_{22} = +j0.1 - j5 = -j4.9$$

$$Y_{33} = -j5 + j0.2 = -j4.8$$


Off diagonal element -

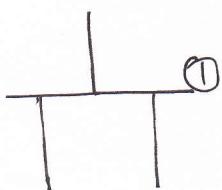Y_{ik} - Negative value of series admittance
Connected b/w bus $①$ & $②$




I_1 - Total incoming current to Bus
 $I_2 \} \quad I_3 \}$ - Total outgoing current.

Bus Frames:-

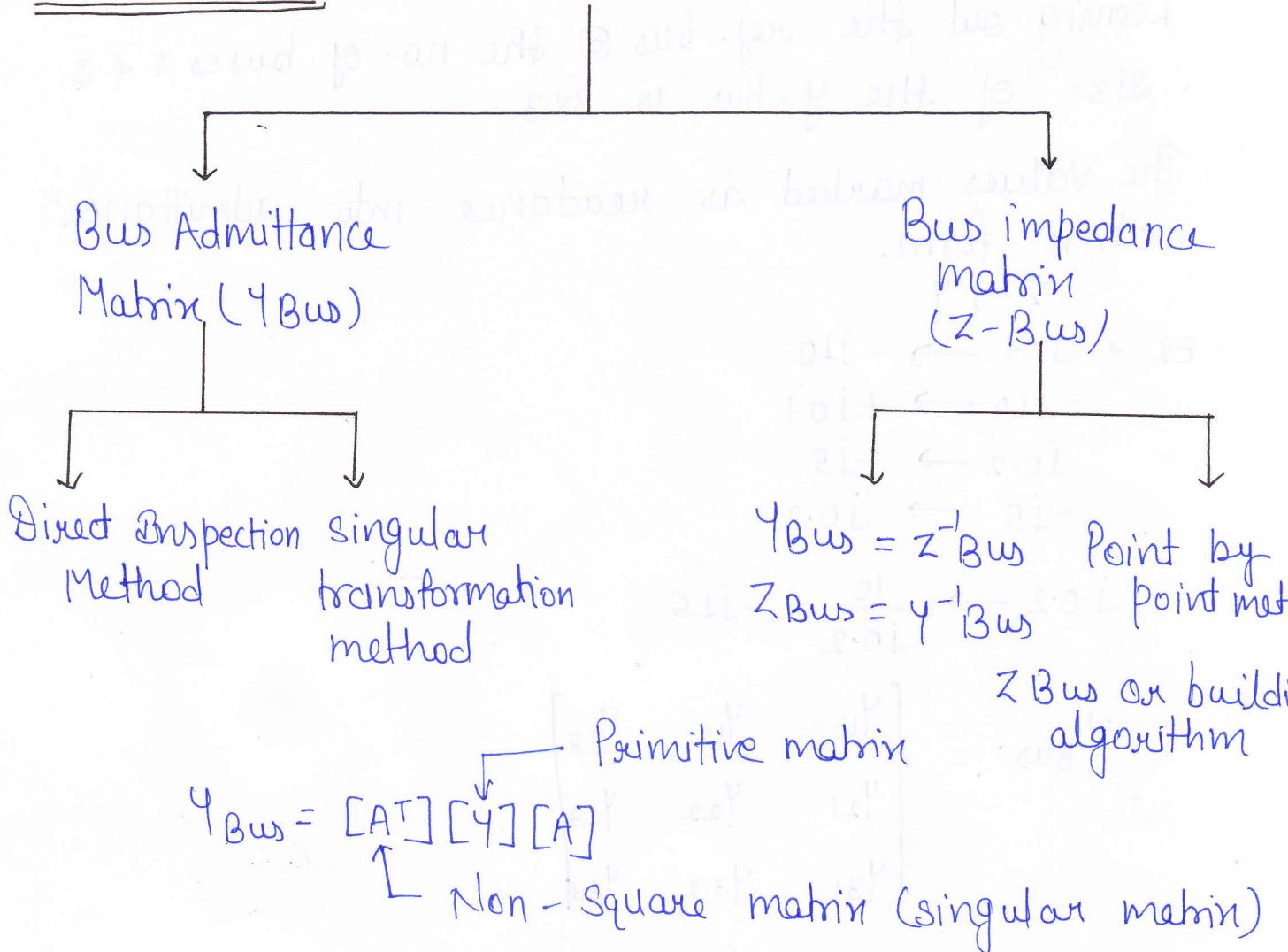

Y - BUS FORMATION :-

(a) Direct Inspection Method -

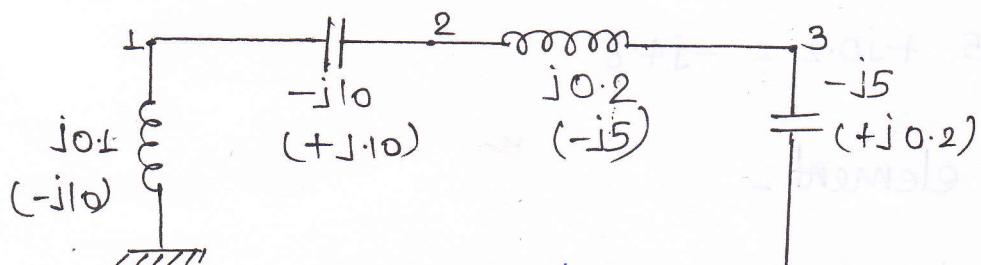

$$Z = R \pm jX$$

$$Y = G \mp jB$$

③

$$\gamma_{12} = \gamma_{21} = -(+0.1) = -j0.1$$

$$\gamma_{13} = \gamma_{31} = -0 = 0 \text{ (No direct connection b/w buss)}$$


① ≠ ③

$$\gamma_{23} = \gamma_{32} = -(-j5) = +j5$$



Network Topology or Graph Theory →

Topology is the subject which deals with the geometrical representation of the various objects.

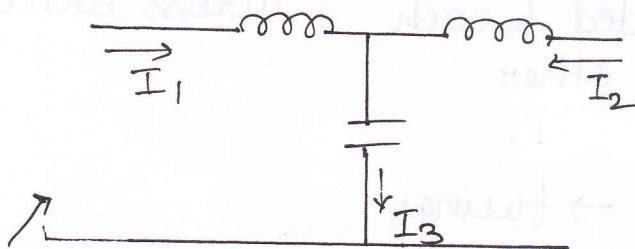Geometrical representation — form loses its identity
not need to take origin a elements.
Just make the graph e.g.




$$I_3 = I_1 + I_2$$

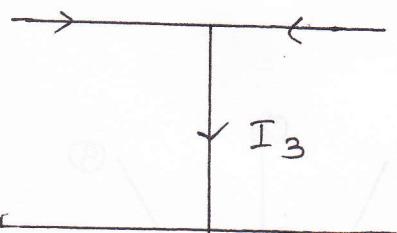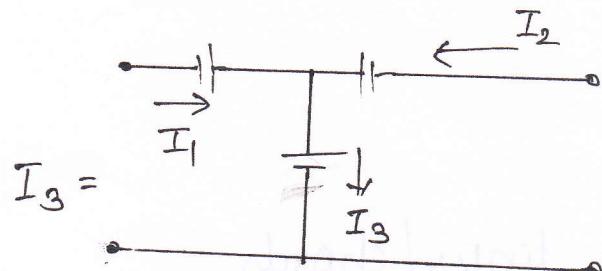


$$I_3 = I_1 + I_2$$

Use incidence
matrix $a_{ij} = \begin{bmatrix} +1 & -1 \\ 0 & 0 \end{bmatrix}$

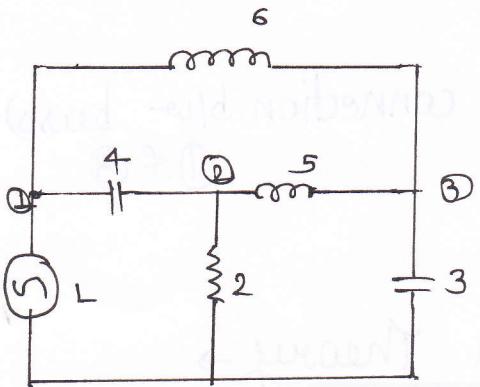- Network algorithm means finding the current through & voltage across every branch of a network.
- Network analysis can be carried out by using either loop analysis or node analysis.
- The basis for the nodal analysis is KCL and for loop analysis is KVL.
- The KCL & KVL do not depend on type of element but depend upon the str of the NW as graph of the NW




Element $e = 6$
node $n = 4$

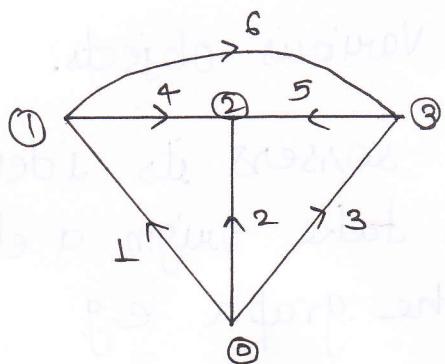


- Main graph
- Oriented graph
- Planner Graph
- Well connected

All the node
connected to each
other

because element
across each other

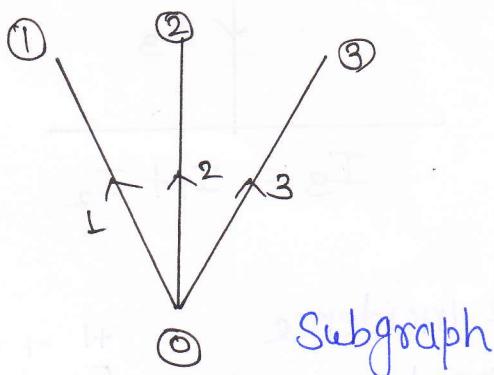


1, 2, 3 → twings
 $t = n - 1$

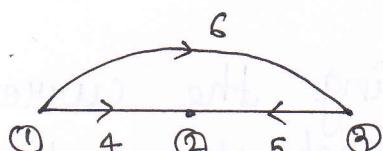

4, 5, 6 → links / chords

$$d = e - (n - 1)$$


$$= e - n + 1$$

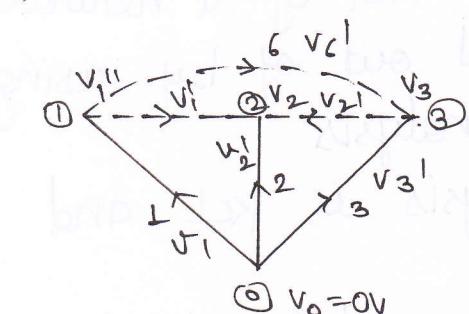

V_0, V_1, V_2, V_3 → node voltage

Power system

④

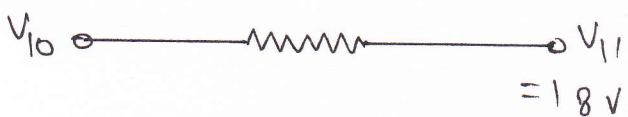

$$V_1' = 20 - 18 = 2\text{V} \rightarrow$$

Branch voltage

$$U_1 = V_0 - V_1 = -V_1$$

$$U_4 = V_1 - V_2$$


$$U_2 = V_0 - V_2 = -V_2$$

$$U_5 = V_3 - V_2$$

$$U_3 = V_0 - V_3 = -V_3$$

$$U_6 = V_1 - V_3$$

Element node incidence matrix

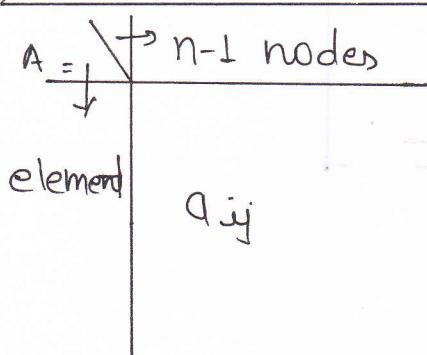

$a_{ij} = +1 \Rightarrow$ if the element is incident away from the junction node and oriented away from junction node.

$-1 \Rightarrow$ Oriented forwards

$0 \Rightarrow$

$A =$

	1	2	3	
①	-1	0	0	
②	0	-1	0	
③	0	0	-1	
④	+1	-1	0	
⑤	0	-1	+1	
⑥	+1	0	-1	

By adding ref. bus
the sum of column
is zero.

$$[V] = [A][v]$$

$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \rightarrow \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \end{bmatrix} = \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$V_1 = -V_1$$

$$V_4 = V_1 - V_2$$

$$V_2 = -V_2$$

$$V_5 = -V_2 + V_3$$

$$V_3 = -V_3$$

$$V_6 = V_1 - V_3$$

Singular Transformation Method:-


$$Y_{BWS} = [A^T][Y][A]$$

$A \rightarrow$ element node incidence matrix

$[Y] \rightarrow P_{ij}$ admittance matrix
 $= [Z^{-1}]$

$[Z] = P_{ij}$ Impedance matrix


Exa:-

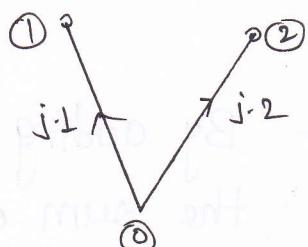

Form Y_{BWS}

(5)

(a) Direct inspection method :-

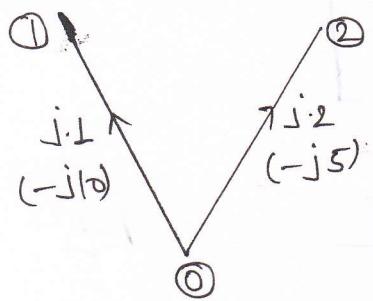

$$Y_{BWS} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -j10 & 0 \\ 0 & j5 \end{bmatrix}$$

Singular Transformation method :-

$$A = \begin{array}{|c|c|} \hline 1 & 2 \\ \hline -1 & 0 \\ \hline 0 & -1 \\ \hline \end{array}$$

$$A^{-1} = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix}$$

$$Z = \begin{array}{|c|c|c|} \hline e^l & -1 & -2 \\ \hline 1 & j0.1 & 0 \\ \hline 2 & 0 & j0.2 \\ \hline \end{array}$$

Z_{11}, Z_{22} - Self impedance


Z_{12}, Z_{21} - Mutual impedance

$$Y = [Z^{-1}] = \begin{bmatrix} 1 & 0 \\ j0.1 & 1 \\ 0 & j0.2 \end{bmatrix} = \begin{bmatrix} -j10 & 0 \\ 0 & -j5 \end{bmatrix}$$

$$Y_{BWS} = [A^T][Y][A]$$

$$= \begin{bmatrix} -j10 & 0 \\ 0 & -j5 \end{bmatrix}$$

Exa - 1

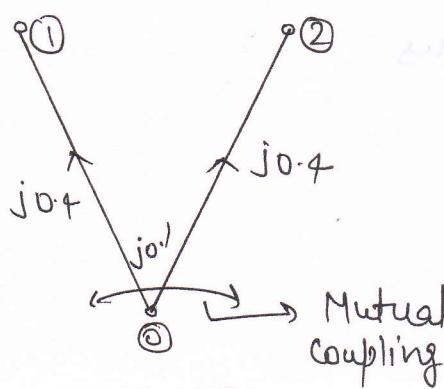

Form Y_{BWS}

$$Y_{Bws} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -j\frac{10}{4} & -j10 \\ -j10 & -j\frac{10}{4} \end{bmatrix} \times \text{(Not valid)}$$

$$A = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix} \quad Z = \frac{1}{2} \begin{vmatrix} j \cdot 4 & j \cdot 1 \\ j \cdot 1 & j \cdot 4 \end{vmatrix}$$

$$Y = Z^{-1} = \frac{1}{AD-BC} \times \begin{bmatrix} D & -B \\ -C & A \end{bmatrix}$$

$$= \frac{1}{j0.4 \times j0.4 - j0.1 \times j0.1} \begin{bmatrix} j0.4 & -j0.1 \\ -j0.1 & j0.4 \end{bmatrix}$$

$$= \frac{1}{-0.15} \begin{bmatrix} j0.4 & -j0.1 \\ -j0.1 & j0.4 \end{bmatrix} = \begin{bmatrix} -j2.67 & +j0.667 \\ +j0.667 & -j2.67 \end{bmatrix}$$

$$Y_{Bws} = [A^T] [Y] [A]$$

$$= \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} -j2.67 & +j0.667 \\ +j0.667 & -j2.67 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} -j2.67 & +j0.667 \\ +j0.667 & -j2.67 \end{bmatrix}$$

Z_{Bws} Building Algorithm:-


$$Z_{Bws} = Y_{Bws}^{-1}$$

Disadvantage:-


- (i) Finding the inverse of such a big matrix is very difficult.
- * Z-bus can be obtain from the inverse of Y-Bus. This method has following disadvantage.
 - ① Owing to the no. of buses in power system the dimension of Y-bus is quite large finding the inverse of such a big matrix is always difficult.
 - ② In Ps N/w changes (element addition deletion, and change the impedance value of element period cally takes place). When such changes takes place formation of the z-bus from beginning through Y-bus is difficult.

To encounter the above difficulties the algorithm known as zbus building algorithm is proposed.

Consider n-bus P.S. $N/w \rightarrow$

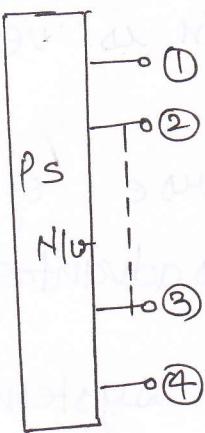

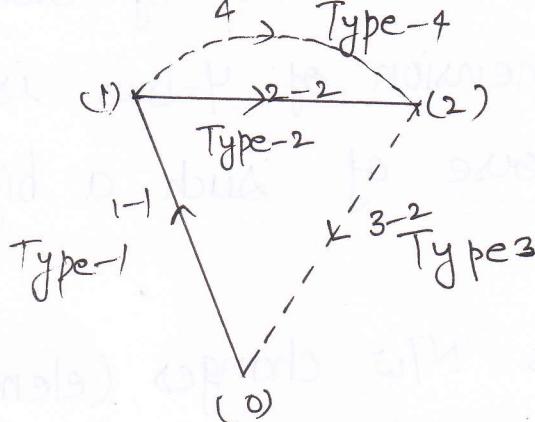
$$Z_{\text{Bus, old}} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1n} \\ Z_{21} & Z_{22} & \cdots & Z_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{n1} & Z_{n2} & \cdots & Z_{nn} \end{bmatrix}_{n \times n}$$



Type-1 Modification:

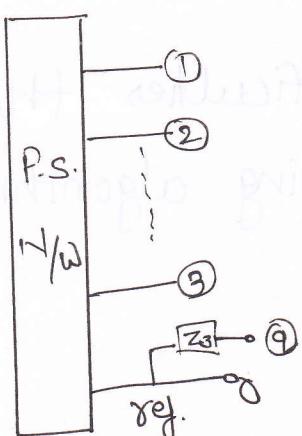An element with self impedance Z_s is added b/w ref bus (0) + new bus ④



* When tying existing then the new node will also exist.

In type-1 one row & one column added due to 1-2 imp exist.

$(Z_{\text{Bus, old}})_{m \times n}$	Z_{1q}
	Z_{2q}
	\vdots
	Z_{nq}
$Z_{q1} \ Z_{q2}$	$Z_{qn} \ Z_{qq}$


$$Z_{\text{BUS, New}} =$$

				0
				0
				0
				0
0	0	0	0	Z_{dq}

* OFF diagonal value will always 0 in type-1.


$$Z_{dq} = Z_s$$

Exp. 1.

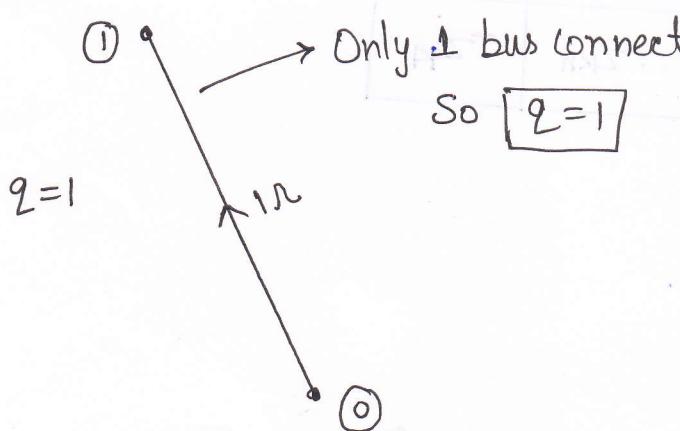

$$Z_{\text{BUS}} = \boxed{\begin{matrix} 1 \\ 1 \end{matrix}}$$


Exp. 2.

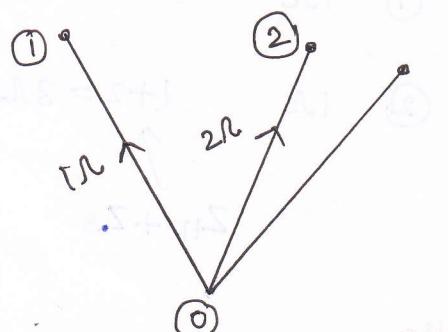

$$\begin{matrix} & \begin{matrix} 1 \\ 1 \end{matrix} & \begin{matrix} 2 \\ 0 \end{matrix} \\ \begin{matrix} 1 \\ 1 \end{matrix} & Z_{11} = 1\Omega & Z_{22} = 2\Omega \\ \begin{matrix} 2 \\ 0 \end{matrix} & 0 & \end{matrix}$$

* Type-2. Modification :-

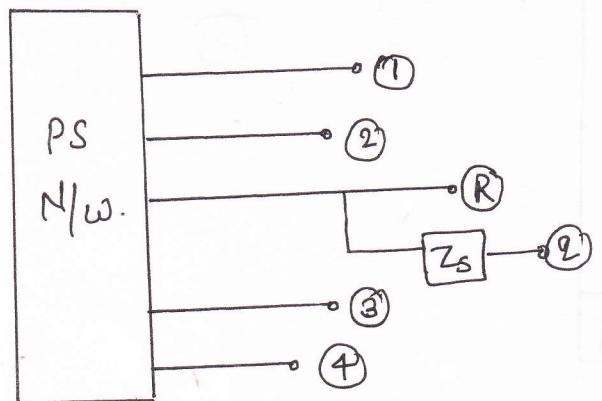An element will self impedance Z_s is added b/w already existing bus (1) & a new bus (2).



$Z_{BUS, old} =$

Z_{11}	$Z_{12} \dots Z_{1K} \dots Z_{1n}$
Z_{21}	$Z_{22} \dots Z_{2K} \dots Z_{2n}$
\vdots	\vdots
Z_{K1}	$Z_{K2} \dots Z_{KK} \dots Z_{Kn}$
Z_{n1}	$Z_{n2} \dots Z_{nk} \dots Z_{nn}$

$Z_{BUS, new} =$

Z_{11}	$Z_{12} \dots Z_{1K} \dots Z_{1n}$	Z_{1K}
\vdots	\vdots	Z_{2K}
Z_{K1}	$Z_{K2} \dots Z_{KK} \dots Z_{Kn}$	Z_{Kn}
Z_{n1}	$Z_{n2} \dots Z_{nk} \dots Z_{nn}$	Z_{nk}


Z_{q1}

q^{th} Row

q^{th} column
copy q^{th} column
+ paste of q^{th} row

Copy k^{th} row & paste as q^{th} row.

Exp. 1 :-

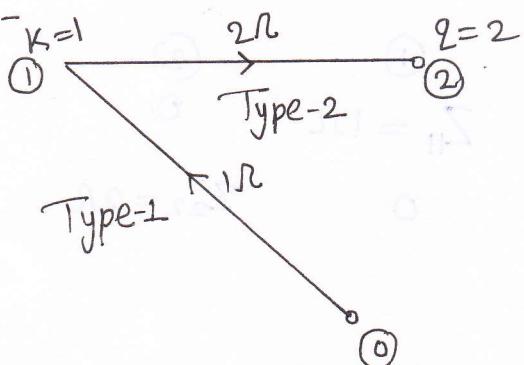


$Z_{BUS} =$

(1)	1 ohm	1 ohm
(2)	1 ohm	$1 + 2 = 3 \text{ ohms}$

$Z_{11} + Z_s$

Exp. 2 :-

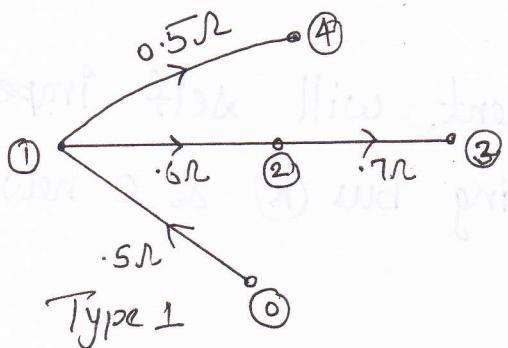

$Z_{BUS} =$

(1)	0.5	0.5	0.5	0.5
(2)	0.5	0.5	0.5	0.5
(3)	0.7	0.7	0.7	0.7
(4)	0.5	0.5	0.5	0.5

$$\rightarrow Z_{BUS} = \textcircled{1} \quad \boxed{.5\Omega}$$


$$\rightarrow Z_{BVS} = \begin{matrix} \textcircled{1} & .5\Omega & \textcircled{2} \\ \textcircled{2} & .5\Omega & 1.1\Omega \end{matrix}$$

$$\rightarrow Z_{BUS} = \begin{matrix} \textcircled{1} & .5 & \textcircled{2} & \textcircled{3} \\ \textcircled{2} & .5 & 1.1 & 1.1 \\ \textcircled{3} & .5 & 1.1 & 1.8 \end{matrix}$$

$$\rightarrow Z_{BUS} = \sum_{k=1}^4 \begin{matrix} \textcircled{1} & \{ .5 & \{ .5 & \{ .5 & \{ .5 \\ \textcircled{2} & \{ .5 & 1.1 & 1.1 & \{ .5 \\ \textcircled{3} & \{ .5 & 1.1 & 1.8 & \{ .5 \\ \textcircled{4} & \{ .5 & \{ .5 & \{ .5 & 1.3\Omega \end{matrix} \text{Parte} \\ \text{Parte} & & & & Z_{11} + Z_s \end{matrix}$$

Type-3 Modification :-

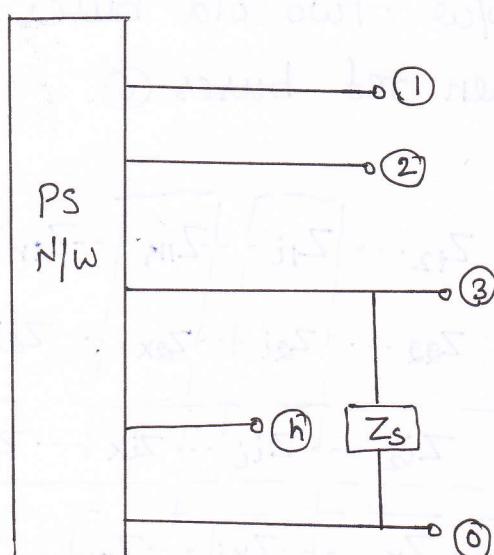An element will self impedance Z_s is added b/w already existing bus (k) & the ref. bus $\textcircled{0}$.



$$Z_{BUS, \text{old}} =$$

$k^{\text{th}} \text{ row}$

$$\begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1k} & \dots & Z_{1n} \\ Z_{21} & Z_{22} & \dots & Z_{2k} & \dots & Z_{2n} \\ \vdots & & & & & \\ Z_{k1} & Z_{k2} & \dots & Z_{kk} & \dots & Z_{kn} \\ Z_{n1} & Z_{n2} & \dots & Z_{nk} & \dots & Z_{nn} \end{bmatrix}$$

$k^{\text{th}} \text{ column}$

$$Z_{BUS, \text{new}} = Z_{BUS, \text{old}} - \frac{1}{Z_{kk} + Z_s} \begin{bmatrix} Z_{1k} \\ Z_{2k} \\ \vdots \\ Z_{kk} \\ Z_{nk} \end{bmatrix} [Z_{k1}, Z_{k2}, \dots, Z_{kk}, Z_{kn}]_n$$

Exp.

$$Z_{\text{BUS, old}} = \begin{array}{|c|c|c|} \hline & \textcircled{1} & \textcircled{2} \\ \hline \textcircled{1} & 1\Omega & 1\Omega \\ \hline \textcircled{2} & 1\Omega & 3\Omega \\ \hline \end{array}$$


Now add odd 3Ω resistance.

but $K=2$ & $\textcircled{0}$

$$\begin{aligned} Z_{\text{BUS, new}} &= \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} - \frac{1}{3+3} \left[\frac{1}{3} \right] [1, 3] \\ &= \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} - \frac{1}{6} \begin{bmatrix} 1 & 3 \\ 3 & 9 \end{bmatrix} \\ &= \begin{bmatrix} 1 & 1 \\ 1 & 3 \end{bmatrix} - \begin{bmatrix} \frac{1}{6} & \frac{1}{2} \\ \frac{1}{2} & \frac{3}{2} \end{bmatrix} \\ &= \begin{bmatrix} \frac{5}{6} & \frac{1}{2} \\ \frac{1}{2} & \frac{3}{2} \end{bmatrix} \end{aligned}$$

Type-4 Modification :-

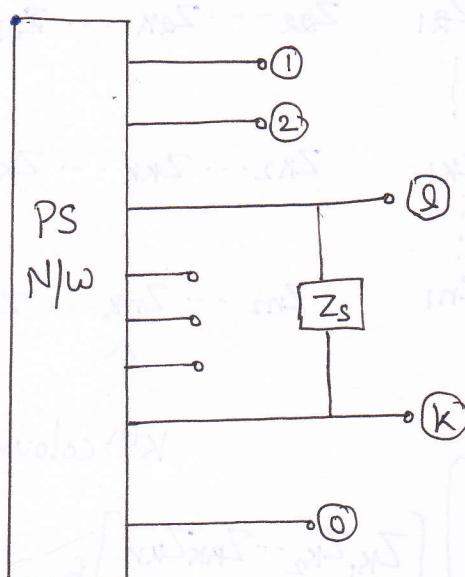An element with self impedance Z_s is added b/w two old buses $\textcircled{1}$ & \textcircled{K} other than ref. buses $\textcircled{0}$.



$$Z_{\text{BUS}} =$$

$$\begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1i} & \cdots & Z_{1K} & \cdots & Z_{1n} \\ Z_{21} & Z_{22} & \cdots & Z_{2i} & \cdots & Z_{2K} & \cdots & Z_{2n} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{Ki} & Z_{K2} & \cdots & Z_{Ki} & \cdots & Z_{KK} & \cdots & Z_{Kn} \\ Z_{n1} & Z_{n2} & \cdots & Z_{ni} & \cdots & Z_{nK} & \cdots & Z_{nn} \end{bmatrix}$$

ith row

Kth row

ith column

Kth column

$$Z_{\text{BUS, new}} = Z_{\text{BUS, old}} - \frac{1}{Z_s + Z_{KK} + Z_{ii} - 2Z_{ik}} \begin{bmatrix} Z_{ki} - Z_{kk} \\ Z_{2i} - Z_{2k} \\ \vdots \\ Z_{ii} - Z_{ik} \\ Z_{ki} - Z_{kk} \\ Z_{ni} - Z_{nk} \end{bmatrix} \begin{bmatrix} Z_{i_1} - Z_{k_1} & Z_{i_2} - Z_{k_2} & \dots \\ \dots & Z_{in} - Z_{kn} \end{bmatrix}$$

From i^{th} column
subtract k^{th} column
→ to write as column

From i^{th} row
subtract k^{th} row
→ to write as a row.

Exp. $Z_{\text{BUS, old}} = \begin{array}{cc} \textcircled{1} & \textcircled{2} \\ \textcircled{1} & 5/6 \quad 1/2 \\ \textcircled{2} & 1/2 \quad 3/2 \end{array}$

$$i=1 ; k=2$$

$$Z_s = 4$$


$$Z_{\text{BUS, New}} = \begin{bmatrix} 5/6 & 1/2 \\ 1/2 & 3/2 \end{bmatrix} - \frac{1}{4 + 3/2 + 5/6 - 1 \times \frac{1}{2}} \begin{bmatrix} 1/3 \\ -1 \end{bmatrix} \begin{bmatrix} 1/3 & -1 \end{bmatrix}$$

$$= \begin{bmatrix} 5/6 & 1/2 \\ 1/2 & 3/2 \end{bmatrix} - \frac{3}{16} \begin{bmatrix} 1/9 & -1/3 \\ -1/3 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 5/6 & 1/2 \\ 1/2 & 3/2 \end{bmatrix} - \begin{bmatrix} 1/48 & -1/16 \\ -1/16 & 3/16 \end{bmatrix}$$

Chapter 3.


(2)

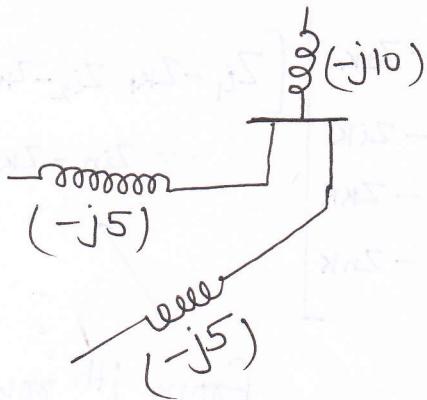

$$\begin{aligned} Y_{22} &= -j10 - j5 - j5 \\ &= -j20 \end{aligned}$$

$$\begin{aligned} (6) \quad Y_{22} &= -j10 - j10 + j0.05 \\ &= -j19.95 \text{ P.U.} \end{aligned}$$
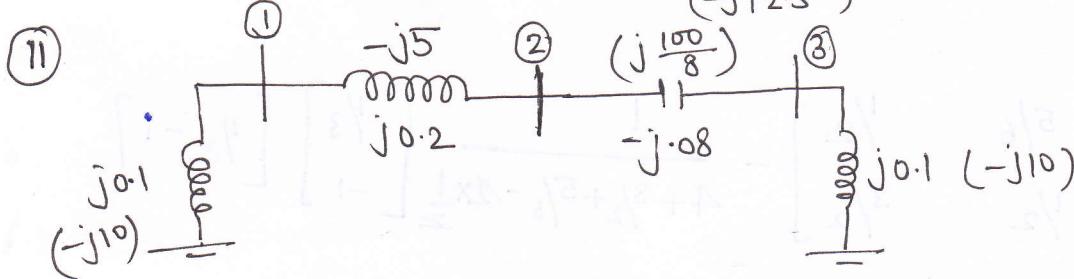
$$(7) \quad Y_{\text{BUS}} = Z_{\text{BUS}}^{-1} = \frac{1}{.9 \times .6 - .2 \times .2} \begin{bmatrix} .6 & .2 \\ -.2 & 0.9 \end{bmatrix} = 1.8 \text{ P.U.}$$



$$= j \begin{bmatrix} 15 & 5 & 0 \\ 5 & 7.5 & -12.5 \\ 0 & -12.5 & 2.5 \end{bmatrix}$$

$\frac{P-52}{30}$

$$Z_s = j0.2 \Omega$$

Connected but bus ② is ref.

Type-3 Modification :-


$$k = 2$$

$$Z_{\text{BUS, new}} = Z_{\text{BUS, old}} - \frac{1}{Z_{22} + Z_s} \begin{bmatrix} j \cdot 2860 \\ j \cdot 3408 \\ j \cdot 2586 \\ j \cdot 2414 \end{bmatrix} \begin{bmatrix} j0.2860 & j0.3408 \\ j0.2586 & j0.2414 \end{bmatrix}$$

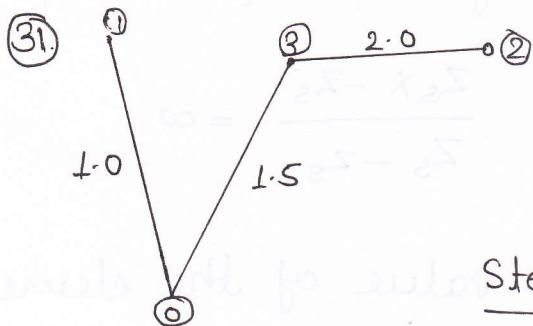
(10)

$$Z_{22, \text{new}} = j \cdot 3408 - \frac{1}{j \cdot 3408 + j \cdot 2} \times j \cdot 3408 \times j \cdot 0 \cdot 3408 \\ = j \cdot 1260 \Omega$$

$$Z_{23, \text{new}} = j \cdot 0.2586 - \frac{1}{j \cdot 3408 + j \cdot 0 \cdot 2} \times j \cdot 3408 \times j \cdot 0 \cdot 2586 \\ = j \cdot 0.095 \Omega$$




$$\underline{\text{add } L\Omega} \\ Z_{Bws} = \begin{array}{|c|c|c|} \hline 1 & 0 & 0 \\ \hline 0 & 1 & 0 \\ \hline 0 & 0 & 0 \\ \hline \end{array}$$

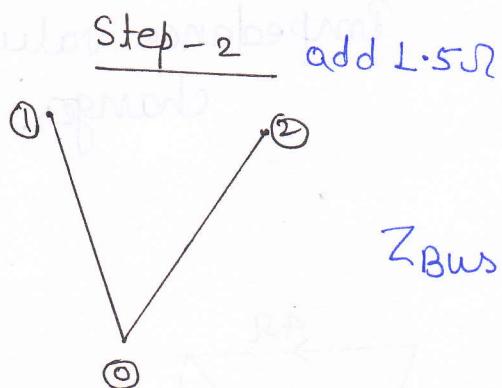

$$Z_{Bws} = \begin{array}{|c|c|c|} \hline 1 & 0 & 0 \\ \hline 0 & 1 & 0 \\ \hline 0 & 0 & 0 \\ \hline \end{array}$$

Step-3 add 2Ω $K=3$ $a=2$

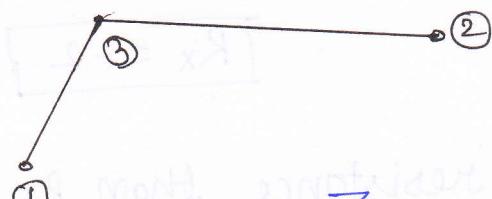

$$Z_{Bws} = \begin{array}{|c|c|c|} \hline 1 & 0 & 0 \\ \hline 0 & 1.5 & 1.5 \\ \hline 0 & 1.5 & 3.5 \\ \hline \end{array}$$


$$\boxed{Z_{22} = 3.5 \Omega}$$

* Element Deletion:-

A self impedance Z_s connected b/w buses ① & ②
bus to be removed say.

→ The procedure is add $-Z_s$ across buses ① & ②


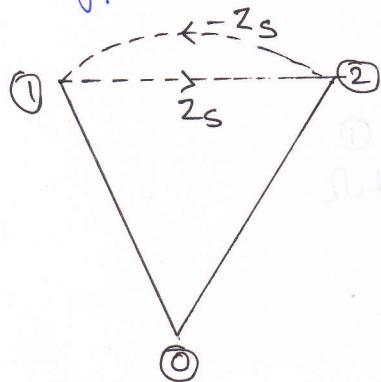
→ Type - 3 OR 4 modification may be required to perform



$$Z_{s||-Z_s} = \frac{Z_s \times -Z_s}{Z_s - Z_s} = \infty$$

Impedance value of the element changes.


Exa:-

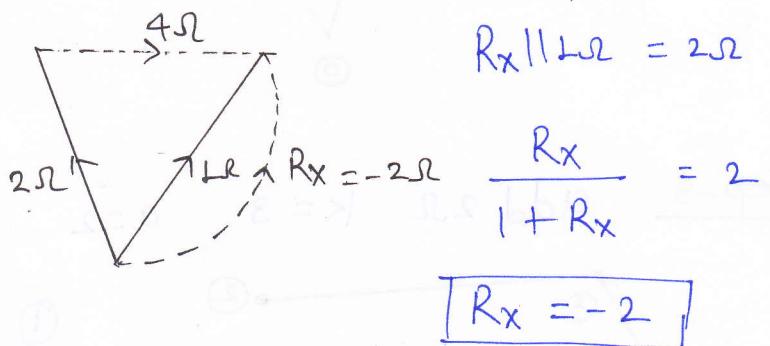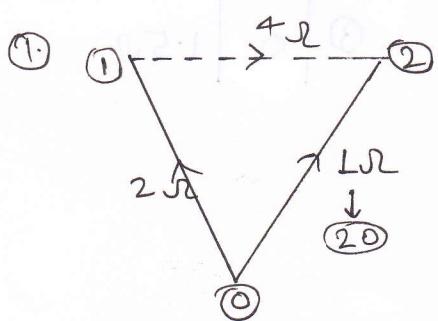

** If increase effective resistance then R_x should negative, If take decrease resistance then R_x should positive.

Ex- Find R from 1Ω to 2Ω

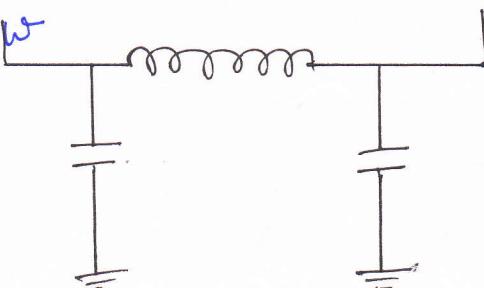* In load flow the N/w always represent in a N/w not in TN/w



PER UNIT METHOD

- A per unit method uses per unit (P.u) values
- A per unit value is a unit less quantity.
- P.u. Value = $\frac{\text{Actual value in same unit}}{\text{Base or ref. value in same unit}}$

Ex:- $V_a = 400 \text{ kV}$

$$V_b = 100 \text{ kV}$$

$$V_{pu} = \frac{400 \text{ kV}}{100 \text{ kV}} = 4 \text{ P.u}$$

+ P.u voltage = 100 kV

Ex- $V_a = 400 \text{ kV}$

$$V_b = 400 \text{ kV}$$

$$V_{pu} = \frac{400 \text{ kV}}{400 \text{ kV}} = 1 \text{ P.u}$$

+ P.u voltage = 400 kV

P.u value $\times 100 = \%$ value

Advantage of P.u. method -

- (1) It simplifies power system calculation.
- (2) It avoids the discontinuity problem posed by the presence of T/F in P.S. N/w

Explanation →

