

or $\frac{dq(t)}{q(t)} = -\frac{dt}{RC} \Rightarrow$ Integrating we have, $\ln q - \ln q_0$

$= -t/RC$

or $q = q_0 e^{-t/RC}$

Thus the capacitor discharges through a load R , ~~exponent~~ and its charge gets decays exponentially.

Now, Defⁿ of time constant for a system relaxing exponentially will be given by, is the time 't' it takes to decay some quantity (q here) from its initial value and becomes $\frac{1}{e}$ of that initial value

Thus time constant or relaxation time $\tau = RC$ (here)

• So what happens in a case of a capacitor filter while its input is given by the output of a full wave rectifier circuit will be like this:-

The charge being ~~is~~ proportional to applied voltage, initially for the rising part of the input voltage the capacitor gets charged and q reaches its peak value q_m at $V = V_m$.

Then ~~at the~~ no more charging happens and now if a load is connected across the capacitor, it

→ it will start to discharge through the load until the input voltage becomes equal or greater than instantaneous voltage of the capacitor. Then again it