

# Potentiometer

It is a versatile instrument. It is basically a long piece of wire uniform wire 5-7 m in length.

Principle A current  $I$  flows through wire which can be varied by variable resistance ( $R$ ) in the circuit.

Principle: As the wire is uniform, the potential difference b/w  $A$  and at any point at distance  $l$  from  $A$  is

$$\boxed{\mathcal{E} = \phi l} \quad \text{--- (1)}$$


↪ potential drop per unit length.

## Application

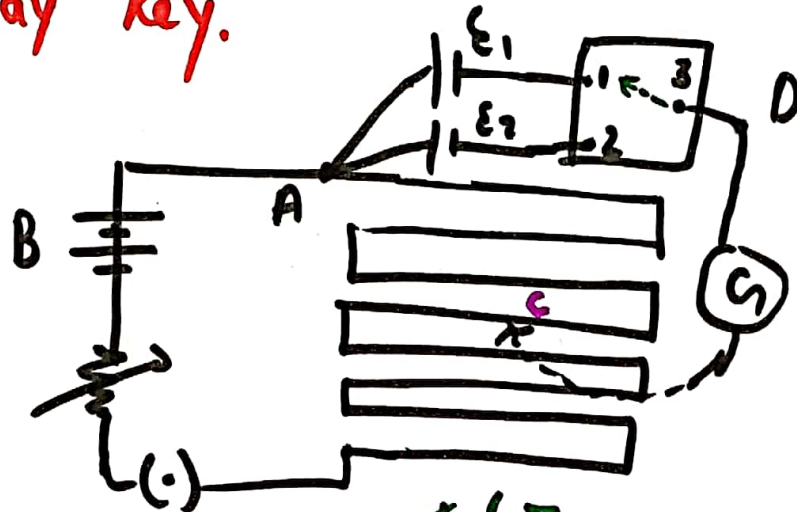- (i) To compare the EMF of two cells
- (ii) To measure internal resistance of cell.

1<sup>st</sup> Application: To compare EMF of cell.

Consider a two cell of emf  $\epsilon_1$  &  $\epsilon_2$  connected to potentiometer using two way key.



let in first key ~~1 & 2~~ <sup>1 & 3</sup> is connected so that Galvanometer is connected to  $\epsilon_1$ .  
let at point C there is no deflection in Galvanometer.

Apply KVL in loop ACDA

$$\oint \epsilon_{AC} - \epsilon_1 = 0$$

$$\oint l_1 - \epsilon_1 = 0 \quad \text{--- (2)}$$

Similarly for another cell, key 2 & 3 is connected & null deflection at ~~new point~~ new point  $C'$

$$\epsilon_{AC'} - \epsilon_2 = 0$$

$$\phi l_2 - \epsilon_2 = 0 \quad \text{--- (3)}$$

Using (2) & (3)

$$\phi l_1 = \epsilon_1 \quad \text{--- (4)}$$

$$\phi l_2 = \epsilon_2 \quad \text{--- (5)}$$

$$(4) \div (5)$$

$$\frac{\phi l_1}{\phi l_2} = \frac{\epsilon_1}{\epsilon_2}$$


$$\boxed{\frac{\epsilon_1}{\epsilon_2} = \frac{l_1}{l_2}}$$

Comp. of emf of two cell.

If one of cell EMF is known then other cell emf can be calculated.

II Application: To measure internal resistance of cell.

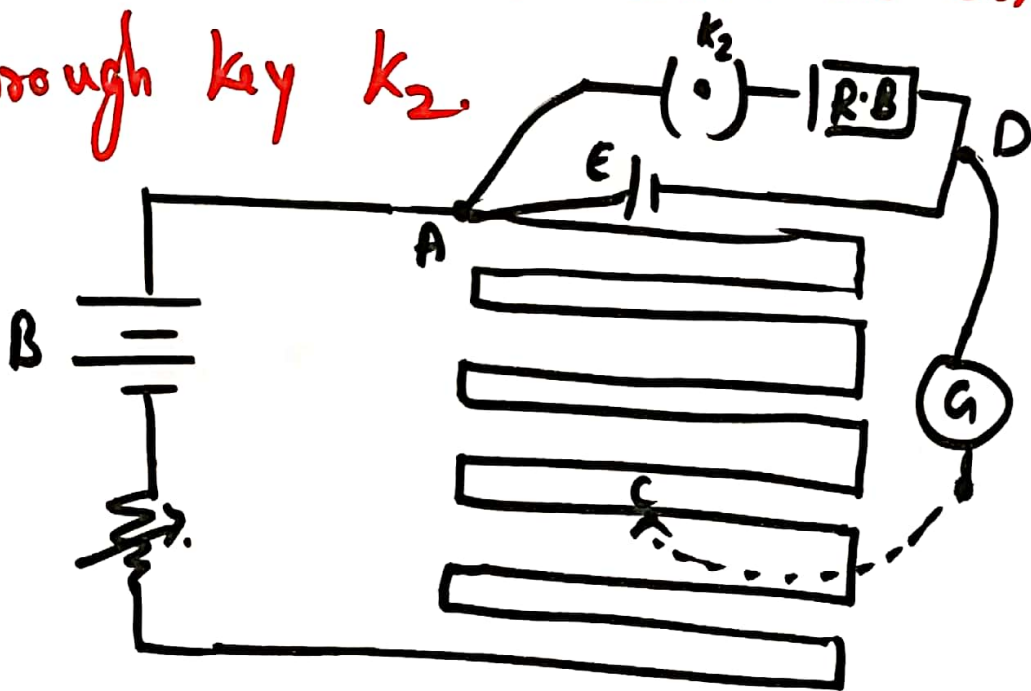Consider a cell of emf  $\mathcal{E}$  whose internal resistance ( $r$ ) is unknown is connected across resistance box through key  $k_2$ .



When key  $k_2$  is open, balance (zero deflection) is obtained at length  $l_1$ ,

$$\mathcal{E} = \phi l_1 \quad \text{--- (1)}$$

When key  $k_2$  is closed, the cell sends a current ( $I$ ) through resistance box ( $R$ ).

If  $V$  is terminal potential difference of cell, a balance (zero deflection) obtained at length  $l_2$

$$V = \phi l_2 \quad \text{--- (2)}$$

① ÷ ②

$$\frac{\mathcal{E}}{V} = \frac{l_1}{l_2} \quad \text{--- ③}$$

We know.

$$\mathcal{E} = I(r + R)$$

$$V = IR$$

Put in ③

$$\frac{\cancel{I}(r+R)}{\cancel{I}R} = \frac{l_1}{l_2}$$

$$r l_2 + R l_2 = R l_1$$

$$r l_2 = R (l_1 - l_2)$$

$$r = \frac{R}{l_2} (l_1 - l_2)$$

$$r = R \left( \frac{l_1}{l_2} - 1 \right)$$

where.  $r \rightarrow$  internal resistance of cell  
 $R \rightarrow$  value of resistance from resistance box.