

Capacitor :- (device.)

Some electric device requires very high current (25-50A) to start them like motor, fan, - camera flash.

\* "capacitor stores Electrical Energy" & supplies it at ONCE. (suddenly.)

\* capacitor is a device which stores Electric charge.

\* Capacitance (property.)

Ability to hold Electrical Energy.

$$C = \frac{Q}{V}$$

→ C is independent of Q & V

→ C depends on, conductor & properties of medium.  
dimension.

$$\left( \text{Unit} = \frac{C}{V} = \frac{\text{Coulomb}}{\text{Volt}} \right) = F.$$


Note :-  $C = 1F$  i.e.  $\frac{1C}{V} \Rightarrow$  if 1C is given to this conductor potential  $\uparrow$  by 1 Volt

$C = 2F \rightarrow 2C \rightarrow 1V \uparrow$ .

$C = 10F \rightarrow 10C \text{ charge} \Rightarrow$  potential  $1V \uparrow$ .



\* Spherical capacitor / conductor :-

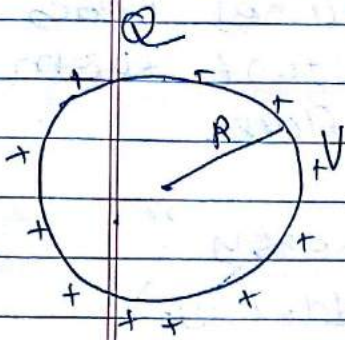

$$C = \frac{Q}{V} = \frac{Q}{\frac{kQ}{R}} = \frac{R}{k} = \frac{1}{4\pi\epsilon_0}$$

$$C = 4\pi\epsilon_0 R$$

→ C depends on dimension (R)  
 → medium ( $\epsilon_0$ ) air.

Q. R = 1m, Find capacitance

$$\therefore C = 4\pi\epsilon_0 R$$

$$= \frac{1}{9 \times 10^9} = 1.1 \times 10^{-10} \text{ F}$$


Q.  $C = 1 \text{ F} \Rightarrow R = \frac{1}{4\pi\epsilon_0} \Rightarrow 9 \times 10^9 \text{ m}$   
 ↓  
 very Big.

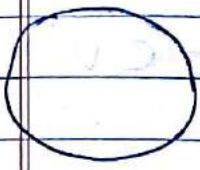problem → For this kind of capacitor capacitance is smaller but size is very Big.



Q

Energy stored in a capacitor (spherical) :-



work done by external agent to bring each dq element from  $\infty$  to this sphere  $\rightarrow$  stores in form of P.E.

$t=0, Q=0, V=0$

$t=t, Q=q, V=q/C$

$t=\infty, Q=Q, V=Q/C$

$\rightarrow$  work done to bring dq charge from  $\infty$  to sphere...

$dW = q/dV \cdot dV = V dq$   
 $dW = \frac{q}{C} dq$

$\rightarrow$  total work by external force

$W_{ext} = \int_0^Q dW = \int_0^Q q dq = \frac{1}{2} (q^2)_0^Q$

$\therefore W_{ext} = \frac{Q^2}{2C} = \underline{\underline{P.E. = \Delta U}}$

$\rightarrow \Delta U = -W_{elec. force} = +W_{ext.}$

$\therefore \Delta U = \frac{Q^2}{2C}$

$\therefore U_f - U_i = \frac{Q^2}{2C}$

$\therefore U - 0 = \frac{Q^2}{2C}$

(In starting no P.E.)

$\therefore U = \frac{Q^2}{2C}$



\* P.E. of spherical conductor }  $U = \frac{Q^2}{2(4\pi\epsilon_0 R)}$

\*  $\rightarrow U = \frac{Q^2}{2C} = \frac{(CV)^2}{2C} \quad (\because Q = CV)$



C & V  $\rightarrow \boxed{U = \frac{1}{2} CV^2}$

Q & V  $\rightarrow U = \frac{Q^2}{2C} = \frac{Q^2}{2(Q/V)} = \boxed{\frac{1}{2} QV = U}$

- Limits :-
- i) low capacitance  $C \downarrow$
  - ii) P.E. losses for attracting nearer charges.  
(i.e. Energy is not bounded.)  
distributed  $Q \rightarrow \infty$ .



\* Parallel plate capacitor :-

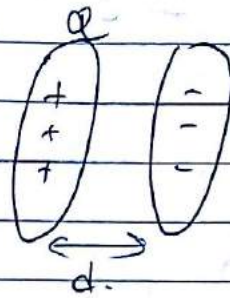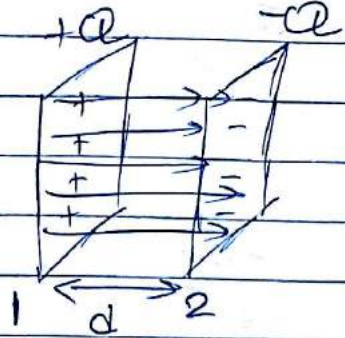

Conditions

i)  $d \ll \text{Area}$ .

ii)  $A_1 = A_2$ .

→ plates behave as  $\infty$  plane.

# capacitance :-  $C = \frac{Q}{\Delta V}$  — charge on plate  
 → p.d. b/w plate.  
 (1)

# Electric field due to first plate }  $E_1 = \frac{\sigma}{2\epsilon_0} \rightarrow$   
 $E_2 = \frac{\sigma}{2\epsilon_0} \rightarrow$

$$\therefore E_{\text{net}} = E_1 + E_2$$

$$= \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0} = E$$

$$\rightarrow \boxed{E = \frac{Q}{A\epsilon_0}}$$

$$\rightarrow \boxed{\Delta V = E d = \frac{Q \cdot d}{A\epsilon_0}} \quad (2) \quad \left( \because dV = -E \cdot dl \right)$$


$$\rightarrow \text{Put (2) in (1) :- } C = \frac{Q}{\frac{Q \cdot d}{A\epsilon_0}} = \frac{\epsilon_0 A}{d}$$

$$\boxed{C = \frac{\epsilon_0 A}{d}}$$



$$Q \quad \text{P.E.} \quad \left. \vphantom{\text{P.E.}} \right\} \quad V = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

Q:-

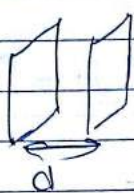

⇒



Find


$$W_{\text{ext}} = \Delta U = U_f - U_i$$

$$= \frac{Q^2}{2C_f} - \frac{Q^2}{2C_i} = \frac{Q^2}{2\epsilon_0 A (2d)} - \frac{Q^2}{2\epsilon_0 A d}$$

$$W_{\text{ext}} = \frac{1}{2} \frac{Q^2}{\epsilon_0 A d} = \frac{Q^2 d}{2\epsilon_0 A}$$

Q Force on one plate of capacitor due to other plate.

For one plate.

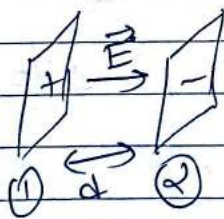

$$E_{\text{net}} = \frac{Q}{2\epsilon_0 A} - \frac{Q}{2\epsilon_0 A}$$

$$F_{\text{net}} = QE_{\text{net}}$$

$$= Q \left( \frac{Q}{2\epsilon_0 A} \right) = \frac{Q^2}{2\epsilon_0 A} = F_{\text{net}}$$

$$\rightarrow W_{\text{ext}} = F \times d = \frac{Q^2 d}{2\epsilon_0 A}$$




(charge distribution on cups)

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

Q what if different charge on each plate

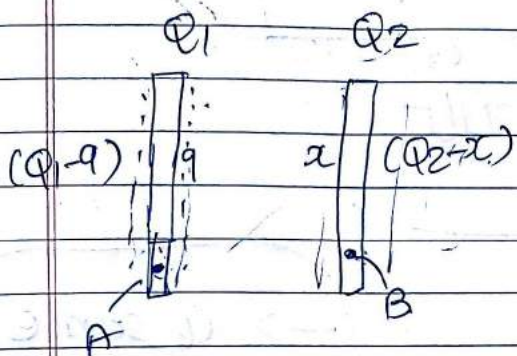

$$\therefore E_A = \frac{(Q_1 - q)}{2A\epsilon_0} - \frac{q}{2A\epsilon_0}$$

$$- \frac{x}{2A\epsilon_0} - \frac{(Q_2 + x)}{2A\epsilon_0}$$

$E_A = E_B = 0$   
(inside conductor)


$$\therefore 0 = \frac{1}{2A\epsilon_0} [Q_1 - q + x - x - Q_2 - x]$$

$$0 = Q_1 - Q_2 - 2q \quad \text{--- (i)}$$

$$\therefore q = \frac{Q_1 - Q_2}{2}$$

$$E = \frac{\sigma}{2\epsilon_0} = \frac{Q}{2A\epsilon_0}$$
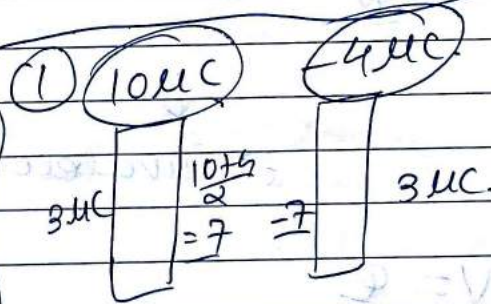
$$E_B = \frac{Q_2 + x}{2A\epsilon_0} - \frac{x}{2A\epsilon_0} - \frac{q}{2A\epsilon_0} - \frac{(Q_1 - q)}{2A\epsilon_0}$$





$$Q_2 - Q_1 - 2x = 0 \quad \text{--- (ii)}$$

$$\therefore x = \frac{Q_2 - Q_1}{2}$$

$$x = -q$$



(2)

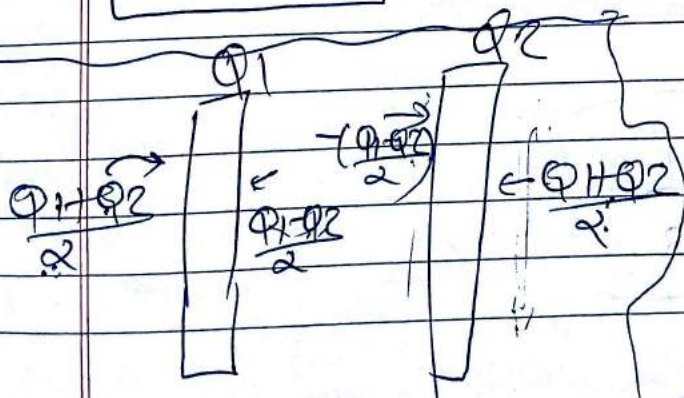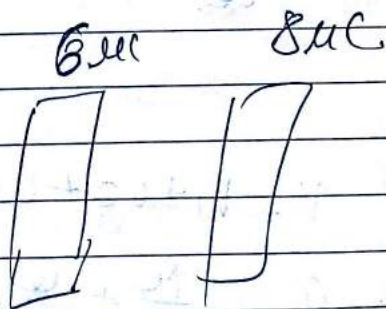



# \* combination of capacitors :-

i) Series.

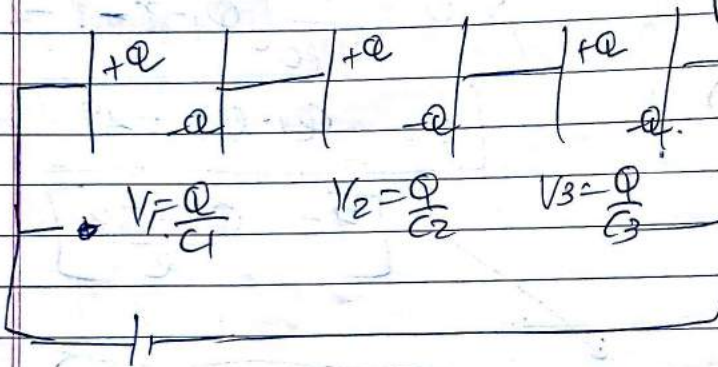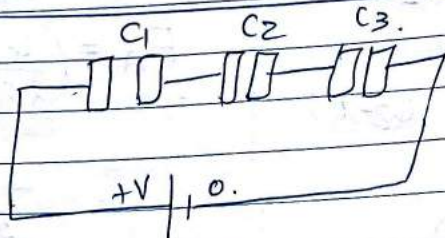


→ Q same  
→ V diff.

$$V \propto \frac{1}{C}$$

$$\Rightarrow V = V_1 + V_2 + V_3$$

Equivalent

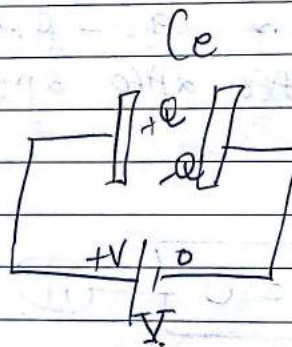

$$\rightarrow V = \frac{Q}{C_e}$$


$$\therefore V = V_1 + V_2 + V_3$$

$$\therefore \frac{Q}{C_e} = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\therefore \frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$




ii) Parallel

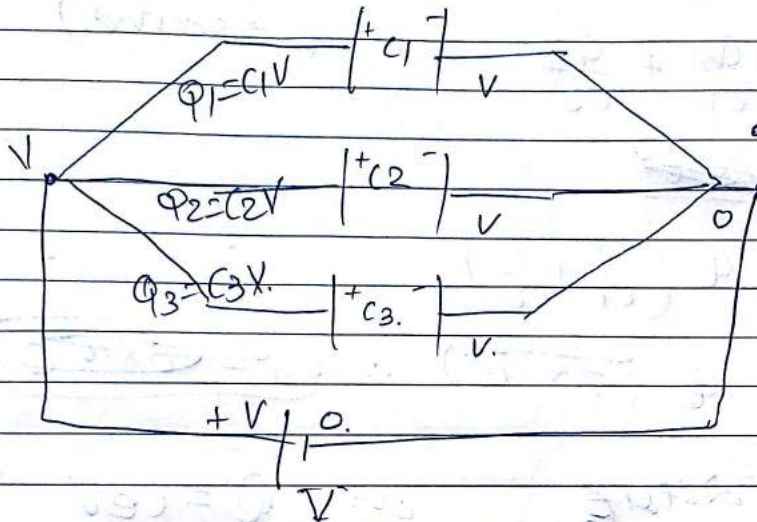

- $V$  same
- $Q$  diffnt

$$Q = Q_1 + Q_2 + Q_3$$

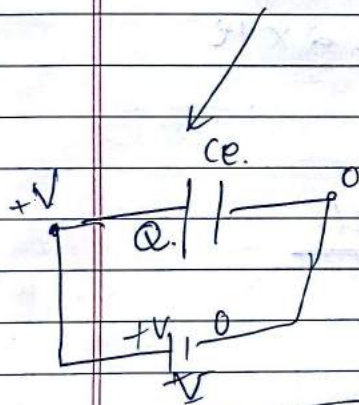


$$\therefore Q = Q_1 + Q_2 + Q_3$$

$$C_e V = C_1 V + C_2 V + C_3 V$$

$$\therefore C_e = C_1 + C_2 + C_3$$

$$\therefore C_e = \frac{Q}{V}$$

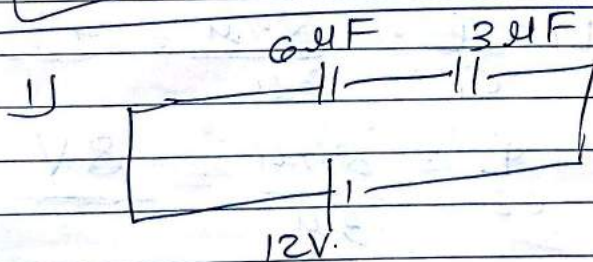

Find.

i)  $C_e$

ii)  $Q$  on each capa

iii)  $V$  on each capa

iv) Energy in  $3 \mu F$  capa stored.

$$\rightarrow C_e = \frac{C_1 C_2}{C_1 + C_2} = \frac{6 \times 3}{6 + 3} = 2 \mu F$$



$$Q = CV$$

classmate

Date

Page

$$\rightarrow V = V_1 + V_2$$

$$\therefore 12 = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} \quad (Q = \text{same})$$

$$= \frac{Q}{2 \times 10^{-6}}$$


$$\therefore 12 = Q \left( \frac{1}{C_1} + \frac{1}{C_2} \right)$$

$$\therefore 12 = Q \left( \frac{1}{2 \times 10^{-6}} \right) \therefore \boxed{Q = 6 \times 10^{-6} \text{ C}}$$

$$\boxed{Q = 24 \mu\text{C}}$$

$$\text{or } Q = CV = 2 \times 12$$
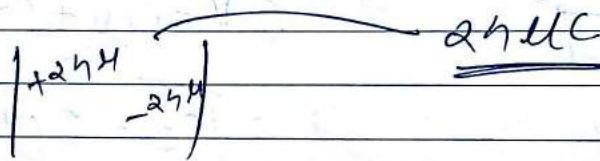
$$\rightarrow \text{ii) } C = 6 \mu\text{F}$$



$$\rightarrow \text{iii) } Q = CV$$

$$\therefore C_1 = \frac{Q}{V_1} \Rightarrow V_1 = \frac{Q}{C_1} = \frac{24 \mu\text{C}}{6 \mu\text{F}} = \underline{4 \text{ V}}$$


$$V_2 = \frac{Q}{C_2} = \frac{24 \mu\text{C}}{3 \mu\text{F}} = \underline{8 \text{ V}}$$

$\rightarrow$  (iv) Energy in  $3 \mu\text{F}$  cap.

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (3 \times 10^{-6}) (8)^2 = \underline{\underline{96 \mu\text{J}}}$$



Q.:-

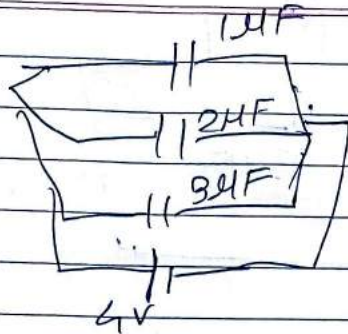i)  $C_e$ ii)  $Q$  in each cap.

iii) p.d. in each cap

iv) Energy stored in  $2\mu F$ .

$$V = 4V = V_1 = V_2 = V_3$$

$$\rightarrow \text{i) parallel } \Rightarrow C_0 = C_1 + C_2 + C_3 = \underline{6\mu F}$$

$$\rightarrow \text{ii) } V \text{ will be same, } Q = C_e V$$

$Q$  different

$$\therefore Q = 6 \times 10^{-6} (4)$$

$$\boxed{Q = 24 \mu C}$$

$$\therefore Q_1 = C_1 V$$

$$= 1 \mu \times 4$$

$$\boxed{Q_1 = 4 \mu C}$$

$$Q_2 = C_2 V$$

$$= 2 \mu \times 4$$

$$\boxed{Q_2 = 8 \mu C}$$

$$Q_3 = C_3 V$$

$$= 3 \mu \times 4$$


$$\boxed{Q_3 = 12 \mu C}$$

$$\rightarrow \text{iii) } V_1 = V_2 = V_3 = V = 4V$$

$$\rightarrow \text{iv) } U = \frac{1}{2} C V^2 = \frac{1}{2} (1 \mu) (16) = 8 \mu J$$



Q3)



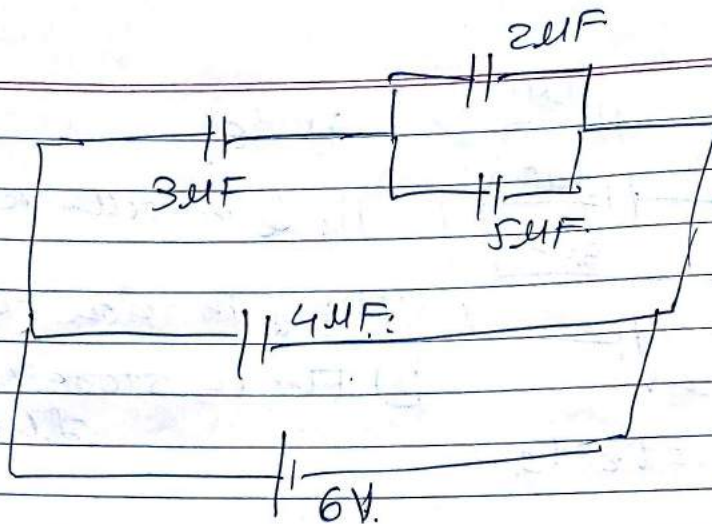


Find ratio of charge on  $5\mu\text{F}$  capd. to  $4\mu\text{F}$  capacitor.

→  $Q = CV$

$\therefore Q = 4\mu(6)$

$Q_1 = 24\mu\text{C}$

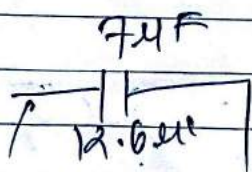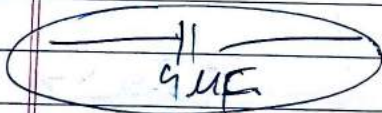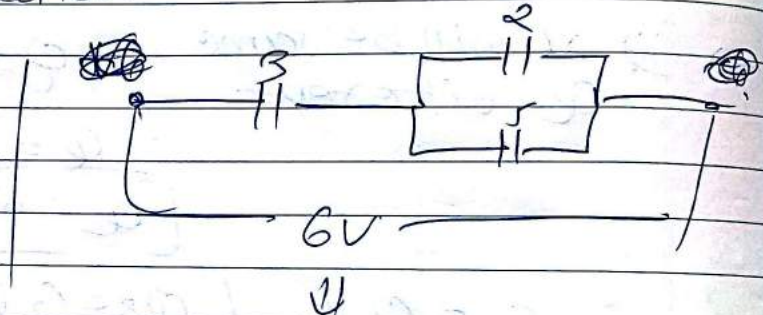


$V = \frac{Q}{C} = \frac{12.6}{7} = 1.8\text{V}$

$\therefore Q = CV$   
 $= 20 \times 6\mu$   
 $= 120\mu\text{C}$

Q:-



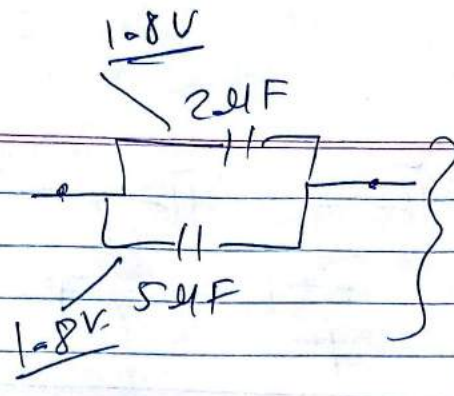


$$Q = CV$$


$$= 5\mu \times 1.8$$

$$Q_2 = 9\mu C$$
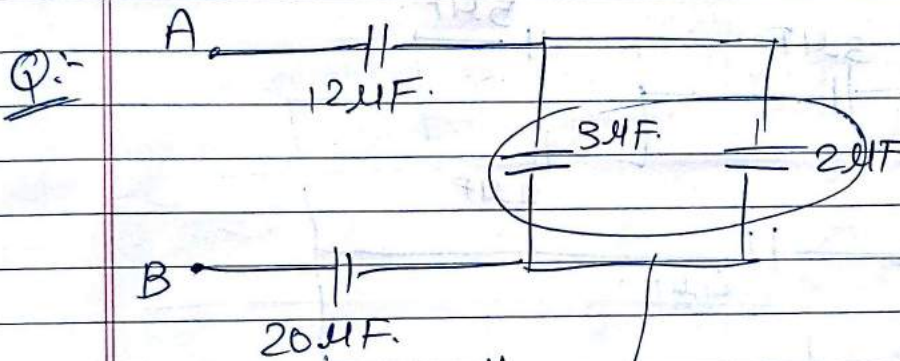
$$\therefore \frac{Q_2}{Q_1} = \frac{3 \times 9\mu C}{8 \times 24\mu C} = \frac{3}{8}$$



Find  $C_e$   
b/w A & B.

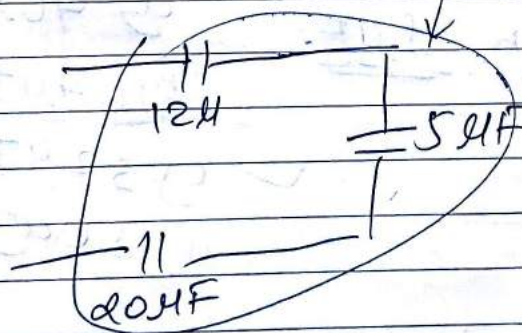

→ series

$$\therefore \frac{1}{C_e} = \frac{1}{5} + \frac{1}{12} + \frac{1}{20}$$


$$= \frac{12 + 5 + 3}{60}$$

$$= \frac{20}{60} = \frac{1}{3}$$

$$C_e = 3\mu F$$




Q:-

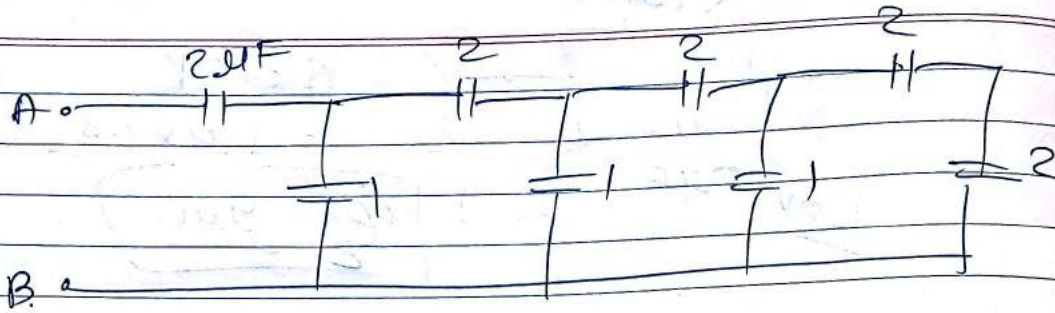

Find Eq. capacitance b/w A & B.

∴ Ans. 1 μF

Q:-

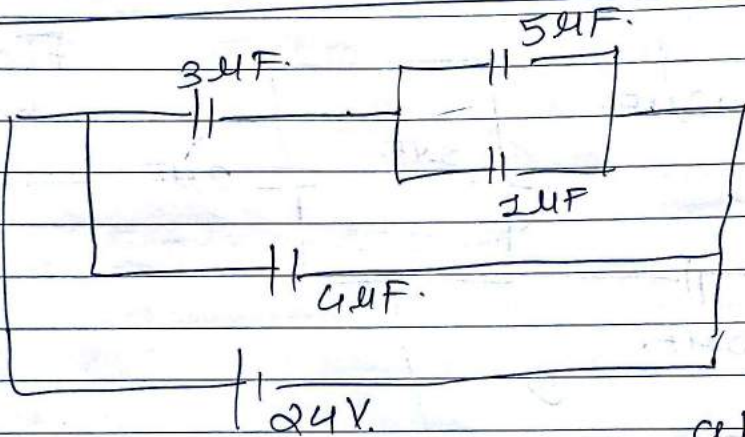

Energy stored in 1 μF

a) 40 μJ

b) 64 μJ

c) 32 μJ


d) 80 μJ

Q:-






\* combination of capacitors continue - - - -

i) ~~wired~~ connection problem.

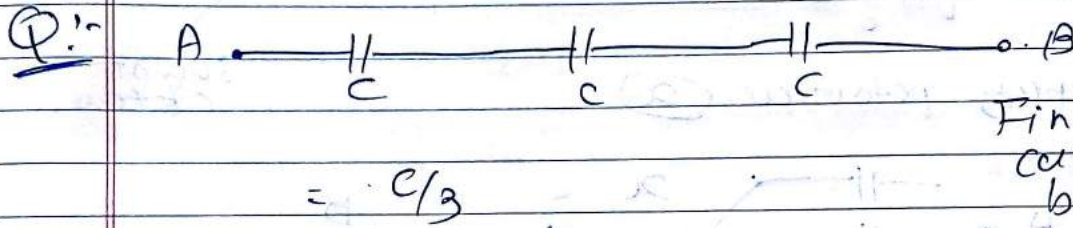


Find eq. cap. b/w A & B

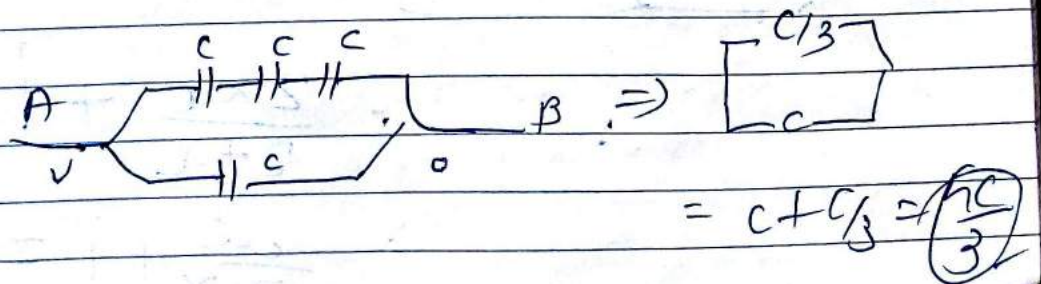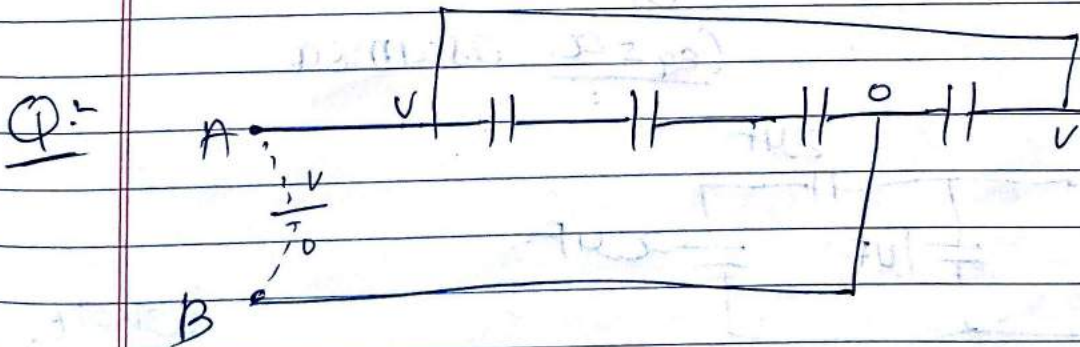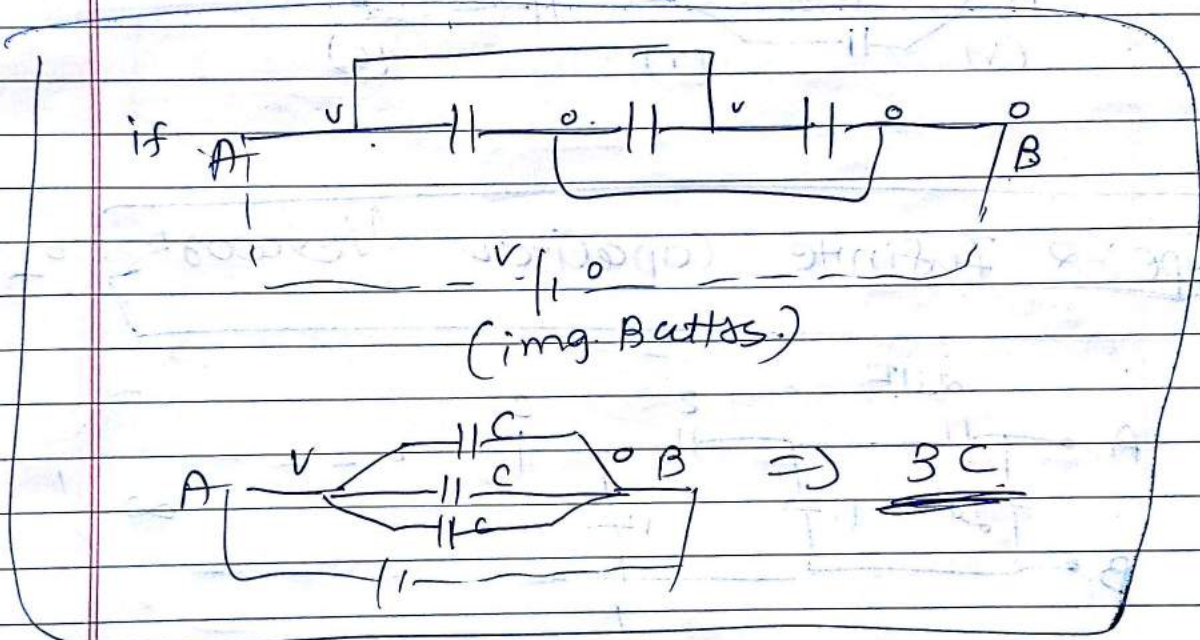




(3)

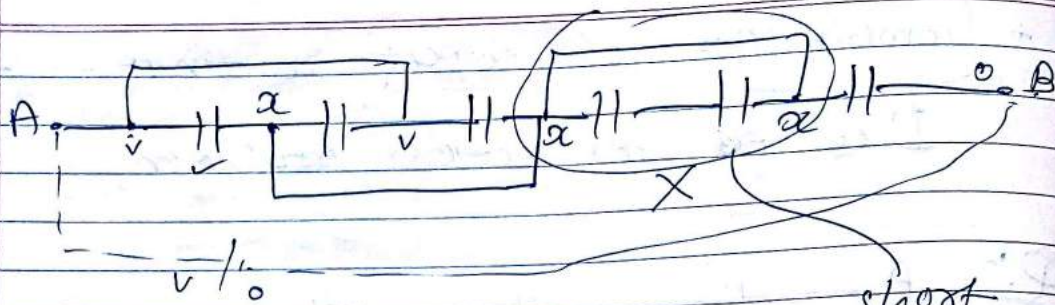


imaginary potential  $\alpha$

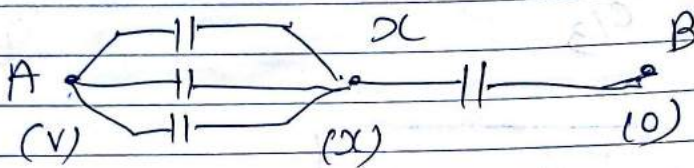


short ckted

Type:- 2 Infinite Capacitor Network

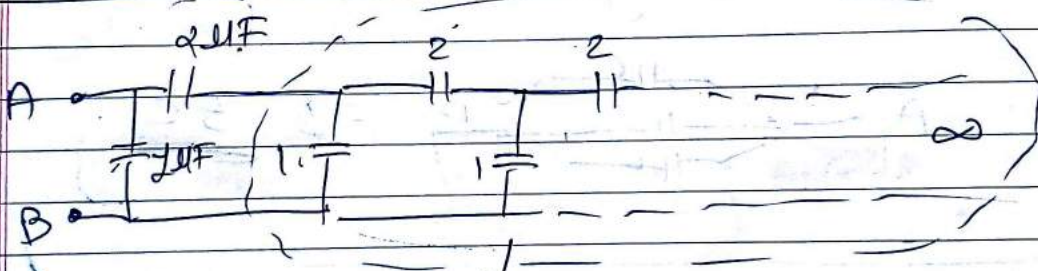

$C_{eq} = \alpha$  assumed

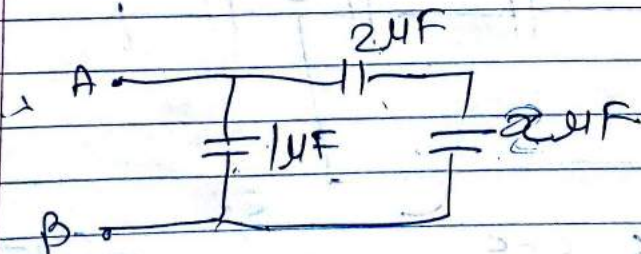

whole

$$\frac{2 \times \alpha}{2 + \alpha} + 1 = C_{eq}$$

$$\therefore \frac{2\alpha}{2 + \alpha} + 1 = \alpha$$

(2)





$$\therefore x = \frac{2+2x}{2+x} = \frac{2+3x}{2+x}$$



$$\therefore 2x+x^2 = 2+3x$$

$$\therefore x^2 - x - 2 = 0 \quad \therefore x^2 - 2x + x - 2 = 0$$

$$\therefore x(x-2) + 1(x-2) = 0$$

$$\therefore x = 2 \quad \text{or} \quad x = -1$$
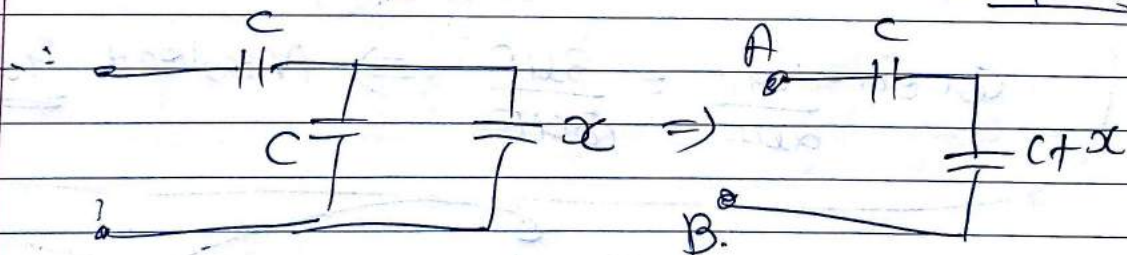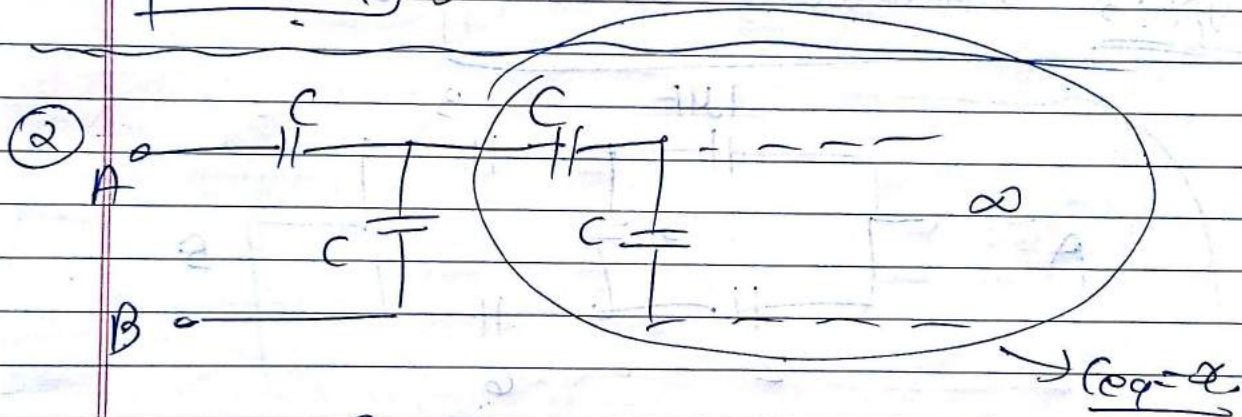
$$\boxed{x = 2 \text{ M.F.}} \quad \checkmark$$



$$\frac{(C+x)C}{C+Cx} = C_{eq}$$

$$\therefore \frac{Cx + C^2}{2C+x} = C_{eq}$$

$$\therefore \cancel{2Cx} = 2Cx + 2C^2$$

$$C^2 + Cx = 2Cx + x^2$$

$$\therefore x^2 + 2Cx - Cx - C^2 = 0$$

$$\boxed{x^2 + Cx - C^2 = 0}$$





$$x = \frac{-c \pm \sqrt{c^2 + 4c^2}}{2}$$

$$x = \frac{-c \pm c\sqrt{5}}{2} \rightarrow \underline{\underline{+ve}}$$

$$\therefore x = \frac{-c + \sqrt{5}c}{2} = \frac{c(\sqrt{5}-1)}{2}$$

Type: 3 wheatstone bridge :-

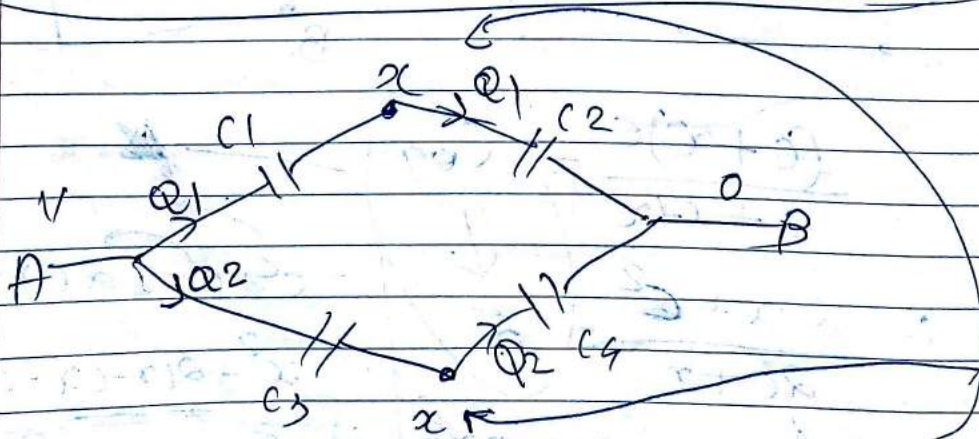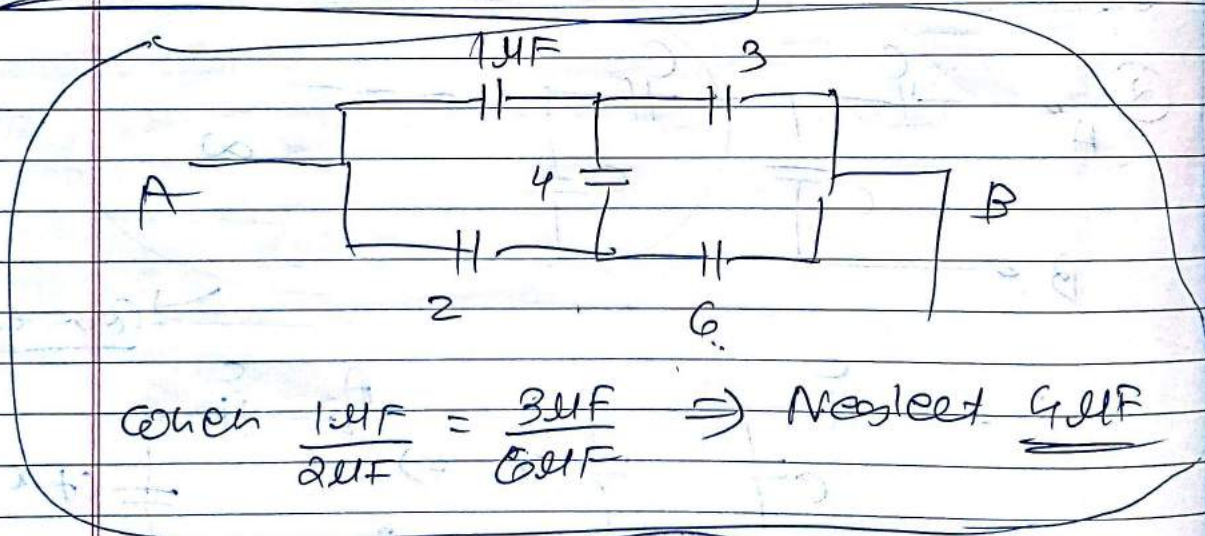

Suppose at edge potential is same

single

Q.5




$$\left. \begin{array}{l} C1 \Rightarrow (V-x) = \frac{Q1}{C1} \\ C3 \Rightarrow (V-x) = \frac{Q2}{C3} \end{array} \right\} \text{ie. } \frac{Q1}{C1} = \frac{Q2}{C3}$$

$$\boxed{\frac{Q1}{Q2} = \frac{C1}{C3}}$$



similarly

$$\left. \begin{array}{l} (x-0) = \frac{Q1}{C2} \\ (x-0) = \frac{Q2}{C4} \end{array} \right\} \Rightarrow \frac{Q1}{Q2} = \frac{C2}{C4}$$
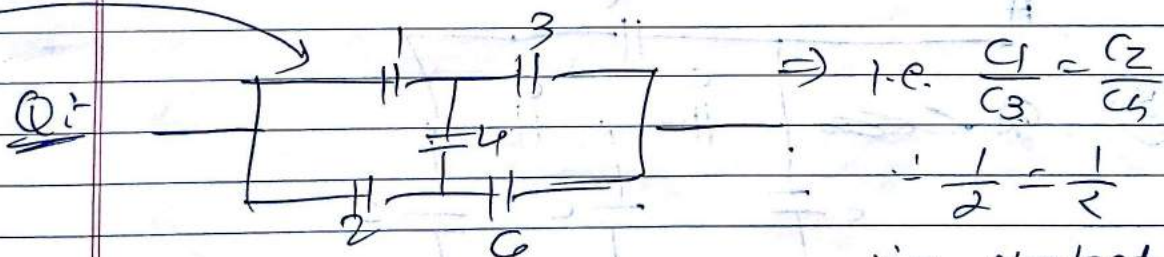
$$\therefore \boxed{\frac{C1}{C3} = \frac{C2}{C4}}$$





ie. Neglect  
4 $\mu$ C

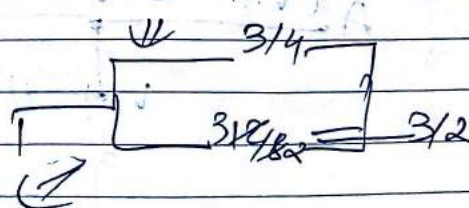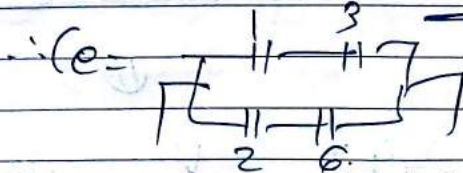

$$C = \frac{3}{4} + \frac{3}{2} = \frac{9}{4} = \boxed{2.25 \mu F}$$




(2)

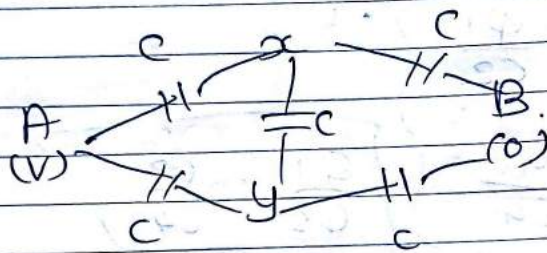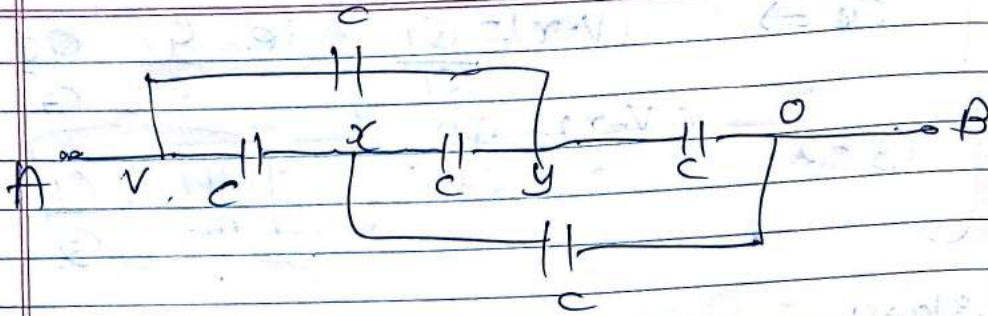

Wheatstone



i.e

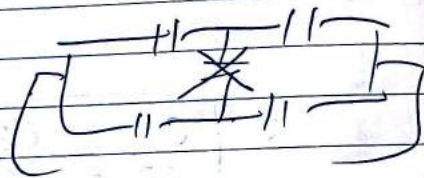

$C_{eq} = C$

TYPE 4

(3)

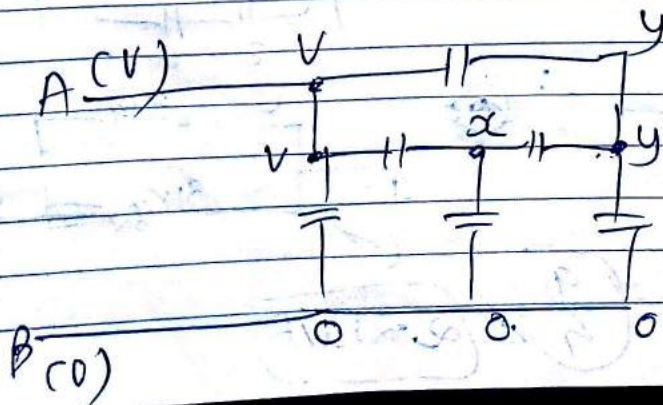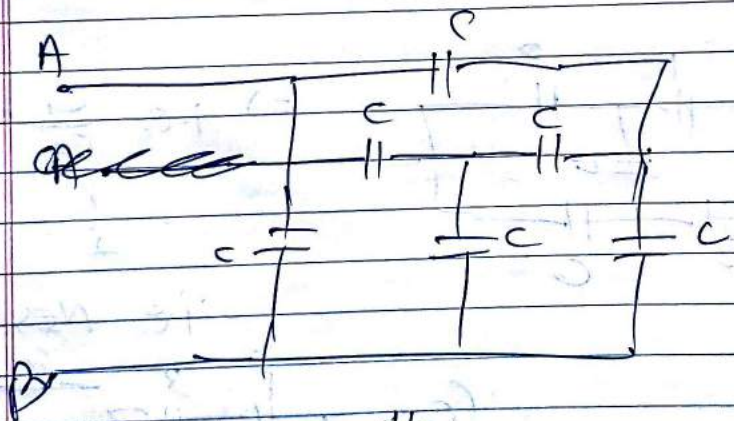


\* Fin


C

B



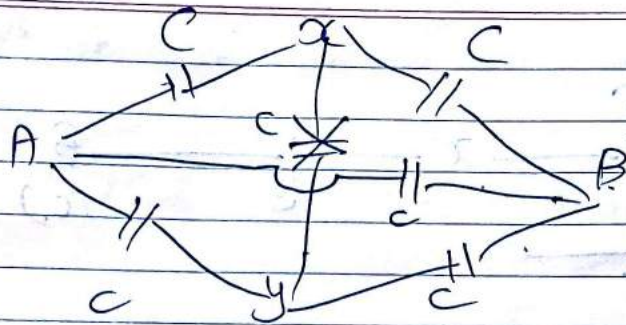

⇓

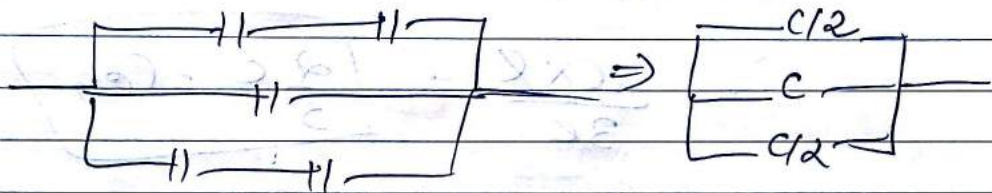


⇓

2C

**TYPE 4**

Parallel plates Problem ?

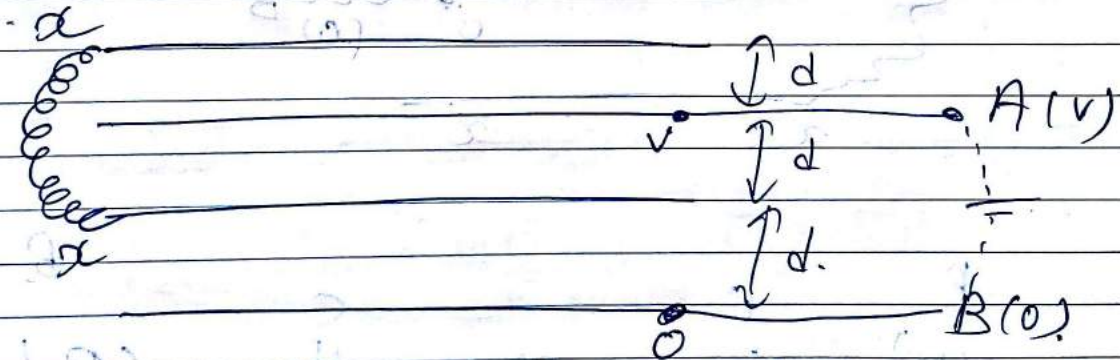


\* Find Equi. capa. b/w A & B

- (1) Area of All plate = A
  - (2) dist b/w parallel plate = d.
- } kept in mind.






$$C = \epsilon_0 \frac{A}{d}$$

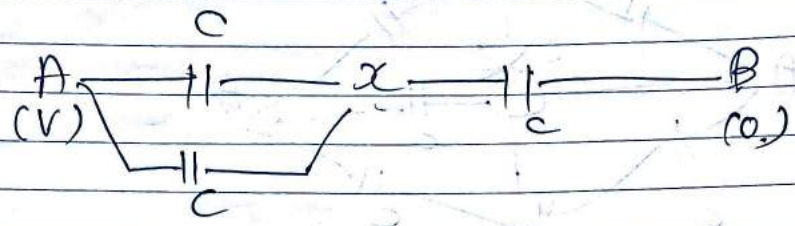

$$\frac{2Cx \times C}{3x} = \frac{2.C.C}{3} = C_{eq}$$

2

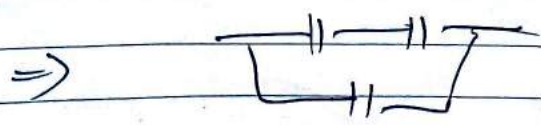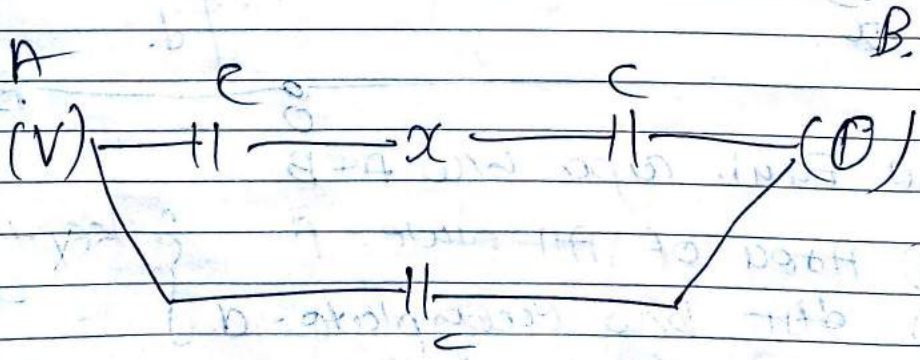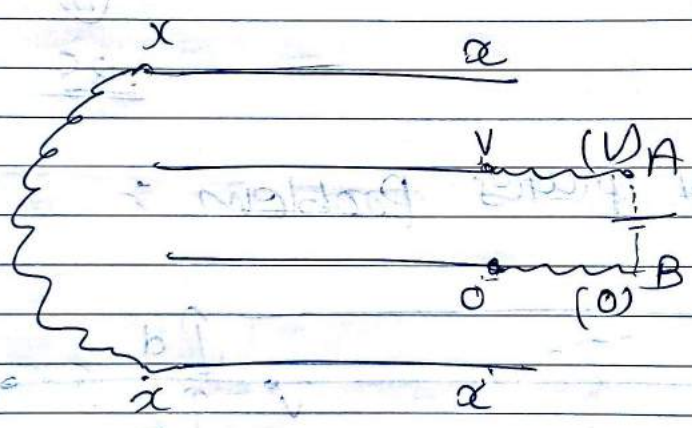




## \* Effect of Dielectrics in Capacitors :-

**Dielectric** → Don't Allow current to flow  
Allow development of  $\vec{E}$  field.

↓  
**Non-conductor** i.e. glass, mica,  
(i.e. conductor x insulator x semiconductor)

→ Electric field polarizes Dielectric material.

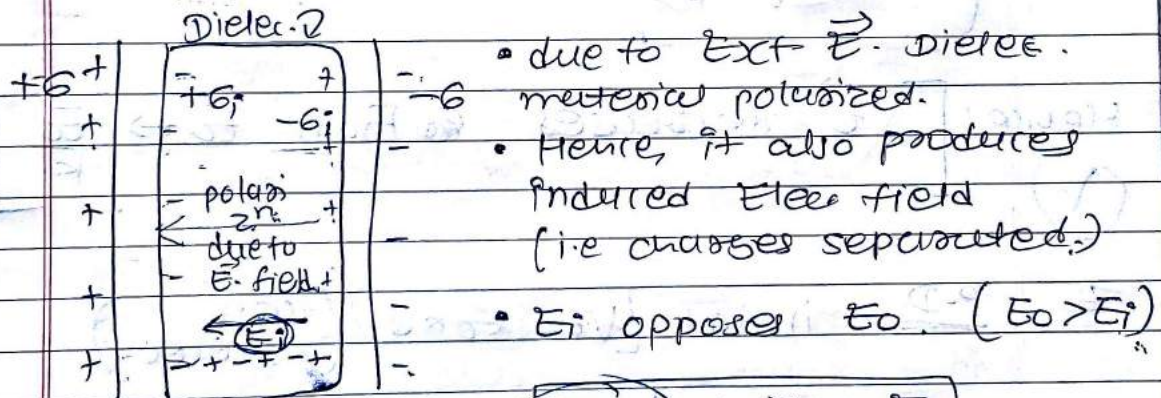→ Use. → C ↑  
→ plates are remain separated.



External E field due to plates.

$$\vec{E}_{NET} = \vec{E}_0 - \vec{E}_i$$

between plates.

•  $K =$  dielectric constant: (Every dielectric material has this.)  
(property of material.)

→ No. of times it decreases,  $\vec{E}_{NET}$  field is called as dielec. no.

(i.e.  $E_0 = 10$ ,  $E_i = 5 \Rightarrow E_{NET} = 10 - 5 = 5$ )

i.e.  $E_{NET} = \frac{E_0}{K} \Rightarrow 5 = \frac{10}{K} \Rightarrow K = 2$



Hence,  $E_{net}$  Reduces due to Dielectric.

→  $E_0 = \frac{Q}{\epsilon_0}$  (original  $E$ ) field

$\left( \begin{matrix} + \\ + \\ + \end{matrix} \right) \frac{Q}{\epsilon_0} \left( \begin{matrix} - \\ - \\ - \end{matrix} \right) \frac{Q}{\epsilon_0}$

$\therefore E_{NET} = E_0 - E_i$

$\therefore \frac{E_0}{k} = \frac{Q}{\epsilon_0} - \frac{Q_i}{\epsilon_0}$

$\therefore \frac{E_0}{k} = \frac{Q}{\epsilon_0} - \frac{Q_i}{\epsilon_0}$

$\therefore \frac{E_0}{k} = E_0 - E_i$

$E_i = E_0(1 - k)$

$E_i =$  induced charge density  
i.e. due to induced dielectric material.

NOTE

Hence,  $E$  decreases from  $E_0 \rightarrow \frac{E_0}{k}$

(1)

# P.D. initial ( $V_0 = E_0 d$ ) (w.o. Dielec.)

Final:  $V = E d = \frac{E_0 d}{k}$  (with dielec.)

$V = \frac{V_0}{k}$

Hence:  $V \downarrow$  from  $V_0 \rightarrow \frac{V_0}{k}$

(2)

ADV



# Capacitance :-  $C = \frac{Q}{\Delta V}$

$C_0 = \frac{Q}{V_0}$  (cap. dielec.)  $\Rightarrow C = \frac{Q}{V} = \frac{Q}{\left(\frac{V_0}{k}\right)} = \frac{kQ}{V_0}$

$C = k_1 C_0$

Hence;  $C \uparrow \Rightarrow$  From  $C_0 \rightarrow C = kC_0$   
 i.e. Increased capacity of storage.

Note :-  $E$  decreases to  $\frac{E_0}{k}$


$V$  " "  $\left(\frac{V_0}{k}\right)$

$C$  increases to  $kC_0$

ADVANTAGE :-

- ① Provide stability to plates
- ② prevent plates from sticking each other.
- ③  $C \uparrow$ .
- ④ can prevent breakdown of medium

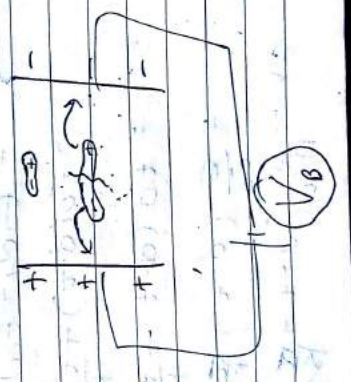
(Use such dielectric which has high B.D. voltage.)





$$(K)_{\text{vacuum}} = \underline{1}$$

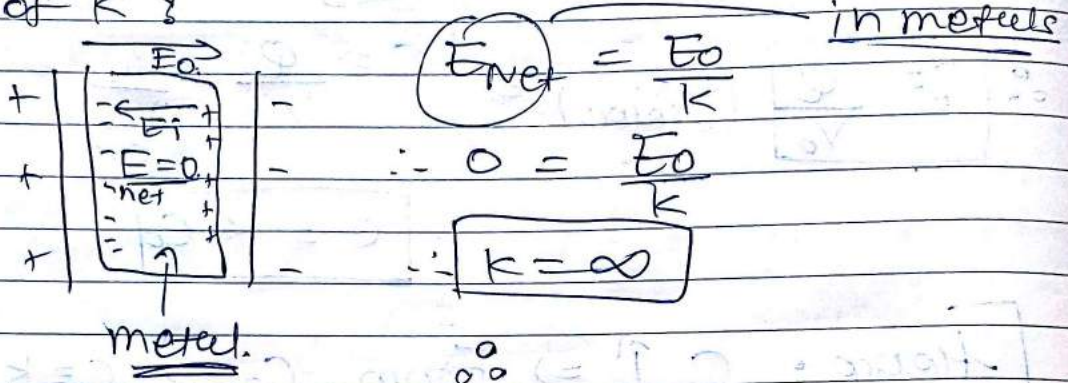Q:- For metals/conductors correct value of  $K$  ?



→  $\sigma_i = ?$

$$\therefore \sigma_i = \sigma \left(1 - \frac{1}{K}\right) = \sigma \left(1 - \frac{1}{\infty}\right) = \sigma$$


$$\boxed{\sigma_i = \sigma}$$

same.

→ In metal  $E_0 = E_i$


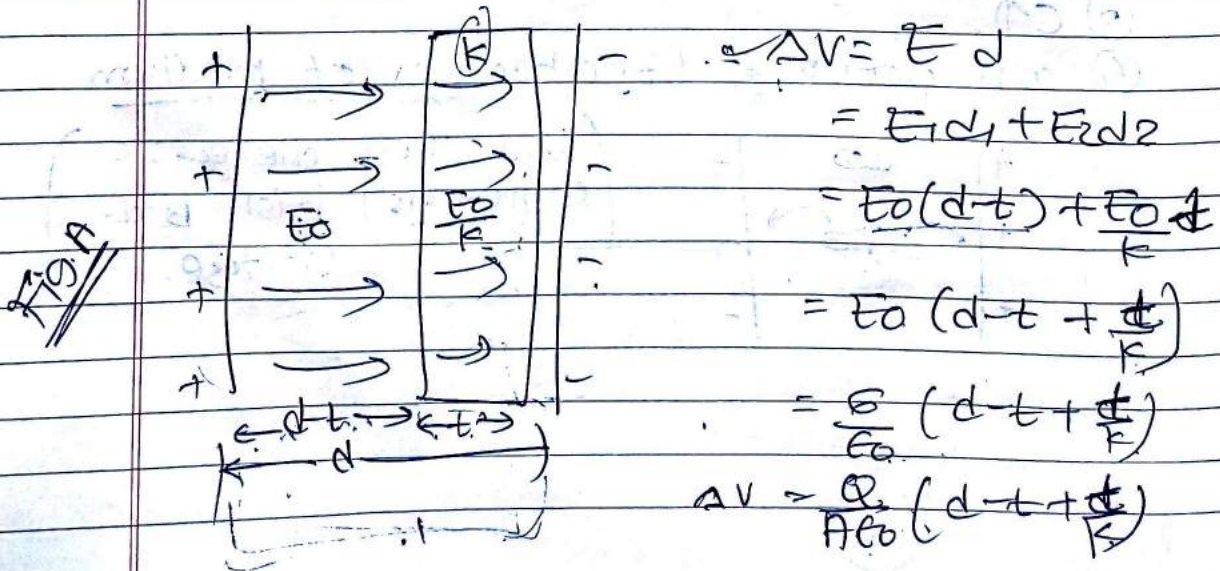
# Capacitor with partially filled Dielectric :-



~~Q19A~~



For metal  $k \rightarrow \infty$

classmate

Date \_\_\_\_\_


Page \_\_\_\_\_

$$\therefore \Delta V = \frac{Q}{A\epsilon_0} \left( d - t + \frac{t}{k} \right)$$

$$\therefore C = \frac{Q}{\Delta V} = \frac{A\epsilon_0}{\left( d - t + \frac{t}{k} \right)} = C$$

$$\left( \because Q = CV \right)$$
$$C = \frac{Q}{V}$$

$C > C_0$

(ii)   $\Rightarrow C = kC_0$

$$C = \frac{k\epsilon_0 A}{d}$$

$\rightarrow$  Fig. A shows two capacitors are in series ( $C_1$  &  $C_2$ )

In air/vacuum  $C_1 = \frac{\epsilon_0 A}{(d-t)}$  ; dielectric  $C_2 = \frac{k\epsilon_0 A}{t}$

$\rightarrow$  For series :-  $\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2}$

$$= \frac{d-t}{\epsilon_0 A} + \frac{t}{k\epsilon_0 A}$$
$$= \frac{d-t}{\epsilon_0 A} + \frac{t/k}{\epsilon_0 A}$$


$$\frac{1}{C_e} = \frac{d-t + t/k}{\epsilon_0 A}$$

$$\therefore C_e = \frac{\epsilon_0 A}{d-t + t/k}$$



Find  $C = ?$ 

Q:-

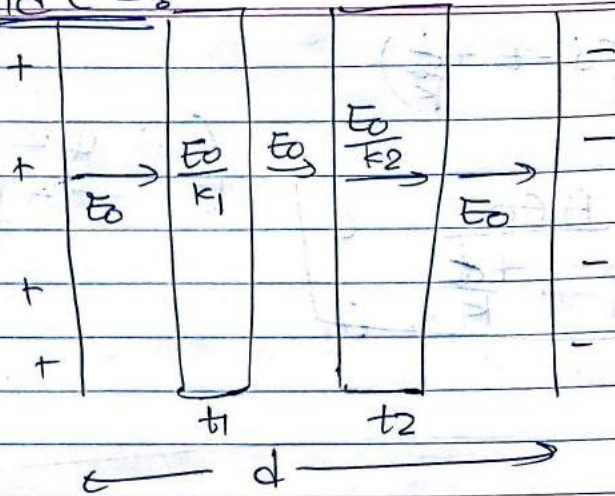

$$\Delta V = E_0 d$$

$$= E_0 d_1 + E_0 d_2 + E_0 d_3$$

(air)      ( $K_1$ )      ( $K_2$ )

$$= E_0 (d - t_1 - t_2) + \left( \frac{E_0}{K_1} \cdot t_1 \right) + \left( \frac{E_0}{K_2} \cdot t_2 \right)$$

$$= E_0 \left( d - t_1 - t_2 + \frac{t_1}{K_1} + \frac{t_2}{K_2} \right)$$

$$\Delta V = \frac{Q}{A \epsilon_0} \left( \dots \right)$$


$$C = \frac{A \epsilon_0}{\left( d - t_1 - t_2 + \frac{t_1}{K_1} + \frac{t_2}{K_2} \right)}$$

For  
n

$$\Rightarrow C = \frac{\epsilon_0 A}{\left( d - t_1 - t_2 - \dots - t_n + \frac{t_1}{K_1} + \frac{t_2}{K_2} + \dots + \frac{t_n}{K_n} \right)}$$





Q:- Find  $c = ?$

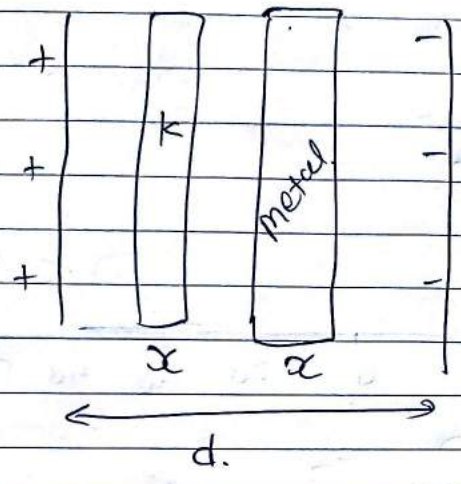



$$C = \frac{\epsilon_0 A}{(d - 2x) + \left(\frac{x}{K} + \frac{x}{\infty}\right)}$$

$$= \frac{\epsilon_0 A}{d - 2x + \frac{x}{K}}$$

# Calculate  $E \rightarrow x$

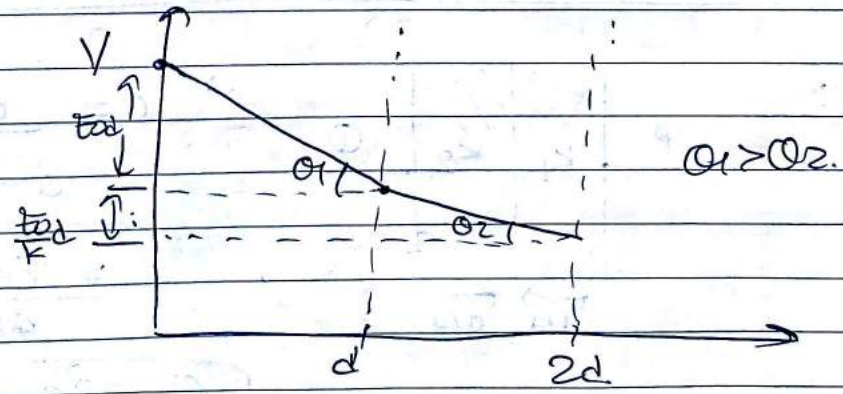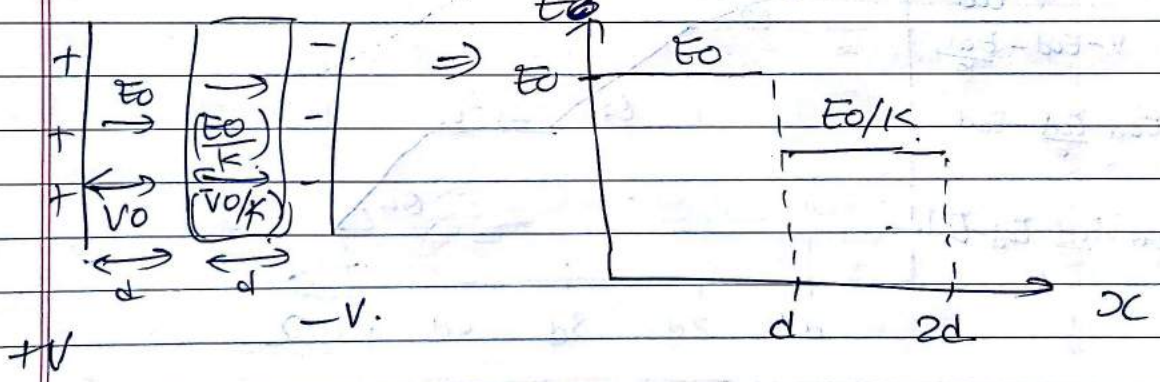



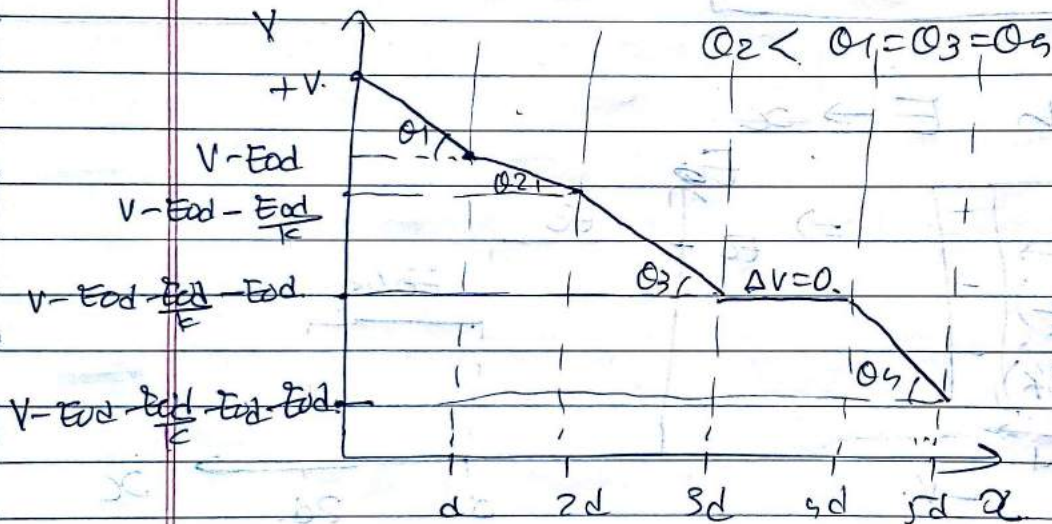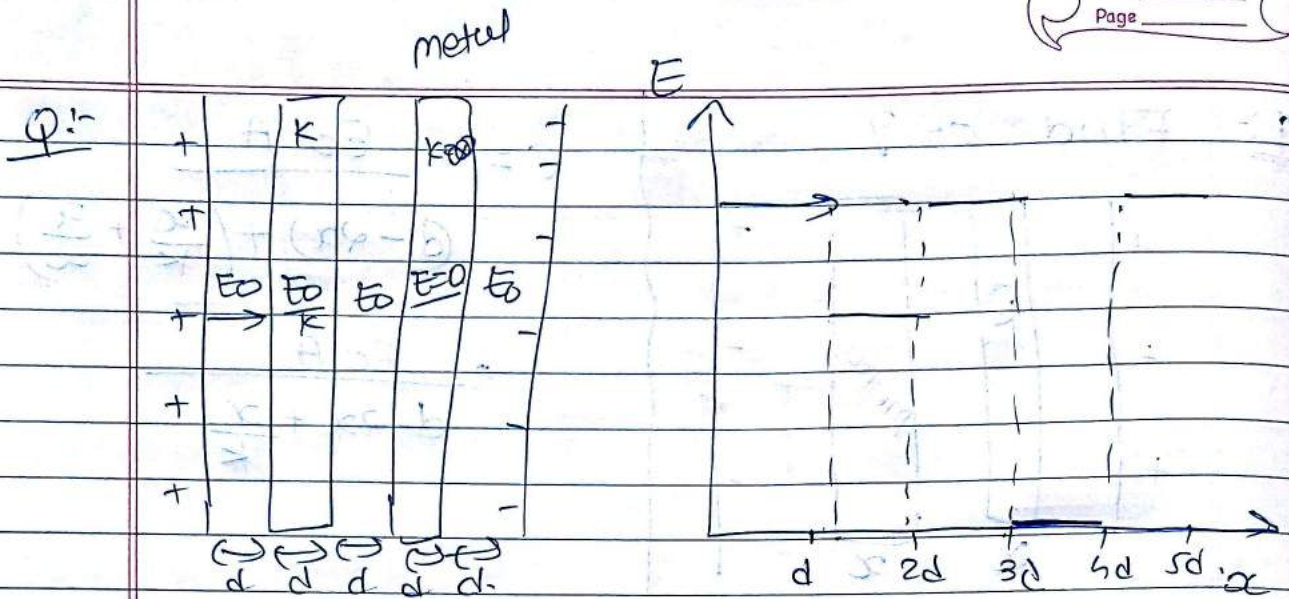

Q:-

$C = \frac{\epsilon_0 A}{\frac{d}{K_1} + \frac{d}{K_2}}$

$d = \left(\frac{d}{2}\right) + \left(\frac{d}{2}\right) + \left(\frac{d}{2}\right) + \left(\frac{d}{2}\right)$

$= \frac{\epsilon_0 A}{\frac{d}{K_1} + \frac{d}{K_2}}$

$C = \frac{2\epsilon_0 A}{d \left( \frac{1}{K_1} + \frac{1}{K_2} \right)}$

(Both caps. are in series.)



$$C_1 = \frac{\epsilon_0 A \kappa_1}{(d/2)} \quad \text{and} \quad C_2 = \frac{\epsilon_0 A \kappa_2}{(d/2)}$$

$$\frac{1}{C_e} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$= \frac{1}{\frac{\epsilon_0 A \kappa_1}{d/2}} + \frac{1}{\frac{\epsilon_0 A \kappa_2}{d/2}}$$

$$= \frac{d}{2\epsilon_0 A \kappa_1} + \frac{d}{2\epsilon_0 A \kappa_2}$$

$$= \frac{d}{2\epsilon_0 A} \left( \frac{1}{\kappa_1} + \frac{1}{\kappa_2} \right)$$

$$\frac{1}{C_e} = \frac{d}{2\epsilon_0 A} \left( \frac{\kappa_2 + \kappa_1}{\kappa_1 \kappa_2} \right)$$


$$C_e = \frac{2\epsilon_0 A}{d} \left( \frac{\kappa_1 \kappa_2}{\kappa_1 + \kappa_2} \right)$$

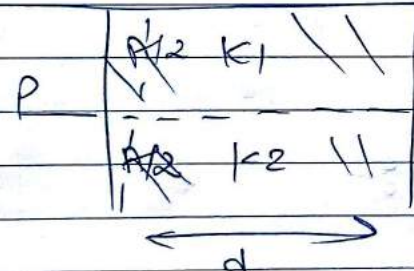Q:  Both are in parallel.

$$\therefore C_{eq} = C_1 + C_2$$

$$= \frac{\epsilon_0 A \kappa_1}{d/2} + \frac{\epsilon_0 A \kappa_2}{d/2}$$


$$C_{eq} = \frac{\epsilon_0 A}{d} (\kappa_1 + \kappa_2)$$

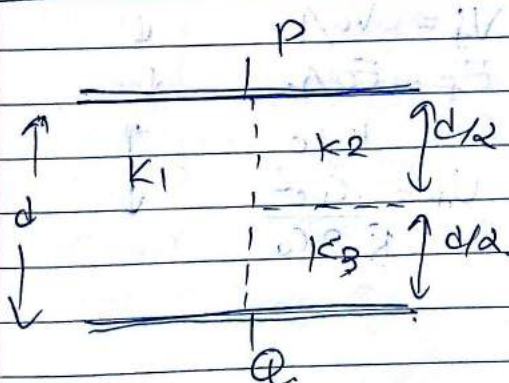Q:  Here 3 capacitors.  $C_2$  &  $C_3$  are in parallel.  $\therefore C_{eq} = (C_2 + C_3) \parallel$  in series with  $C_1$ .


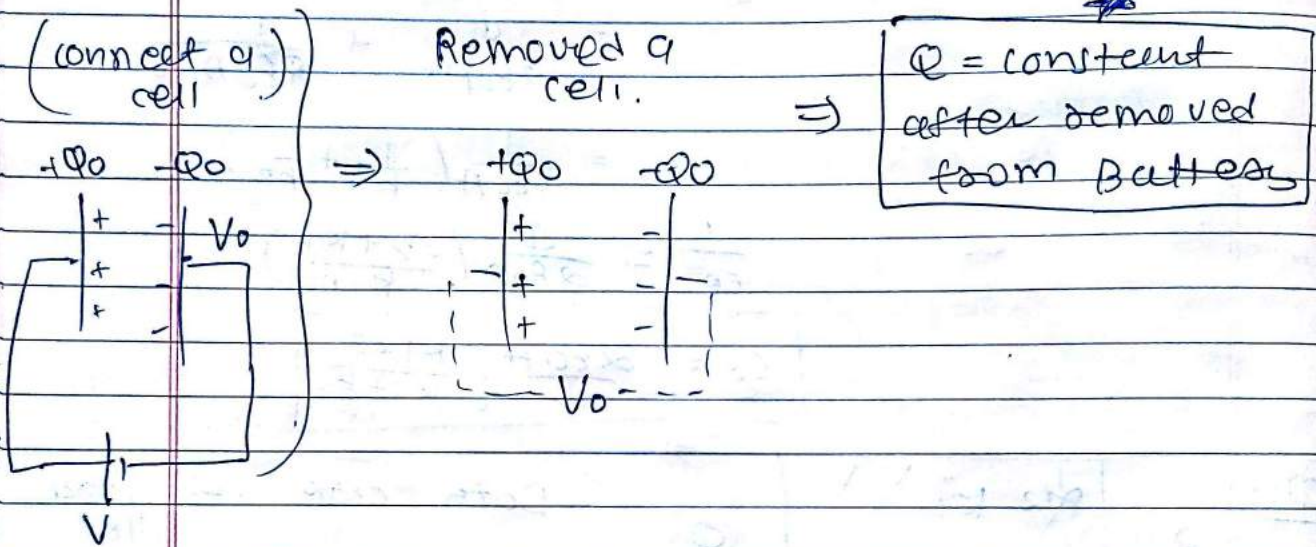
## \* Battery Connected/Removed & Dielectric Inserted :-

Case - I :- Battery Removed & Dielectric Inserted



Now:

$\Rightarrow$  Insert Dielectric slab :-

Before inserted	After inserted	
$\rightarrow Q_i = Q_0$	$\rightarrow Q_f = Q_0$	const
$\rightarrow V_i = V_0$	$\rightarrow V_f = V_0/k$	$\downarrow$
$\rightarrow E_i = E_0$	$\rightarrow E_f = E_0/k$	$\downarrow$
$\rightarrow C_i = C_0$	$\rightarrow C_f = k C_0$	$\uparrow$
$\rightarrow U_i = \frac{Q_0^2}{2C_0}$	$\rightarrow U_f = \frac{Q_0^2}{2kC_0}$	$\downarrow$




$F_{ext}$  (by external agent to remove/avoid acceleration of dielectric)

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_

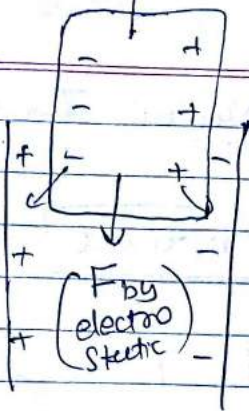

$\therefore$  w.d. by external agent


$$\therefore W_{ext} = F_{ext}(-x)$$

= -ve.

i.e. work is obtained.

$$\left( \begin{aligned} W_{ext} &= \Delta U = U_f - U_i \\ &= \frac{Q_0^2}{2k\epsilon_0} - \frac{Q_0^2}{2\epsilon_0} = \frac{Q_0^2}{2\epsilon_0} \left( \frac{1}{k} - 1 \right) = W_{ext} \end{aligned} \right)$$

# Force on Plates :-

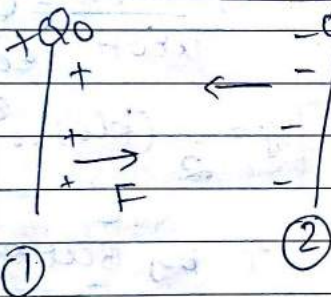

• Force on 2 due to 1

$$\therefore F_{21} = qE_{21}$$

$$= Q_0 \left( \frac{\epsilon}{2\epsilon_0} \right)$$


$$= Q_0 \left( \frac{Q_0}{2A\epsilon_0} \right)$$

$$= \frac{-Q_0^2}{2A\epsilon_0} = F_{21}$$

Initial

i.e.  $F_i = \frac{Q_0^2}{2\epsilon_0 A}$

After

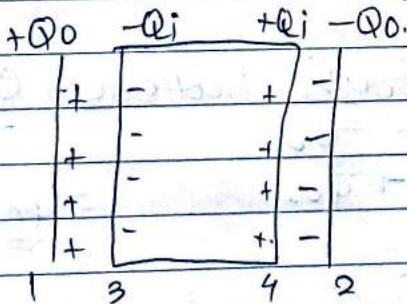

$\therefore E$  on 2 due to 1, 3 & 4.

$$F_2 = \frac{Q_0}{2\epsilon_0 A} - \frac{Q_i}{2\epsilon_0 A} + \frac{Q_i}{2\epsilon_0 A}$$


$$F_2 = \frac{Q_0}{2\epsilon_0 A}$$

$$\Rightarrow F_f = \frac{Q_0^2}{2\epsilon_0 A}$$

Remains same.



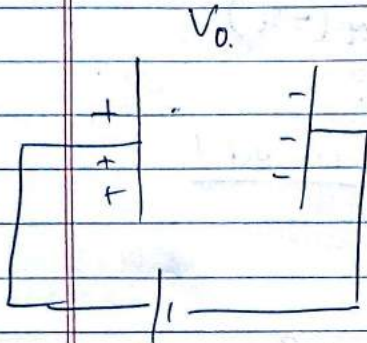Case: (II) Batteries connected + Dielec. Inserted



Here:  $V = \text{constant}$

Before  $k$   
 $C_i = C_0$   
 $V_i = V_0$   
 $Q_i = Q_0$

After  $k$   
 $C_f = k \cdot C_0 \uparrow$   
 $V_f = V_0 = \text{constant}$   
 $Q_f = CV = C_0 k V_0 = k Q_0 \uparrow$

$E_i = E_0 = \frac{Q_0}{\epsilon_0 A}$

$E_f = \frac{Q_f}{k \epsilon_0 A} = \frac{Q_0}{\epsilon_0 A}$  (same)

$E_i = \frac{1}{2} C_0 V_0^2$

$E_f = \frac{1}{2} (k C_0) V_0^2 \uparrow$


( $\uparrow$  by Batteries)

( $W_{ext} = F_{ext}(x) = -V_e$  obtained by Batteries)

# charge supplied through batteries =  $Q_0 k - Q_0$

$Q_i = Q_0$   
 $Q_f = k Q_0$   
 $Q_i = +Q_0$   
 $Q_f = -k Q_0$

$= Q_0(k-1)$

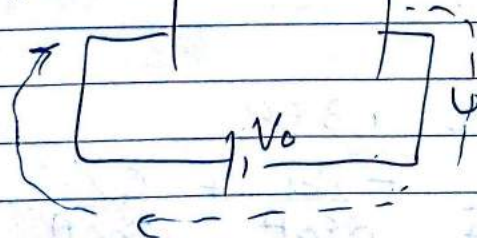

W.D. by Batteries

$= qV$

$= Q_0(k-1)V_0$

$W_{Batt} = Q_0 V_0 (k-1) = C_0 V_0^2 (k-1)$



$$\left\{ \Delta U = U_f - U_i = \frac{1}{2} (C_0 V_0^2) (k-1) \right\} \rightarrow \text{given to capacitor}$$

other half gone to ext. Agent.  $\left\{ W_{\text{ext}} = \frac{1}{2} (C_0 V_0^2) (k-1) \right\}$


Q: Batl. conn. - inserted dielec., in this cond. w.d. by Batter is  $2J$ . what is change in P.E. of dielec.  $\Rightarrow$  Half =  $1J$

other half  $\rightarrow 1J$  to  $\uparrow$  Energy of capacitor
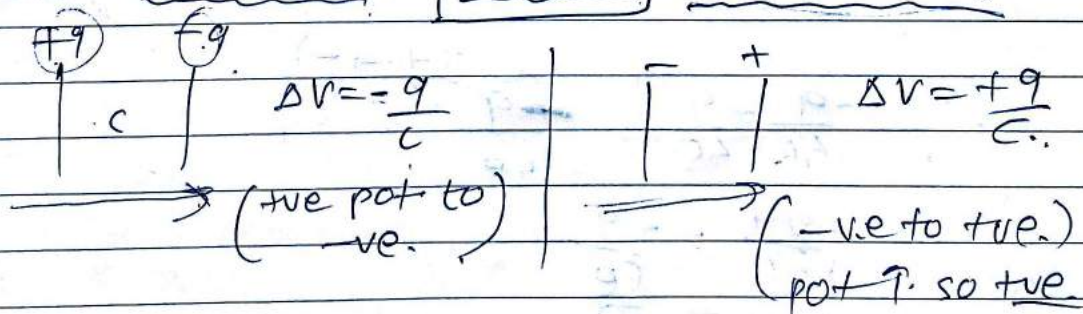
### CHARGE DISTRIBUTION Method :-

All q. are solvable.


- ① connect img. ... cell.
- ② Take +ve charge from +ve ter of cell, -q from -ve ter of cell to ckt.
- ③ Distribute charge on each capel.
- ④ For closed loop  $\left[ \sum \Delta V = 0 \right]$  (K. 2nd law)



- ⑤ Find charge on all capel.
- ⑥ choose 1 path from +ve to -ve terminal of cell
- ⑦ Calculate  $\sum \Delta V$  along one path  
 equate this  $\left[ \sum \Delta V = \frac{+q}{C_0} \right]$




Q.1

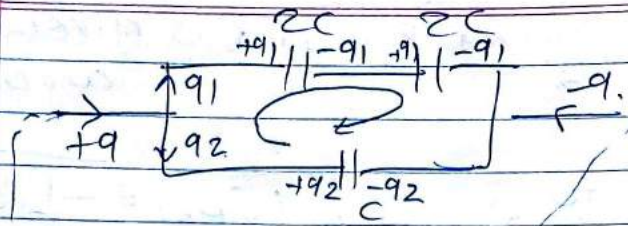

$$[q_1 + q_2 = q] \quad (1)$$

→ closed &  $\sum \Delta V = 0$   
loop

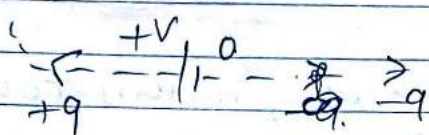

$$\therefore \frac{-q_1}{2C} - \frac{q_1}{2C} + \frac{q_2}{C} = 0$$



$$-\frac{q_1}{C} + \frac{q_2}{C} = 0$$

$$\therefore [q_1 = q_2] \quad (2)$$

i.e.  $q_1 = q_2 = \left[\frac{q}{2}\right]$  → on each cap.

→ 1 part :-
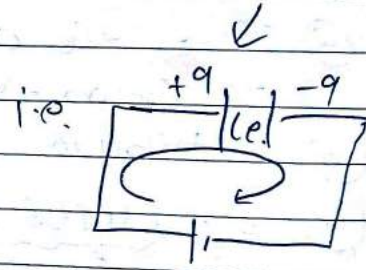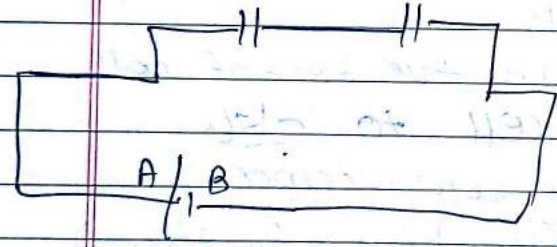
$$\therefore \frac{-q/2}{2C} - \frac{q/2}{2C} = \pm \frac{q}{C_e}$$



$$\therefore \frac{-q}{4C} - \frac{q}{4C} = \frac{+q}{C_e} \quad \left(\frac{+}{q} \rightarrow \frac{-}{q}\right)$$




$$\therefore \frac{-2q}{4C} = \frac{-q}{C_e}$$

$$\therefore [C_e = 2C]$$

Q.2



Q.2.

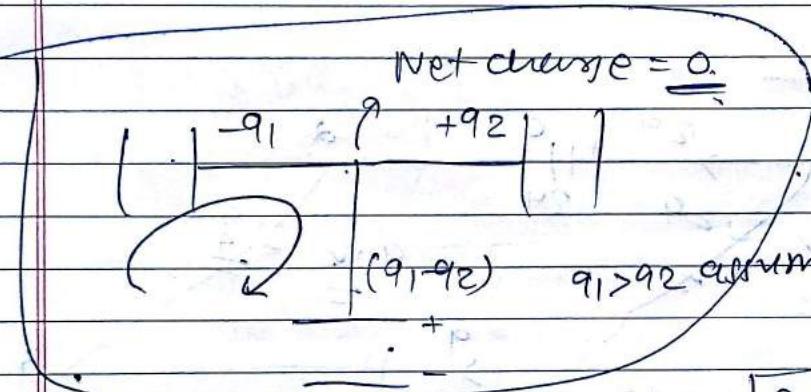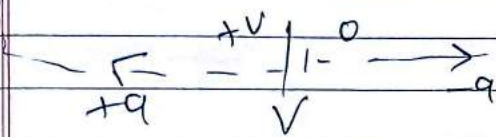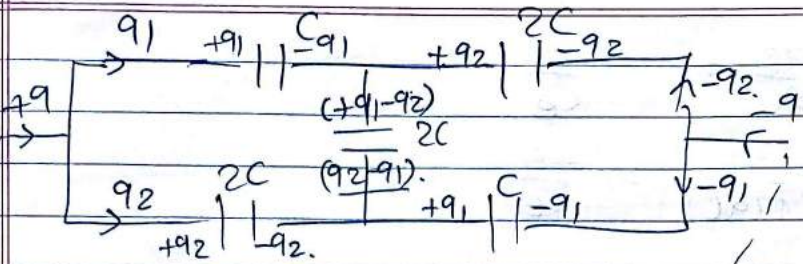

Closed loop :-

$\sum \Delta V = 0$

i.e.  $q_1 + q_2 = q$  — (i)

$\frac{-q_1}{C} - \frac{(q_1 - q_2)}{2C} + \frac{q_2}{2C} = 0$


assumed  $q_1 > q_2$

$q_2 = \frac{3}{2} q_1$  — (ii)

$q_1 = \frac{2}{5} q$  — (A)

$\therefore q_2 = \frac{2}{5} \times \frac{3}{2} q = \frac{3}{5} q = q_2$  — (B)

→ 1 path :-

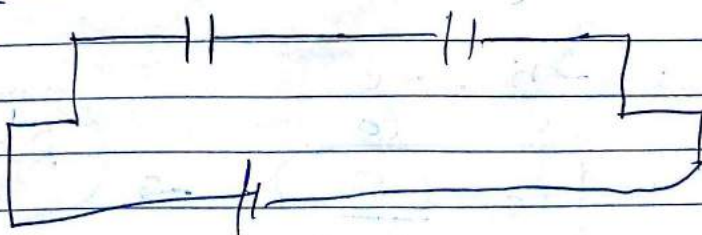




$$\therefore -\frac{9}{C} - \frac{9}{2C} = -\frac{9}{C_e}$$

$$\therefore -\frac{29}{5C} - \frac{39}{5(2C)} = -\frac{9}{C_e}$$

$$\boxed{C_e = \frac{10}{7} C}$$

all are  $C$

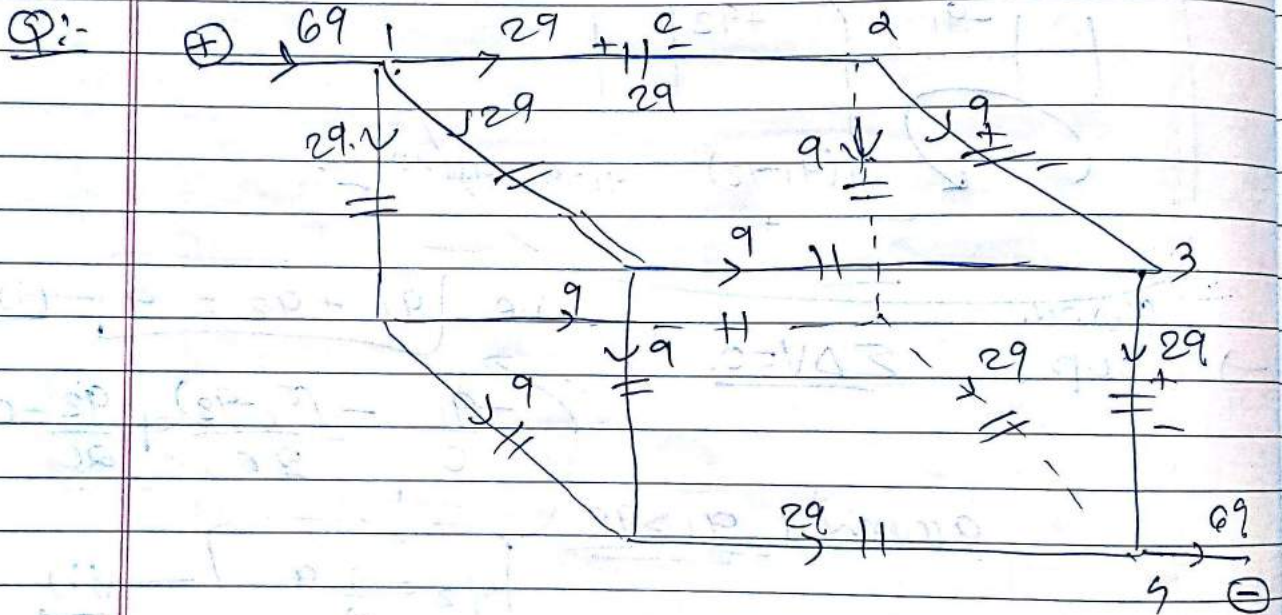

→ 1234 path :-

$$\therefore -\frac{29}{C} - \frac{9}{C} - \frac{29}{C} = -\frac{69}{C_e}$$

$$\therefore -\frac{2+1+2}{C} = -\frac{6}{C_e}$$

$$\therefore \frac{+5}{C} = \frac{+6}{C_e}$$

$$\therefore \boxed{C_e = \frac{6C}{5}}$$


$$\Rightarrow R_{eq} = \frac{5}{6} R$$







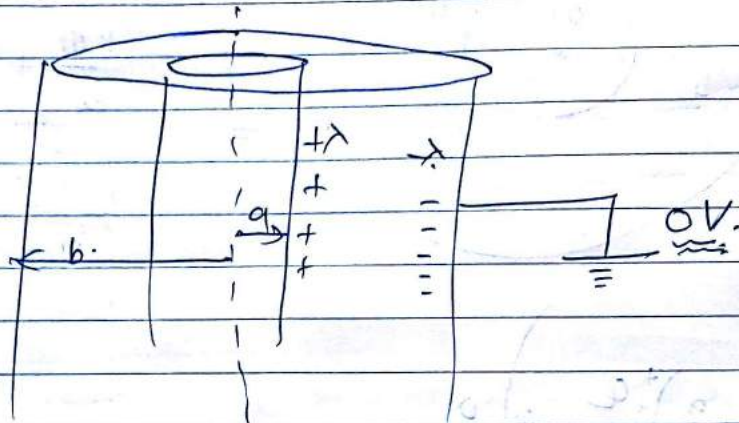A. Cylindrical capacitor :- ( $\infty$  length)



$$\therefore C = \frac{Q}{\Delta V} = \frac{\lambda l}{\Delta V}$$

$$\left[ \frac{C}{l} = \frac{\lambda}{\Delta V} = \text{capac. per unit length} \right]$$

$$(\Delta V) = \int E \cdot dr = \int_a^b \frac{\lambda}{2\pi\epsilon_0 r} dr = \frac{\lambda}{2\pi\epsilon_0} \int_a^b \frac{1}{r} dr$$

$$= \frac{\lambda}{2\pi\epsilon_0} \left[ \log_e r \right]_a^b = \frac{\lambda}{2\pi\epsilon_0} \log_e \frac{b}{a}$$


$$\rightarrow \therefore C = \frac{\lambda}{\frac{\lambda}{2\pi\epsilon_0} \log_e \frac{b}{a}}$$

$$\left[ \frac{C}{l} = \frac{2\pi\epsilon_0}{\log_e(b/a)} \right]$$



$q_B = ?$

Q:-

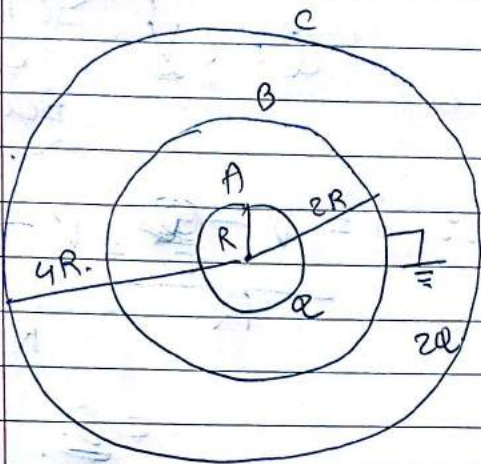

$\therefore V_B = 0$

$\therefore V_{B_A}^{out} + V_B^{sub} + V_B^{in} = 0$


$\therefore \frac{kq}{2R} + \frac{kq}{2R} + \frac{k(2q)}{4R} = 0$

$\therefore q + q + \frac{1}{2}2q = 0$

$\therefore 2q = -q$

$\therefore q = -2q$

\* Circuit with Cap + Resistor :-


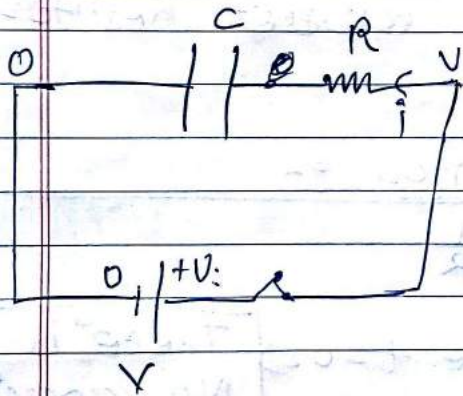


• initial  $\rightarrow$  switch is closed;  
 $\rightarrow t=0 \Rightarrow (q=0)$  cap.

$\therefore (\Delta V)_C = \frac{q}{C} = 0$

$\therefore i = \frac{V}{R}$


at  $t=t$

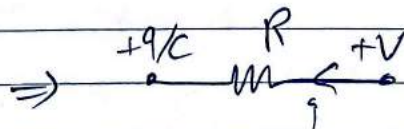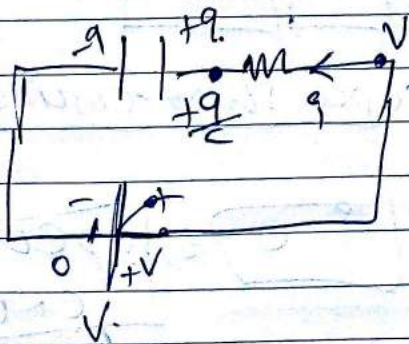

$i = \frac{V - \frac{q}{C}}{R}$



$t = \infty$

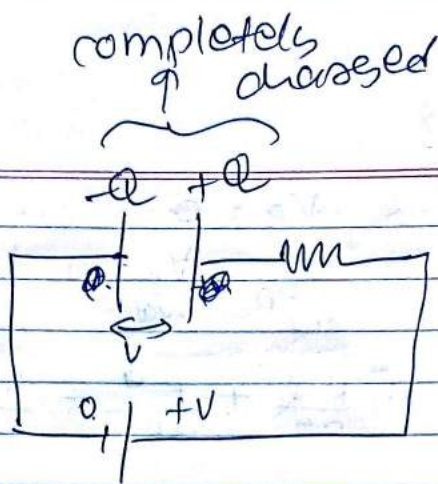

$Q = CV$  same as RC circuit


$$i = \frac{V - \frac{Q}{C}}{R} = \frac{V - \frac{eV}{e}}{R} = 0$$

i.e. caper Fully charged  $\Rightarrow i = 0$  from ckt


i.e. No need of Resistor.

# Two states of capacitor :-

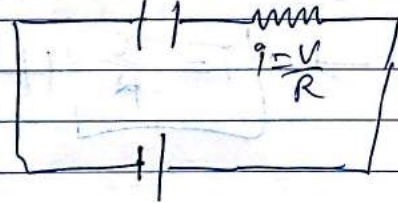1) initial  $\Rightarrow t = 0 \Rightarrow i = \frac{V}{R}$




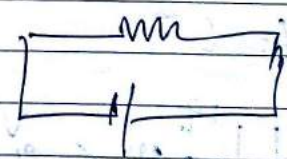i.e.  $t = 0 \Rightarrow$  There is NO capacitor




capacitor short-circuited

ii)  $t = \infty$ , steady state

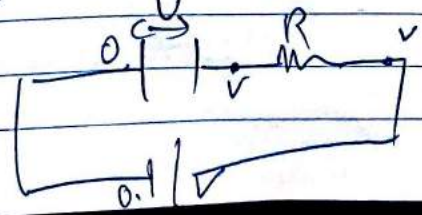


$i = 0 \Rightarrow$  open ckt

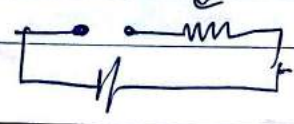




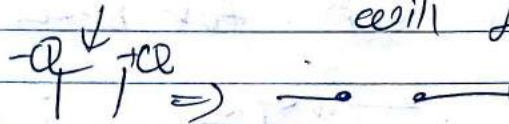Capac.  $\Rightarrow$  Fully charged  $\Rightarrow$  No current will flow




Q.2)

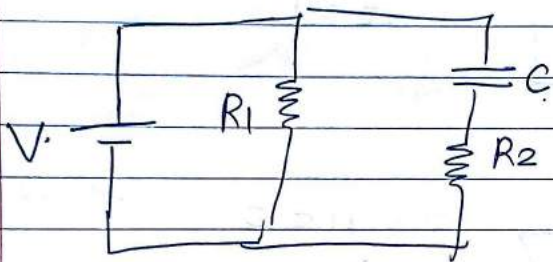

• Find current  $i_1$  &  $i_2$  in each resistor at


i)  $t=0$

ii) Steady state

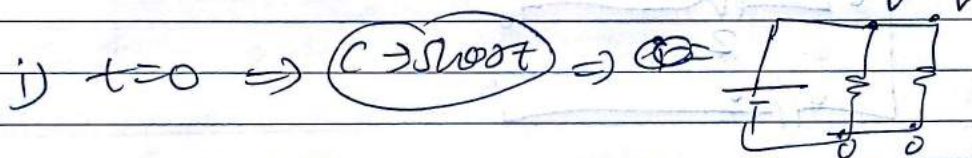



~~$\therefore R = \frac{R_2 R_1}{R_1 + R_2} \Rightarrow i = \frac{V}{R} = \frac{V}{R_2}$~~   $i_1 = \frac{V}{R_1}$   
 $i_2 = \frac{V}{R_2}$

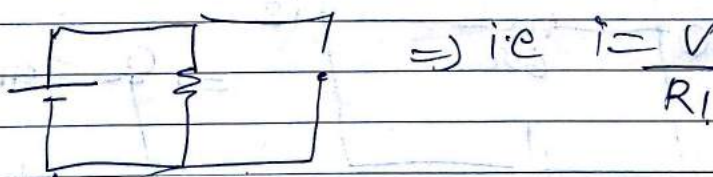ii)  $t = \infty$  steady  $\Rightarrow$  capac is open ckted.





2) Find Eq. Resistance at i)  $t=0$

ii)  ~~$t = \infty$~~  steady state

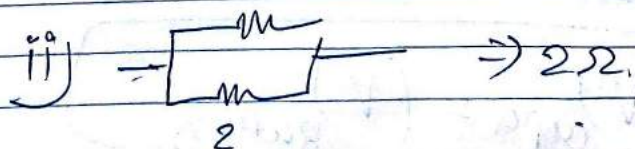
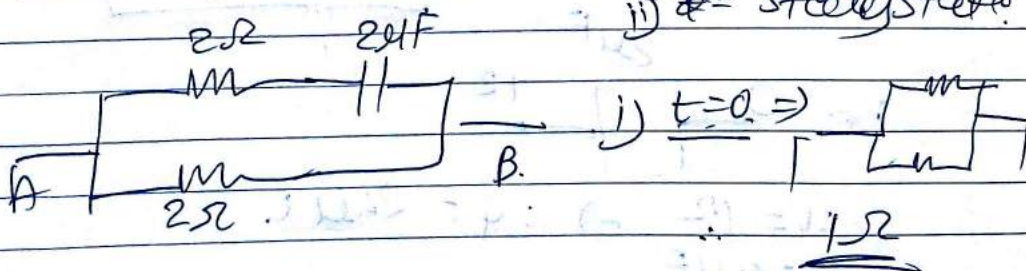




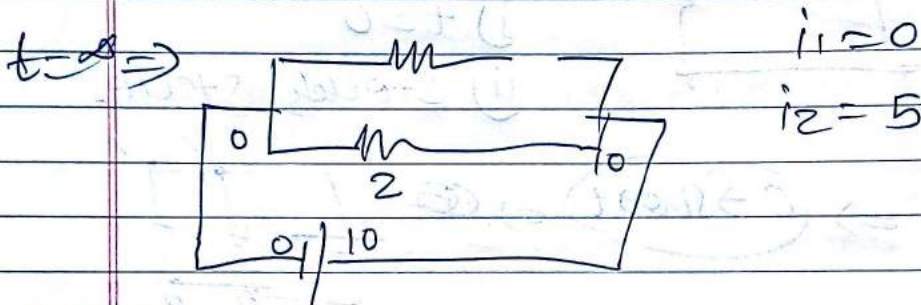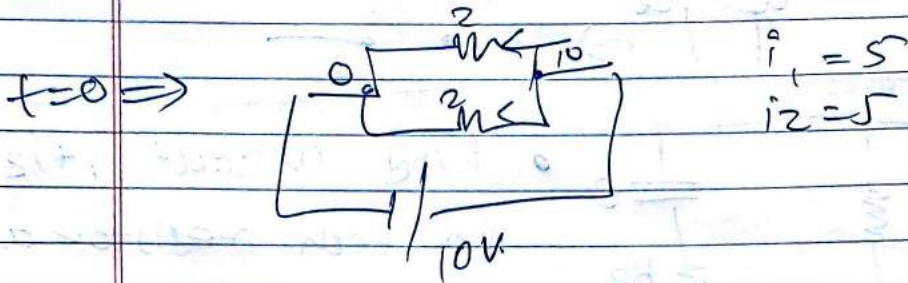Q.3) Find current in each branch in prev. ex for both cases 10V 5



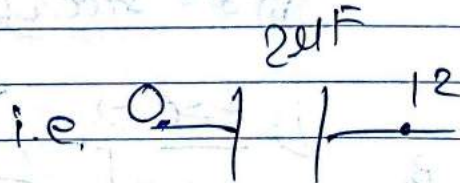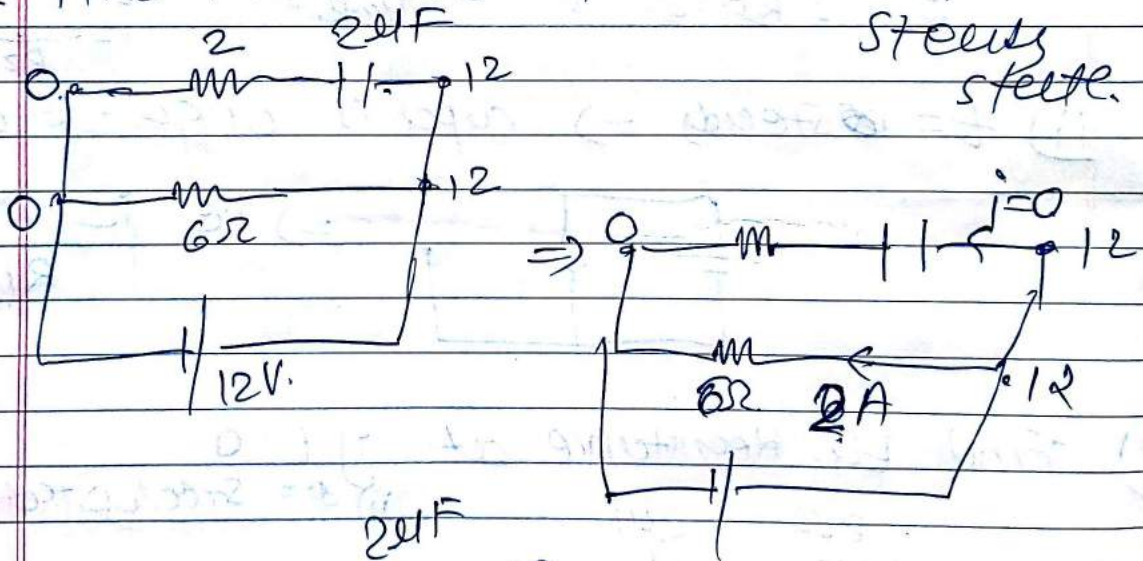Q.4.) Find the charge stored on cap. in steady state.




$\therefore V = 12 \Rightarrow \therefore Q = 24 \mu C$   
 $C = 2 \mu F$

$\Rightarrow$  Steady state  $(V)_{capa} = (V)_{battery}$




⑤

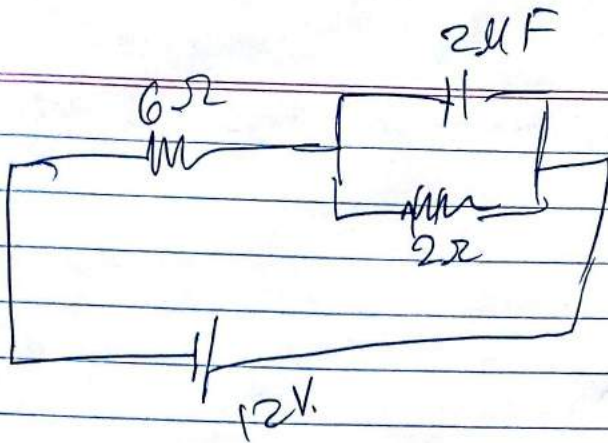

\* Find charge on cap<sup>n</sup> in steady state

→ steady state ⇒ open cap<sup>n</sup>.

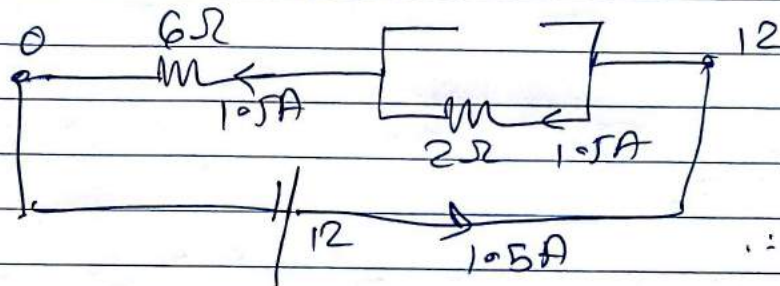

$$i = \frac{V}{R}$$

$$\therefore i = \frac{12}{6+2} = \frac{12}{8}$$

$$\therefore i = \frac{3}{2} = 1.5A$$

$$\therefore V_{2\Omega} = IR$$

$$= 1.5 \times 2$$

$$V_{2\Omega} = 3 \text{ volt} \Rightarrow V_C = 3V$$

$$Q = CV$$

$$= 2\mu \times 3 = \underline{\underline{6\mu C}}$$