

CAPACITOR



1 Capacitor



Capacitor is a passive device of the circuit which stores electrical energy or charge. It is also known as **condenser**.

$$C = \frac{Q}{V} \quad \text{or} \quad C = \frac{\epsilon_0 A}{d}$$

Capacitance is measured in **Farad (F)**

Q = Charge


A = Area

V = Voltage

d = Diameter

2 Combination

i Series

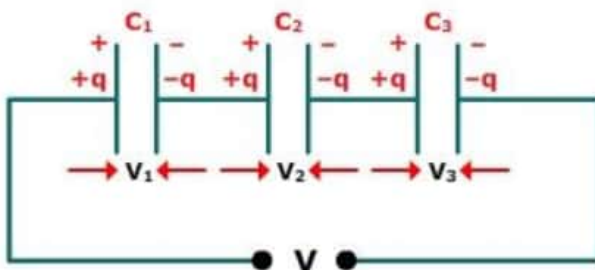

- Charge stored on each capacitor is same and equal to the magnitude of the charge, which comes from the battery..

$$Q = q_1 = q_2 = q_3$$


- The sum of voltage across the individual capacitor is equal to the voltage of the battery.

$$V = V_1 + V_2 + V_3$$

- $$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

- Equivalent capacitance of the capacitor is always less than the smallest value of the capacitance of the capacitor in the circuit.

ii Parallel

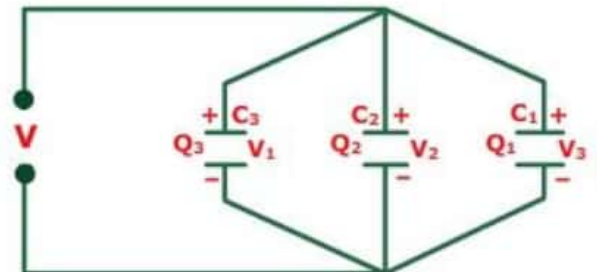

- The Voltage across each capacitor is the same, and it is equal to the voltage of the battery.

$$V = V_1 = V_2 = V_3$$

- The sum of the charge stored on an individual capacitor is equal to the magnitude of the charge, which comes from the battery.

$$Q = q_1 + q_2 + q_3$$

- $$C_{eq} = C_1 + C_2 + C_3$$

- Equivalent capacitance of the capacitor is always greater than the largest value of the capacitance of the capacitor in the circuit.

CIRCUIT SOLUTION

CHARGING AND DISCHARGING OF A CAPACITOR

CHARGING OF A CAPACITOR

$q = q_0 [1 - e^{-\frac{t}{RC}}]$

Where q_0 = maximum final value of charge at $t = \infty$.
Time $t = RC$ is known as **Time Constant**.

$I = I_0 [e^{-\frac{t}{RC}}]$

During charging

During discharging

If $t = RC = \tau$ = Time constant
Then, $I = 0.37 I_0$

DISCHARGING OF A CAPACITOR

$q = q_0 [e^{-\frac{t}{RC}}]$


$q = \frac{q_0}{e} = 0.37 q_0$

If $t = RC = \tau$ = time constant,
Then, $q = 0.37 q_0$

FORCE BETWEEN THE PLATES OF A CAPACITOR


$$F = - \frac{d}{dx} \left[\frac{q^2}{2\epsilon_0 A} x \right] = \frac{-1}{2} \frac{q^2}{\epsilon_0 A}$$

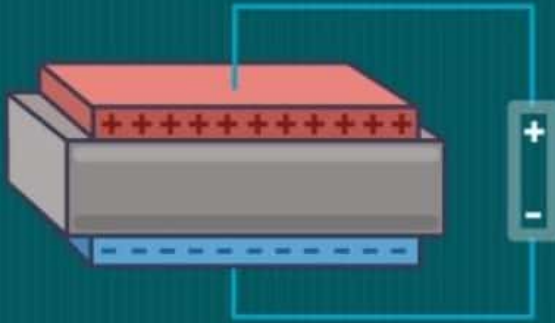The negative sign implies that the force is attractive.



CAPACITOR WITH DIELECTRIC

1. Without Dielectric

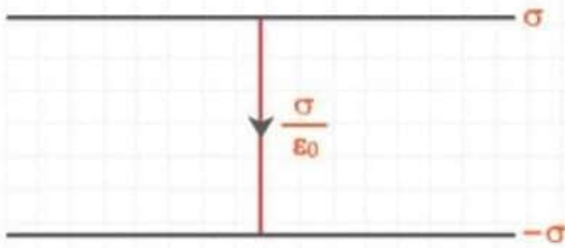

$$E = \frac{\sigma}{\epsilon_0}$$


2. With Dielectric



$$C = \frac{AK\epsilon_0}{d}$$


A = Area of Dielectric Slab

3. Dielectric Placed Vertically

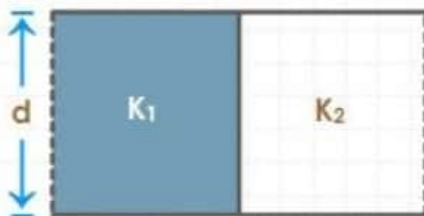

$$C = C_1 + C_2 \rightarrow C = \frac{\epsilon_0(K_1 + K_2)A}{2d}$$

4. Dielectric Placed Horizontally

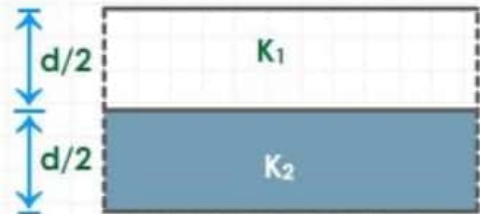

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \rightarrow C = \frac{2\epsilon_0 AK_1 K_2}{(K_1 + K_2)d}$$

5. Dielectric Placed Diagonally



$$C = \frac{\epsilon_0 AK_1 K_2}{(K_2 - K_1)} \log_e \frac{K_1}{K_2}$$

6. Capacitor With 3 Dielectrics



$$C = \frac{\epsilon_0 A}{d} \left[\frac{K_1}{2} + \frac{K_2 K_3}{K_2 + K_3} \right]$$