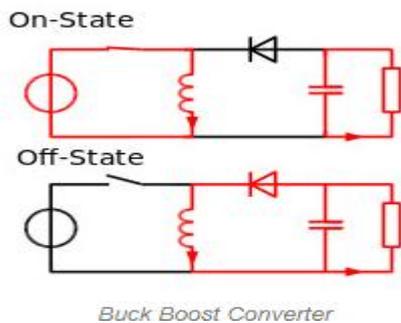


## Buckboost converter

It is a type of DC to DC converter and it has a magnitude of output voltage. It may be more or less than equal to the input voltage magnitude. The buck boost converter is equal to the fly back circuit and single inductor is used in the place of the transformer. There are two types of converters in the buck boost converter that are buck converter and the other one is boost converter. These converters can produce the range of output voltage than the input voltage. The following diagram shows the basic buck boost converter.



### Working principle of Buck Boost Converter


The working operation of the DC to DC converter is the inductor in the input resistance has the unexpected variation in the input current. If the switch is ON then the inductor feed the energy from the input and it stores the energy of magnetic energy. If the switch is closed it discharges the energy. The output circuit of the capacitor is assumed as high sufficient than the time constant of an RC circuit is high on the output stage. The huge time constant is compared with the switching period and make sure that the steady state is a constant output voltage  $V_o(t) = V_o(\text{constant})$  and present at the load terminal.

There are two different types of working principles in the buck boost converter.

- Buck converter.
- Boost converter.
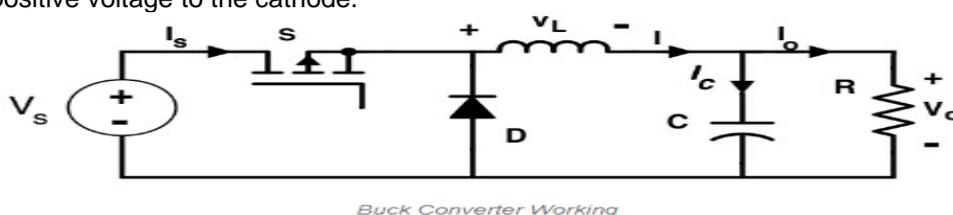
### Buck Converter Working

The following diagram shows the working operation of the buck converter. In the buck converter first transistor is turned ON and second transistor is switched OFF due to high square wave frequency. If the gate terminal of the first transistor is more than the current pass through the magnetic field, charging C, and it supplies the load. The D1 is the Schottky diode and it is turned OFF due to the positive voltage to the cathode.




The inductor L is the initial source of current. If the first transistor is OFF by using the control unit then the current flow in the buck operation. The magnetic field of the inductor is collapsed and the back e.m.f is generated collapsing field turn around the polarity of the voltage across the inductor. The current flows in the diode D2, the load and the D1 diode will be turned ON. The discharge of the inductor L decreases with the help of the current. During the first transistor is in one state the charge of the accumulator in the capacitor. The current flows through the load and during the off period keeping  $V_{out}$  reasonably. Hence it keeps the minimum ripple amplitude and  $V_{out}$  closes to the value of  $V_s$

### Boost Converter Working

In this converter the first transistor is switched ON continually and for the second transistor the square wave of high frequency is applied to the gate terminal. The second transistor is in conducting when the on state and the input current flow from the inductor L through the second transistor. The negative terminal charging up the magnetic field around the inductor. The D2 diode cannot conduct because the anode is on the potential ground by highly conducting the second transistor. By charging the capacitor C the load is applied to the entire circuit in the ON State and it can construct earlier oscillator cycles. During the ON period the capacitor C can discharge regularly and the amount of high ripple frequency on the output voltage. The approximate potential difference is given by the equation below.

$$V_S + V_L$$

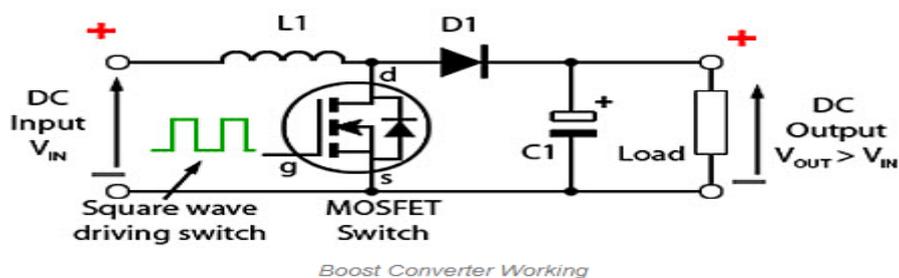

During the OFF period of second transistor the inductor L is charged and the capacitor C is discharged. The inductor L can produce the back e.m.f and the values are depending up on the rate of change of current of the second transistor switch. The amount of inductance the coil can occupy. Hence the back e.m.f can produce any different voltage through a wide range and determined by the design of the circuit. Hence the polarity of voltage across the inductor L has reversed now.

The input voltage gives the output voltage and atleast equal to or higher than the input voltage. The diode D2 is in forward biased and the current applied to the load current and it recharges the capacitors to  $V_S + V_L$  and it is ready for the second transistor.