

AC \rightarrow



Date / /


Page

Resistor containing circuit,

Capacitor containing circuit,

Inductor containing circuit,

Resistor containing circuit,

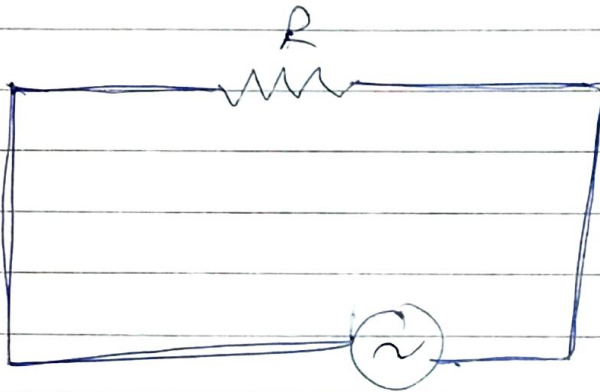

$$V = V_0 \sin \omega t$$



By using Ohm's law,

$$V = I R$$


$$I = \frac{V_0 \sin \omega t}{R}$$

$$I = I_0 \sin \omega t$$

Phasor diagram

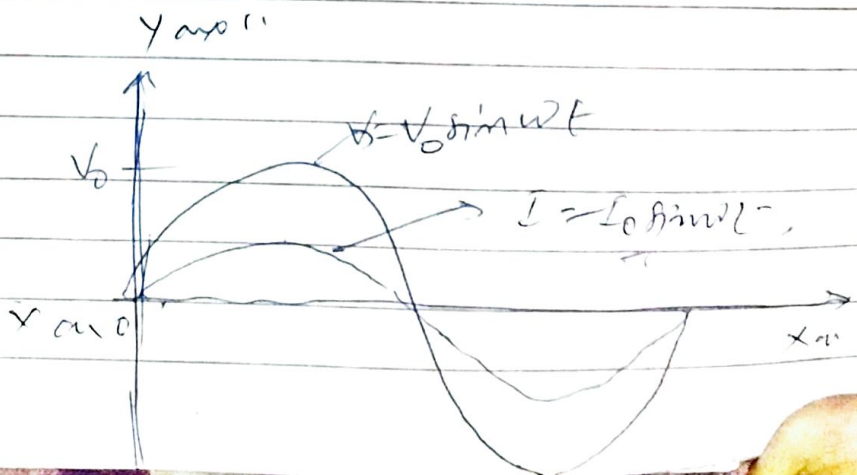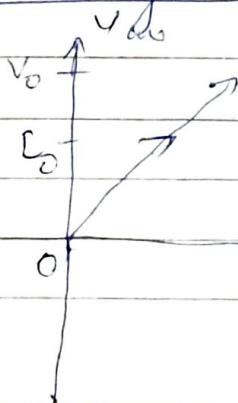

Capacitive circuit,

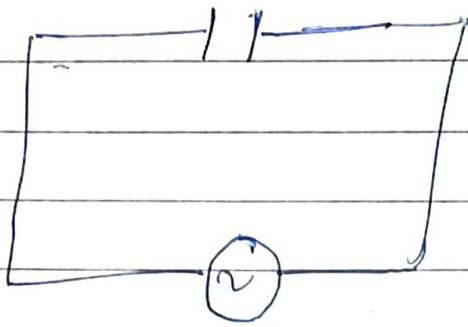

$$V = V_0 \sin \omega t$$

Consider a capacitor of capacitance C connected in the circuit. The P.D. is

$$V = V_0 \sin \omega t$$

~~we know~~

$$q = CV$$

$$q = C V_0 \sin \omega t$$

$$i = \frac{dq}{dt}$$

$$i = \frac{d(C V_0 \sin \omega t)}{dt}$$

$$\frac{d \sin \omega t}{dt} = \omega \cos \omega t$$

$$i = C \omega V_0 \cos \omega t$$

$$i = \frac{V_0}{1/\omega C} \cos \omega t$$


$$i = i_0 \cos \omega t$$

$$= \frac{1}{\omega C}$$

capacitive


Reactance
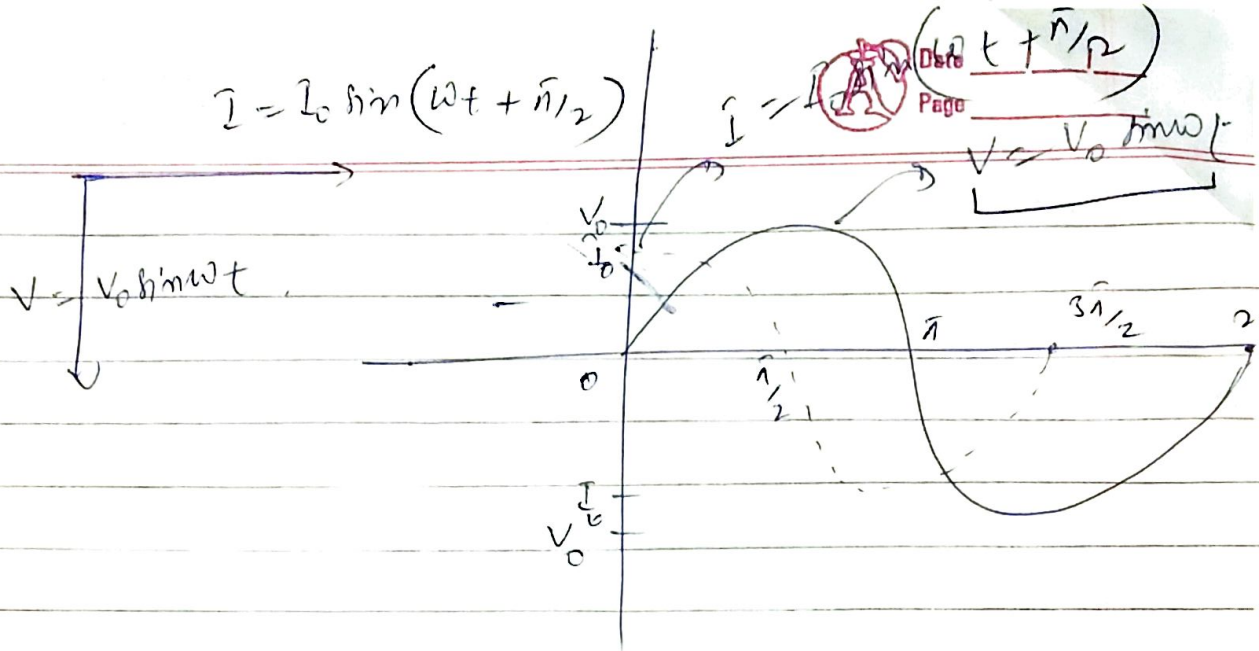
$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$



Inductors containing inductor,

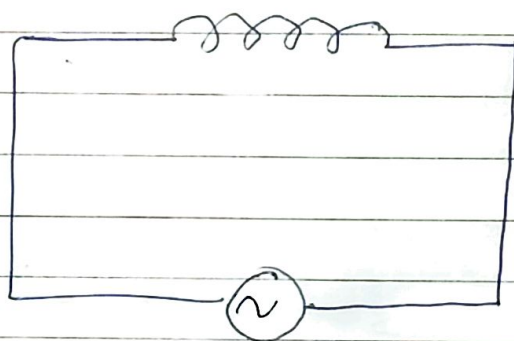If an Inductor
of Inductance L
connected
in the circuit
then
P.d
 $V = V_0 \sin \omega t$



$$V = V_0 \sin \omega t$$

$$E = - \left(-L \frac{dI}{dt} \right) \quad \text{fs ac supply}$$

$$E = L \frac{dI}{dt}$$

$$V_0 \sin \omega t = L \frac{dI}{dt}$$

$$\int L dI = \int V_0 \sin \omega t dt$$

$$I = \frac{V_0}{L\omega} (-\cos \omega t)$$

Date _____
Page _____

$$\int \sin \omega t \, dt = -\frac{\cos \omega t}{\omega}$$

$$= \frac{V_0}{L\omega} \sin(\omega t - \pi/2)$$

$$X_L = L\omega$$

This is called Inductive Reactance.

$$I = I_0 \sin(\omega t - \pi/2)$$

